

Alternating Current

⇒ Capacitor growth and decay = $t = I \ln 2 = \tau \ln 2 = \tau \left(\frac{1}{R}\right) \ln 2$.

* Root mean square Current (RMS) :-

$$I_{\text{rms}} = \sqrt{\langle I^2 \rangle}$$

Ex! $I = I_0 \sin \omega t$

$t=0$ to $t = \frac{2\pi}{\omega}$

$$= I^2 = I_0^2 \sin^2 \omega t$$

RMS

$$\langle I^2 \rangle = \frac{\int_0^{2\pi/\omega} I^2 dt}{\int dt}$$

$$\langle I^2 \rangle = \frac{\int_0^{2\pi/\omega} I_0^2 \sin^2 \omega t dt}{\int dt}$$

$$\langle I^2 \rangle = I_0^2 \frac{\int_0^{2\pi/\omega} (1 - \cos 2\omega t) dt}{2}$$

$$= \frac{\omega I_0^2}{2\pi \times 2} \left[t - \frac{\sin 2\omega t}{2\omega} \right]_0^{2\pi/\omega}$$

$$= \frac{\omega I_0^2}{4\pi} \left((t-0) - \frac{1}{2\omega} \left[\frac{\sin 2\omega \times 2\pi}{\omega} - \sin 0 \right] \right)$$

$$= \frac{\omega I_0^2}{4\pi} \left(\frac{2\pi}{\omega} \right)$$

$$\langle I^2 \rangle = \frac{\omega I_0^2}{4\pi} \left(\frac{2\pi}{\omega} \right)$$

$$\langle I^2 \rangle = \frac{I_0^2}{2}$$

mean square
Current

$$I_{rms} = \frac{I_{max}}{\sqrt{2}}$$

$$I_{rms} = \sqrt{\langle I^2 \rangle} = \sqrt{\frac{I_0^2}{2}}$$

$$I_{rms} = \frac{I_0}{\sqrt{2}} = 0.707 I_0$$

Area under the
curve
time int

* Note:

$$\theta = 0 \text{ to } 2\pi$$

$$\langle \sin \theta \rangle = 0$$

$$\langle \cos \theta \rangle = 0$$

$$\langle \sin^2 \theta \rangle = \frac{1}{2}$$

$$\langle \cos^2 \theta \rangle = \frac{1}{2}$$

$$\frac{\text{max value} + \text{min value}}{2}$$

(Ex-2): $I = I_0 \sin \omega t$

$$I^2 = I_0^2 \sin^2 \omega t$$

$$\langle I^2 \rangle = I_0^2 \langle \sin^2 \omega t \rangle$$

$$\langle I^2 \rangle = \frac{I_0^2}{2}$$

$$I_{rms} = \sqrt{\frac{I_0^2}{2}} = \frac{I_0}{\sqrt{2}}$$

Ex! $V = V_0 \cos \omega t$

$$V = IR = \frac{V}{R}$$

$$V^2 = V_0^2 \cos^2 \omega t$$

$$\langle V^2 \rangle = V_0^2 \langle \cos^2 \omega t \rangle$$

$$\langle V^2 \rangle = V_0^2 \times \frac{1}{2}$$

$$V_{rms} = \sqrt{\frac{V_0^2}{2}} = \frac{V_0}{\sqrt{2}} \text{ Ans}$$

Ex $I = a + b \sin \theta$ $I_{rms} = ?$

~~$I^2 = a^2 + b^2 \sin^2 \theta$~~
 ~~$\langle I^2 \rangle = a^2 + b^2 \langle \sin^2 \theta \rangle$~~

~~$I_{rms} = (a^2 + b^2) \times \frac{1}{2}$~~

~~$I_{rms} = \sqrt{\frac{a^2 + b^2}{2}}$~~

$I^2 = a^2 + b^2 \sin^2 \theta + 2ab \sin \theta$

$\langle I^2 \rangle = a^2 + b^2 \langle \sin^2 \theta \rangle + 2ab \langle \sin \theta \rangle$

$\langle I^2 \rangle = a^2 + b^2 \times \frac{1}{2} + 2ab \times 0$

$\langle I^2 \rangle = \frac{a^2 + b^2}{2} = \frac{2a^2 + b^2}{2}$

$I_{rms} = \sqrt{\langle I^2 \rangle}$

$= \sqrt{\frac{2a^2 + b^2}{2}}$

Ex: $a \sin \theta + b \cos \theta$

$I^2 = a^2 \sin^2 \theta + b^2 \cos^2 \theta + 2ab \sin \theta \cos \theta$
 $= 2 \sin \theta$


$= a^2 \sin^2 \theta + b^2 \cos^2 \theta$

$\langle I^2 \rangle = \frac{a^2}{2} + \frac{b^2}{2} + ab \langle \sin 2\theta \rangle$

$I_{rms} = \sqrt{\frac{a^2}{2} + \frac{b^2}{2}} = \sqrt{\frac{a^2 + b^2}{2}}$

$= \frac{\sqrt{a^2 + b^2}}{\sqrt{2}}$

Ex 1

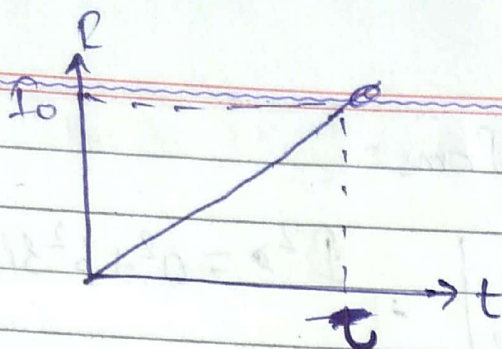

$$y = mx$$

$$I = \frac{I_0}{\tau} t$$

$$I^2 = \frac{I_0^2}{\tau^2} t^2$$

$$\langle I^2 \rangle = \int_0^{\tau} I^2 dt$$


$$\int_0^{\tau} dt$$

$$\langle I^2 \rangle = \frac{I_0^2}{\tau^2} \frac{\int_0^{\tau} t^2 dt}{\int_0^{\tau} dt}$$


$$\langle I^2 \rangle = \frac{I_0^2}{\tau^2} \frac{\tau^3}{3\tau} = \frac{I_0^2}{3}$$

$$\Rightarrow \boxed{I_{rms} = \sqrt{\frac{I_0^2}{3}} = \frac{I_0}{\sqrt{3}}} \quad \text{less}$$

(14-2)

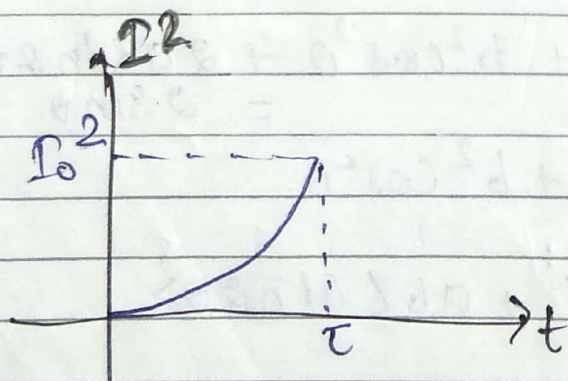

Ex!

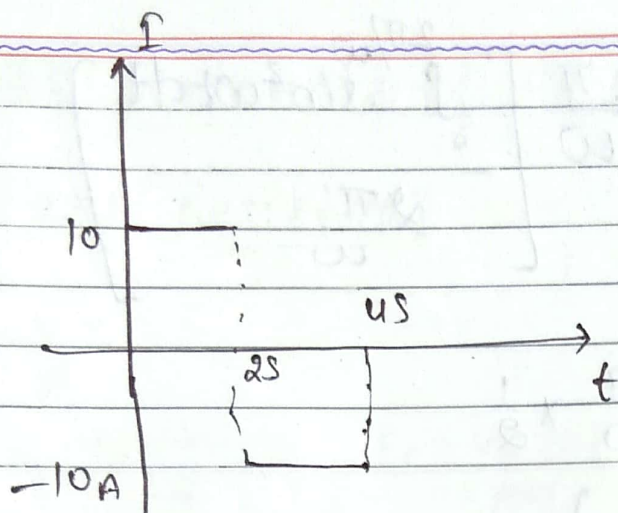

find out I_{rms} b/w $t=0$ to $t=4\text{ Sec}$.


$$\langle I^2 \rangle = \frac{\int_0^4 I^2 dt}{\int_0^4 dt}$$

$$= \frac{\text{Area}}{4}$$

$$\langle I^2 \rangle = \frac{400}{4} = 100.$$

$$I_{\text{rms}} = \sqrt{100} = 10\text{ A}$$

Ex!

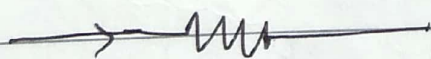

$$I = I_0 \sin \omega t \quad t=0 \text{ to } t = \frac{2\pi}{\omega}$$

$$H = ?$$

$$H = \int I^2 R dt$$

$$H = \int_0^{\frac{2\pi}{\omega}} I_0^2 R \sin^2 \omega t dt =$$

$$I_{dc} = I_{rms} = \frac{I_0}{\sqrt{2}}$$


$$H = I_0^2 R \times \frac{2\pi}{\omega} \left[\int_0^{2\pi/\omega} \sin^2 \omega t dt \right]$$

$$H = I_0^2 R \frac{2\pi}{\omega} \times \frac{1}{2}$$

$$H = \frac{I_0^2}{2} R \left(\frac{2\pi}{\omega} \right)$$

$$H = \left(\frac{I_0}{\sqrt{2}} \right)^2 R \frac{2\pi}{\omega}$$
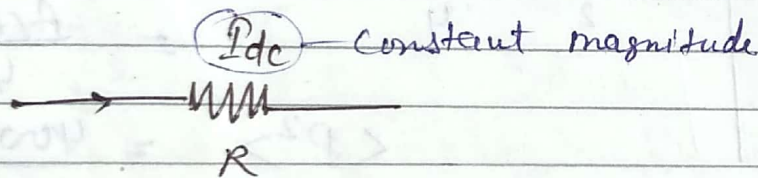
$$H = I_{rms}^2 R \left(\frac{2\pi}{\omega} \right)$$



$$H = I_{dc}^2 R \frac{2\pi}{\omega}$$

$$I_{dc} = I_{rms}$$


Note: AC Ammeter and Voltmeter ~~placed~~ are based on heating effect of current and measure rms value.

* Avg. current and Avg. voltage for AC is considered zero for long time interval

* Elements of AC:

(i) Pure Resistor:

$$i = \frac{V \cdot t}{R}$$

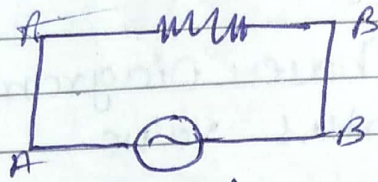


$$V = v_0 \sin \omega t$$

$$i = \frac{v_0 \sin \omega t}{R} \quad i_0 = \frac{v_0}{R}$$

$$i = \frac{i_0 \sin \omega t}{R} \quad i_0 = \frac{v_0}{R} \quad I = I_0 \sin \omega t$$

$$I_{rms} = \frac{I_0}{\sqrt{2}} \quad \frac{V_0}{R}$$



$$I_{rms} = \frac{V_{rms}}{R}$$

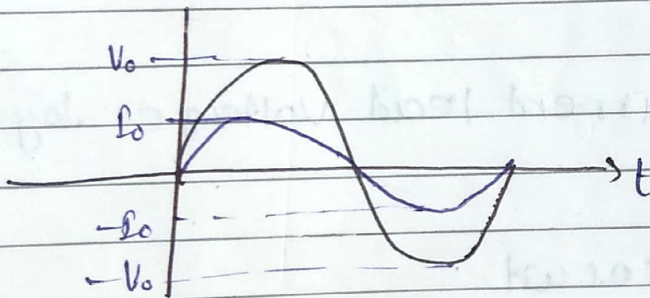

$$V = V_0 \sin \omega t$$

$$I = I_0 \sin \omega t$$

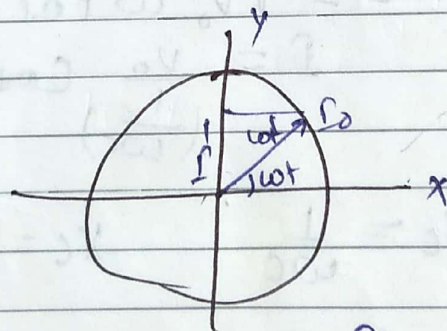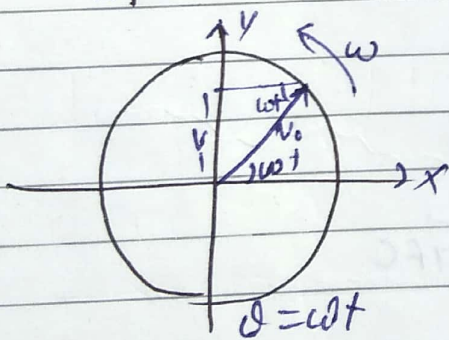
$$\Delta \phi = \omega t - \omega t = 0$$



$$I = I_0 \sin \omega t$$

$$\sin \omega t = \frac{V}{V_0}$$

$$V = V_0 \sin \omega t$$

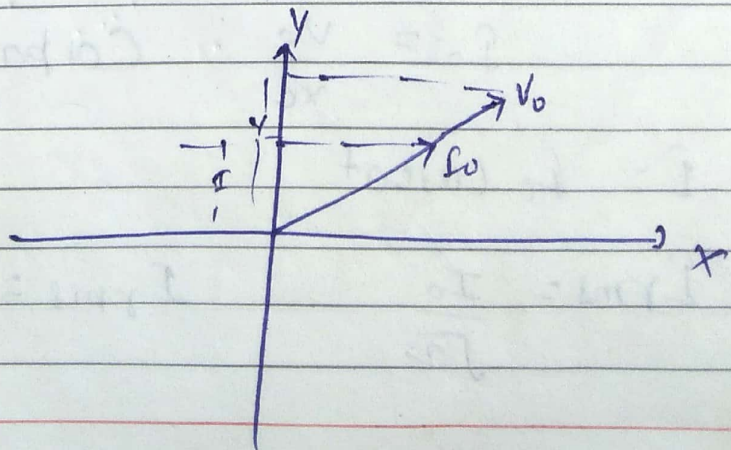

* In Pure Resistor Current and voltage are in same phase


* In Phasor Diagram Projection on y axis represent Instantaneous value

(iii) Pure Capacitor!

$$q = CV$$

$$q = CV_0 \sin \omega t$$

$$I = \frac{dq}{dt}$$

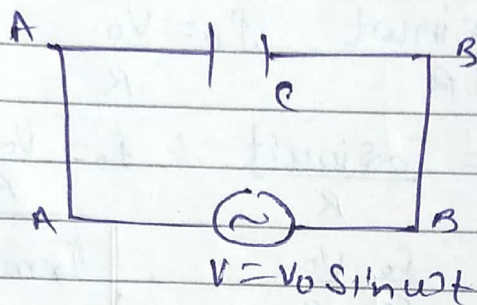

In Pure Capacitor current lead voltage by an angle $\pi/2$.

$$I = CV_0 \omega \cos \omega t$$

$$I = \frac{V_0 \cos \omega t}{\left(\frac{1}{\omega C}\right)}$$

$$X_C = \frac{1}{\omega C}$$

$$X_C = \frac{1}{2\pi f C}$$

$$I = \frac{V_0 \cos \omega t}{X_C}$$

$$I_0 = \frac{V_0}{X_C}$$

Capacitive Reactance

$$X_C = \frac{1}{\omega C} \text{ unit } \Omega$$

$$I = I_0 \cos \omega t$$

$$I_{rms} = \frac{I_0}{\sqrt{2}}$$

$$I_{rms} = \frac{1}{\sqrt{2}} \frac{V_0}{X_C}$$

Q2 upto 21
34, 35, 36
J-M

$$I_{rms} = \frac{V_{rms}}{X_C}$$


$$V = V_0 \sin \omega t$$

$$I = I_0 \cos \omega t$$

$$I = I_0 \sin \left(\frac{\pi}{2} + \omega t \right)$$

$$\Delta \phi = \frac{\pi}{2} + \omega t - \omega t$$


$$\Delta \phi = \frac{\pi}{2}$$

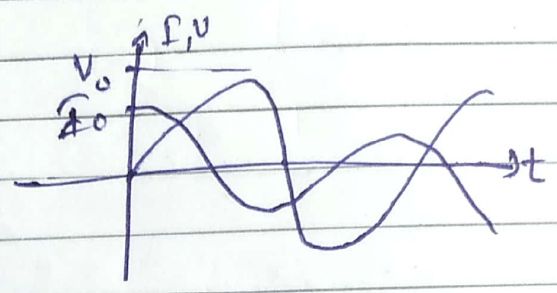

* LCR : circuit :

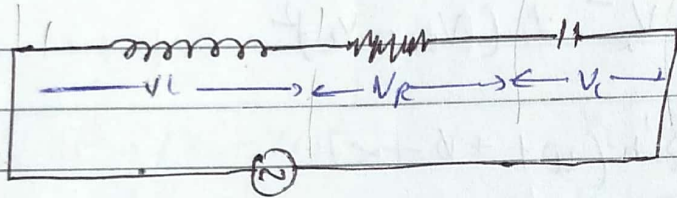(1) In series LCR circuit current remains same in all three elements ~~only~~ potential difference across the elements are different

2] To find Rms value, avg. value or maximum value we draw phaser for voltage and current in all the three elements



$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$V_{net} = \frac{V_0 \sin(\omega t + \phi + \alpha)}{\text{amplitude}}$$

$$(1) V_0 = \sqrt{V_R^2 + (V_L - V_C)^2}$$



$$(2) V_0 = I^2$$

$$(3) Z (\text{Impedance}) = \sqrt{R^2 + (X_L - X_C)^2}$$

$$(4) \tan \alpha = \left(\frac{X_L - X_C}{R} \right)$$

$$V = IR$$

$$I = \frac{V}{R}$$

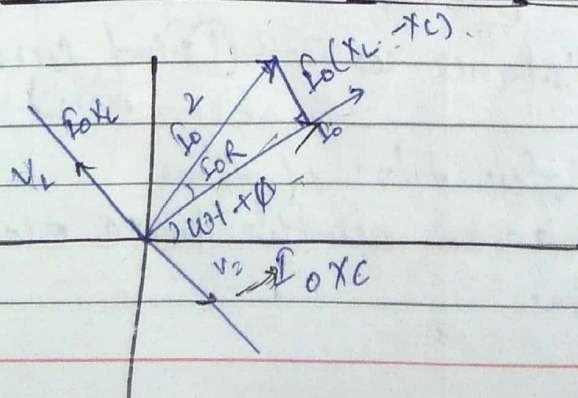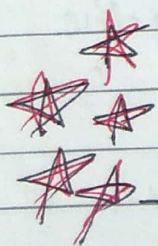

Important

Watt less \Rightarrow Loss
Power factor = $\cos \phi$

Phase diff
 $= \tan^{-1}$

PDP
 HNB

$$i = I_0 \sin(\omega t + \phi)$$

$$V_L = I_0 X_L \sin(\omega t + \phi + \pi/2)$$

$$V_R = I_0 R \sin(\omega t + \phi)$$

$$V_C = I_0 X_C \sin(\omega t + \phi - \pi/2)$$

$$V_0 = V_L + V_R + V_C$$

$$I_0 R \sin(\omega t + \phi + \pi/2) + I_0 R \sin(\omega t + \phi) + I_0 X_C \sin(\omega t + \phi - \pi/2)$$

$$I_0^2 Z^2 = I_0^2 R^2 + I_0^2 (X_L - X_C)^2$$

$$V_{\text{net}}^2 = V_R^2 + (V_L - V_C)^2$$

$$V = V_0 \sin(\omega t + \phi + \alpha)$$

Phase Diff. $\Rightarrow \tan \alpha = \frac{I_0 (X_L - X_C)}{I_0 R}$

* Impedance:


Net Resistance offered by the circuit to the flow of current is known as Impedance, denoted by Z .

Ques: Inductor, Capacitor and Resistor are connected in series to an AC source of emf

$250 \text{ V} \sin(100\pi t + \frac{\pi}{6})$ Capacitance having capacitance of $\frac{500}{\pi} \text{ mf}$. Inductance = is of value.

50 mH . Resistance 5Ω (Find current in the circuit).

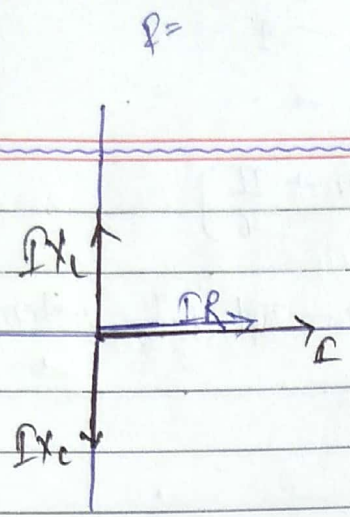- (i) Current as a function of time.
- (ii) Voltage drop across all the three elements as a function of time.



$$B^2 = h^2 - p^2$$

$$B^2 = h^2 - p^2$$

$$h = 15 \text{ mH}$$

$$\frac{18}{20} = \frac{15}{20}$$

$$125 = 25$$

$$\sqrt{100} = 10$$

$$h^2 = 25 +$$

$$p^2 = 10^2 - 15^2$$

$$B^2 = h^2 - p^2$$

$$h^2 = B^2 + p^2$$

$$E_{mf} = 250 \text{ V} \sin(100\pi t + \frac{\pi}{6})$$

$$C = \frac{500}{\pi} \text{ mF}$$

$$L = \frac{5}{\pi} \text{ mH}$$

$$R = 0.5 \text{ } \Omega$$

$$Z = \sqrt{(R)^2 + (X_L - X_C)^2}$$


$$X_L - X_C =$$

$$\omega L - \frac{1}{\omega C} =$$

$$= 100\pi \times \frac{50}{\pi} - \frac{1}{100}$$

$$Z = \sqrt{\quad}$$

$$\frac{15}{25}$$

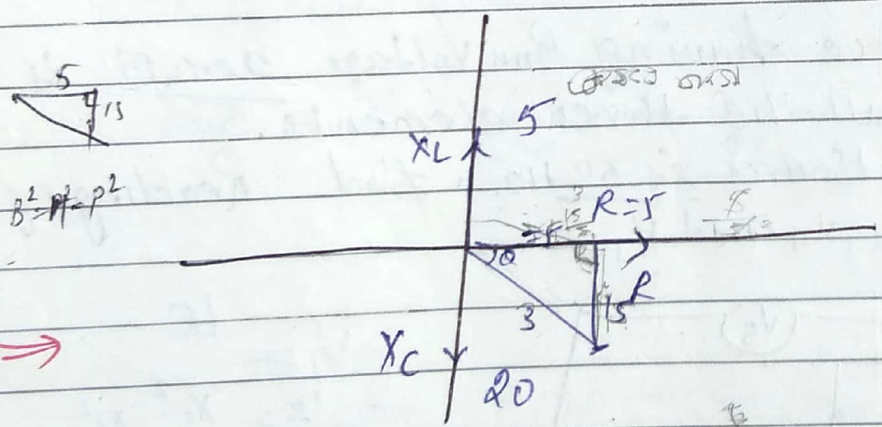

$$X_L = \omega L = 100\pi \times \frac{50}{\pi} \times 10^{-3}$$

$$= 5 \text{ } \Omega$$

$$X_C = \frac{1}{\omega C} = \frac{1}{100\pi \times \frac{500}{\pi} \times 10^{-2}}$$

$$= 20$$

$$R = 5$$

$$Z = \sqrt{(15)^2 + (5)^2}$$

$$= 5\sqrt{10} = \sqrt{250}$$

$$V = IR \Rightarrow V_0 = IZ$$

$$250 = I \sqrt{250}$$

$$I = \sqrt{250} \text{ A}$$

C - D.

L →

② $V = 250 \sin [100\pi t + \frac{\pi}{6}]$

$I = \sqrt{250} \sin (100\pi t + \frac{\pi}{6} + \tan^{-1}(3))$.

③ $V = IR$


$V_L = 5\sqrt{250} \sin (100\pi t + \frac{\pi}{6} + \tan^{-1}(3) + \frac{\pi}{2})$

$V_R = 5\sqrt{250} \sin [100\pi t + \frac{\pi}{6} + \tan^{-1}(3)]$


$V_C = 20\sqrt{250} \sin [100\pi t + \frac{\pi}{6} + \tan^{-1}(3) - \frac{\pi}{2}]$

Q. In an AC circuit L C R are in series comb.
 L of inductor = 1000 mH. = $\frac{1}{\pi}$ H. C have value of $\frac{100}{\pi}$ MF. Resistance of Resistor is 100Ω .

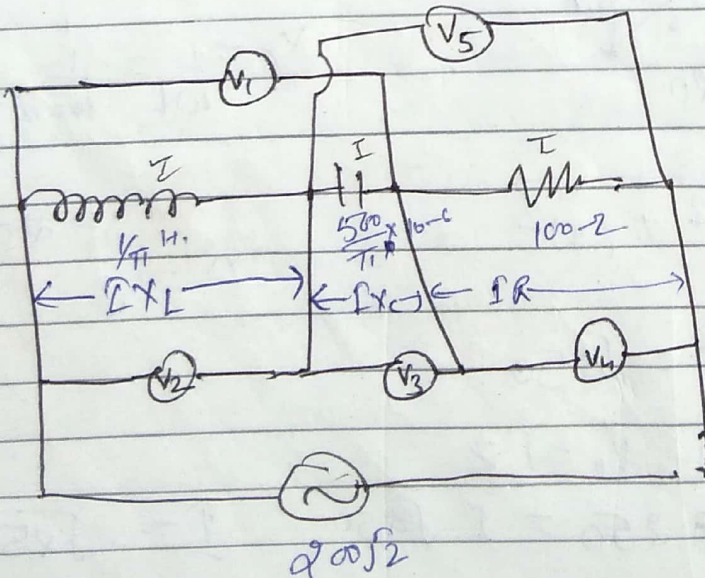An AC source having Rms Voltage $200\sqrt{2}$ is applied across all the three elements.
 frequency of AC source is 50 Hz. find Reading of Voltmeter V_1, V_2, V_3, V_4 and V_5



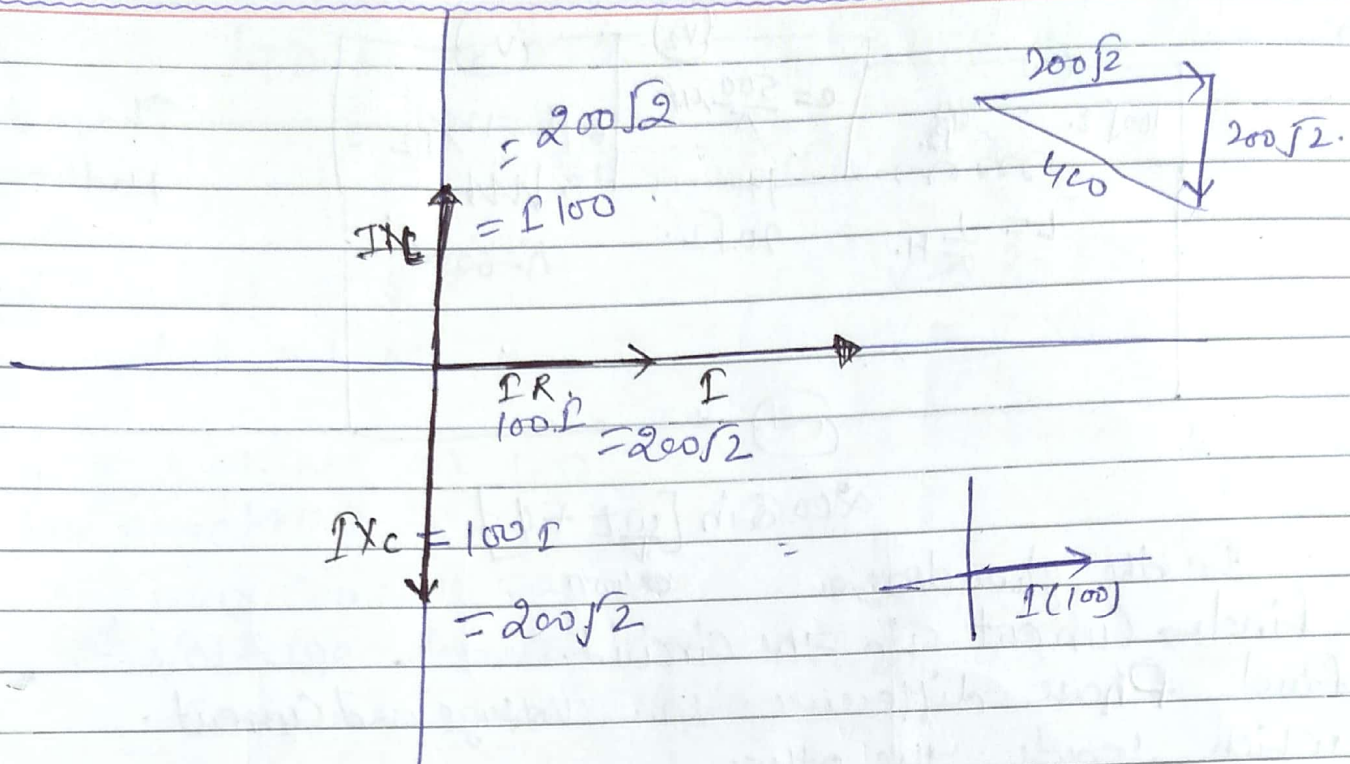$V_1 = LC$
 $Z = X_C^2 + X_L^2$
 $Z = (\frac{1}{100})^2 + (100)^2$
 $Z = \frac{1}{2\pi f C} + 2\pi f L$
 $= \frac{1}{2\pi \times 50 \times \frac{100}{\pi} \times 10^{-6}} + 2\pi \times 50 \times \frac{1}{\pi}$



$$X_L = \omega L = 2\pi 50 \frac{1000}{\pi} \times 10^{-3}$$

$$I = \frac{V}{R}$$

$$X_L = 100$$

$$V = 100$$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi/50 \times \frac{100}{\pi} \times 10^{-6}}$$

$$\frac{200\sqrt{2}}{100} = I$$

$$I = 2\sqrt{2}$$

$$X_L = \underline{100}$$

$$I_{total} = 100 = 200\sqrt{2}$$

$$\boxed{I = 2\sqrt{2}}$$


$$V_{total} = 100$$

$$200\sqrt{2} = 2\sqrt{2} \times 2 = Z = 100 \text{ A}$$



Based on set Am.

Q →

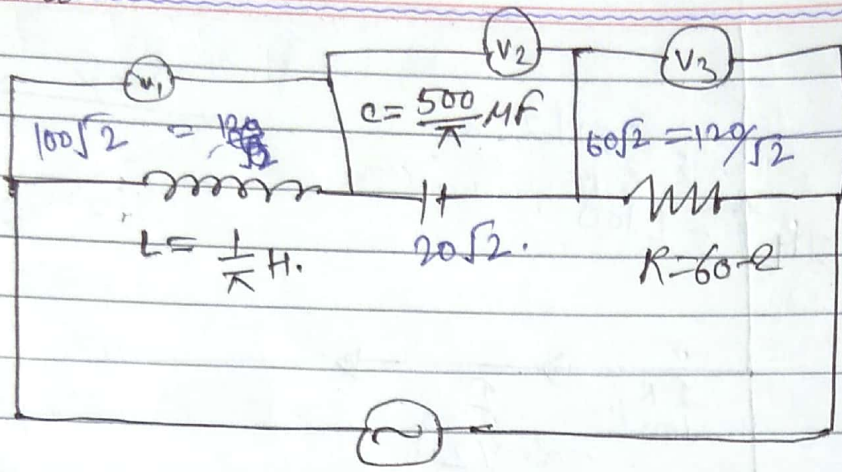


Phasor Method.

$200 \sin[\omega t + \phi]$

In the given diagram $\omega = 100\pi$

- (i) find max Current in the circuit.
- (ii) find Phase difference b/w Voltage and Current. which leads the other.
- (iii) find Current as a % of time.
- (iv) find voltage across each element at $t = \frac{50}{50}$ sec.
- (v) find v_1, v_2, v_3 .

$v = IR$

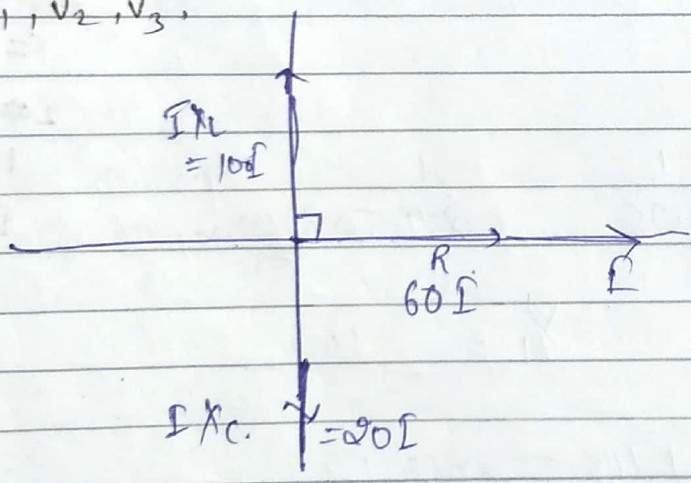


$X_L = \omega L$
 $= 100\pi \times \frac{1}{\pi}$
 $= 100$

$X_C = \frac{1}{\omega C} = \frac{1}{100\pi \times \frac{500}{\pi} \times 10^{-6}}$
 $= \frac{1 \times 10^2}{5} = \frac{100}{5} = 20$

$X_C = 20$

(vi) find Z in the circuit.

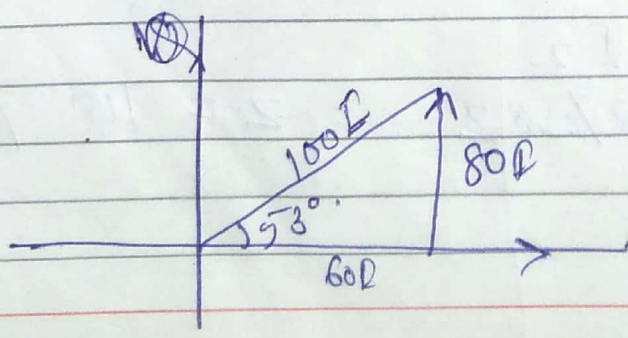

$Z = \sqrt{3600 + 6400}$
 $= \sqrt{10000}$
 $= 100$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$X = |X_L - X_C|$$

$$\frac{4}{5} \sin 53^\circ$$

$$\cos 53^\circ = \frac{3}{5}$$

$$\textcircled{1} \quad 100 I = 200$$

$$I = \frac{200}{100} = 2$$

$$\textcircled{2} \quad V_{\text{net}} = I Z$$

$$V_{\text{net}} = I 100$$

$$V = 80 I$$

$$V = I X$$

$$\textcircled{3} \quad \text{Impedance} \Rightarrow 100$$

$$\textcircled{2} \quad \text{Reactance} = 80$$

$$\textcircled{3} \quad \text{max Current} = 2$$

\textcircled{4} Voltage leads Current by 53° .
Current lags Voltage.

$$\textcircled{5} \quad I = I_0 \sin[\omega t + \phi]$$

$$= 2 \sin[100 \pi t - 53^\circ]$$

$$I = \frac{8}{5} \quad I = 2 \sin\left[100^2 \pi \times \frac{1}{50} - 53^\circ\right] =$$

$$I = \frac{8}{5}$$

$$V_R = I R = 2 \left[\frac{-4}{5}\right] 60 = -96 = 120 \sin[100 \pi t - 53^\circ]$$

$$V_L = 200 \sin[100 \pi t - 53^\circ + 90^\circ] = 200 \times \frac{3}{5}$$

$$V_C = 40 \sin[100 \pi t - 53^\circ - 90^\circ] = 120$$

$$= \frac{40}{5} \left[\frac{-3}{5}\right] = -24 \text{ A}$$



Avg \Rightarrow Reading \div Only
use vector method.

$$P = VI$$

Net Voltage.

$$V = 200 \sin\left(\frac{100\pi \times 1}{50}\right)$$

Instantaneous $= 200 \sin 2\pi$
 $= 0.$

$$= \sqrt{(V_L - V_C)^2 + V_R^2}$$

* Power factor

Power factor is define as the Ratio of power dissipated in the AC circuit to det. of max. Rms power in the dissipated in the circuit.

$$P = VI$$

$$= E_0 \sin(\omega t) I_0 \sin(\omega t + \phi)$$

$$\langle P \rangle = \frac{\int P dt}{\int dt} = \frac{E_0 I_0}{2} \cos \phi$$



$$= E_{rms} I_{rms} \cos \phi$$

$$\langle P_{max} \rangle = E_{rms} I_{rms}$$

Power factor = $\cos \phi$

$$\cos \phi = \frac{IR}{I^2 Z}$$

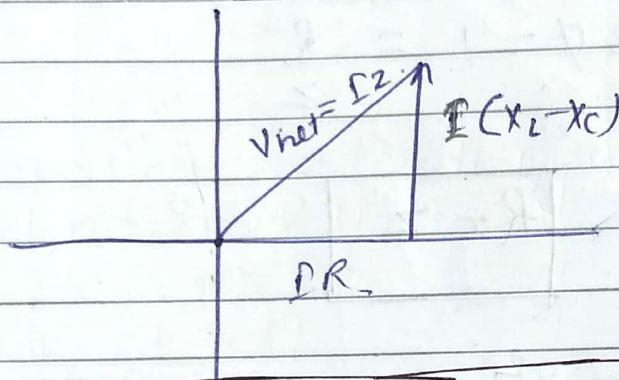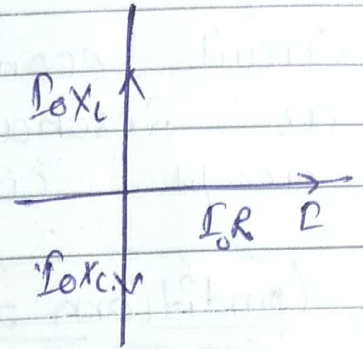Power factor $\rightarrow \cos \phi = \frac{R}{Z}$




Power dissipated = $I_{rms} I_{rms} \cos \phi$

* Wattless Current (Power less current):

Component of portion of a current which does not contribute to power dissipated in the circuit is known as watt less current.

Watt less Current = $I \sin \phi$

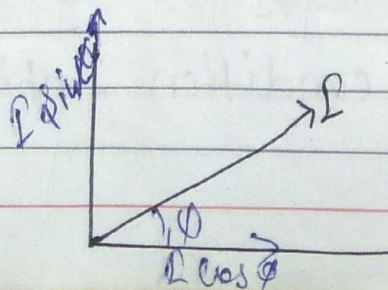

* Resonating circuit:

When power dissipated in this circuit become maximum this circuit is known as Resonating circuit. It is also known as acceptor circuit.

* Condition for Resonance:

$$\cos \phi = 1 = \frac{R}{Z}$$

$$R = Z$$

$$R^2 = Z^2$$

$$R^2 = R^2 + (X_L - X_C)^2$$

$$X_L = X_C \quad \text{Resonance}$$

$$\omega L = \frac{1}{\omega C}$$

$$\omega^2 = \frac{1}{LC}$$

$$\omega = \frac{1}{\sqrt{LC}}$$

$$Q \text{TFR} = \frac{1}{\sqrt{LC}}$$

$$f = \frac{1}{2\pi\sqrt{LC}}$$


frequency

* Important Point for Resonance or Circuit:

- (1) In Resonating condition Impedance of a circuit is minimum.

$HLO \rightarrow 0 \rightarrow \beta \rightarrow 3 \rightarrow 4$
 $R_{ace} \rightarrow 2$
 $E_{mi} - R_{CV}$


$$Z_{min} = R$$

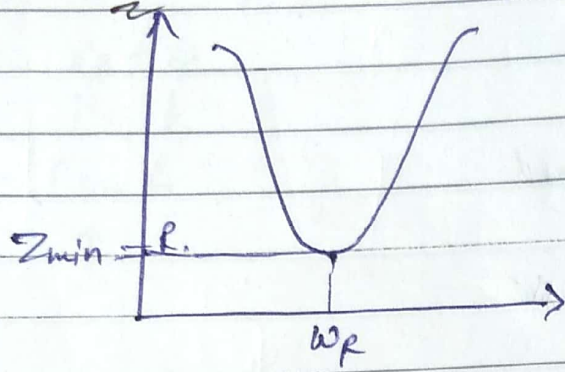

(2) In Resonating condition current in the circuit is maximum

$$V = IZ$$

$$I = \frac{V}{Z}$$

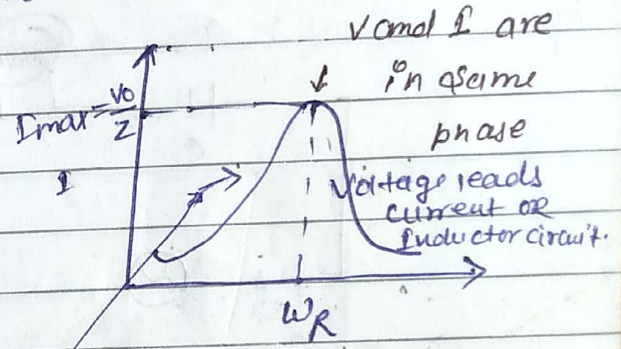

$$X_L = j\omega L$$

$$C \quad R \quad L$$

Current leads
 Voltage of
 Capacitive circuit.

$$\omega C L = X_L = \omega L$$

* $\omega_0 = \omega_R$ $\phi = 0$ Current and Resistance are in same phase.

* During Resonance Power factor of circuit is one.

Ques 1 $V = 100 \sin 100 \pi t$
 $I = 2 \sin(100 \pi t + \frac{\pi}{3})$

$V = IR$
 $R = \frac{V}{I} = 50$

$\frac{100}{\sqrt{2}} \times \sqrt{2} \times \frac{2}{\sqrt{2}}$
 $= 200$

find avg power


$P_{avg} = V_{rms} I_{rms} \cos \phi$

$P_{avg} = \frac{100 \times 2}{2} \cos 60^\circ$

$P_{av} = 50 \text{ watt}$

$\frac{100}{\sqrt{2}}$

Q.

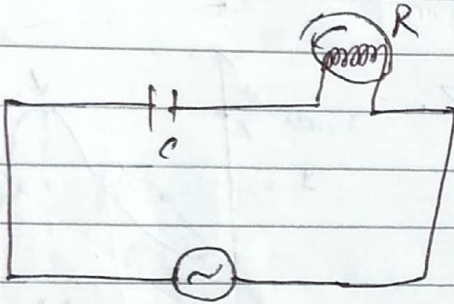

If dielectric is introduced b/w the plates of Capacitor then what will be change in brightness of the bulb?

↑

$P = I_{rms}^2 R$

$I_{rms} = \frac{V_{rms}}{Z}$

$Z = \sqrt{R^2 + X_C^2}$

$X_C = \frac{1}{\omega C}$

$Z = \sqrt{R^2 + X_C^2}$

$I_{rms} = \frac{V_{rms}}{Z}$

$P = I_{rms}^2 R$

ii) What will be change in Rms Voltage across the Capacitor

$$V^2 = V_R^2 + V_C^2$$


\uparrow \uparrow \downarrow
 $V_R = I_{rms} R$
 \uparrow \uparrow

$$I_{rms} = \frac{V_{rms}}{Z}$$

$$Z = \sqrt{R^2 + X_L^2}$$

$$V_C = I R_C = \frac{V_{rms}}{\omega C R}$$

Ex:

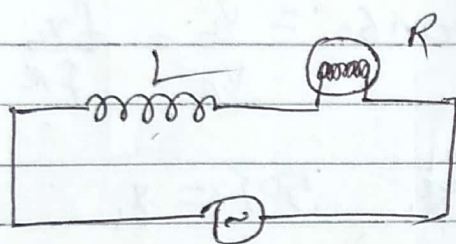

If iron rod is inserted inside the inductor then what be change of Brightness of bulb?

$$V^2 = V_R^2 + V_C^2$$

$$\uparrow X_L = \omega L \uparrow$$

$$L = \mu_0 n^2 \pi R^2 l$$

$$L' = \mu_r \mu_0 n^2 \pi R^2 l$$

$$Z = \sqrt{R^2 + X_L^2}$$


\uparrow \uparrow

$$\downarrow I_{rms} = \frac{V_{rms}}{Z \uparrow}$$

$$P = I_{rms}^2 R$$

\downarrow \downarrow



Q.

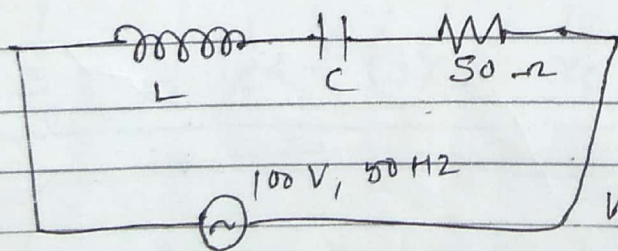

If only capacitor is removed then current lead by voltage by an angle 60° .


and if only inductor is removed the current lead voltage by 60° then find out rms current in it when

When all three element are connected

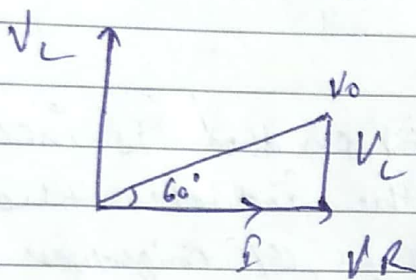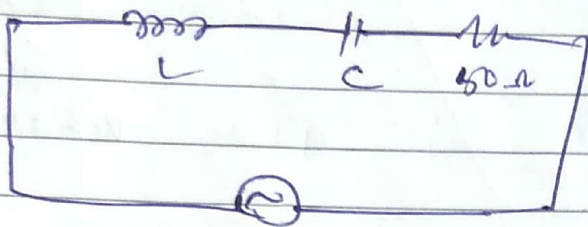


$$\tan 60^\circ = \frac{V_L}{V_R} = \frac{fX_L}{fR}$$
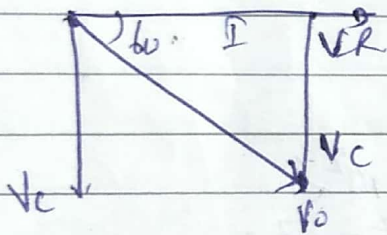
$$\tan 60^\circ = \frac{X_L}{R} \quad 50\sqrt{3} = X_L$$



$$\tan 60^\circ = \frac{V_C}{V_R} = \frac{X_C}{R}$$

$$X_C = 50\sqrt{3}$$

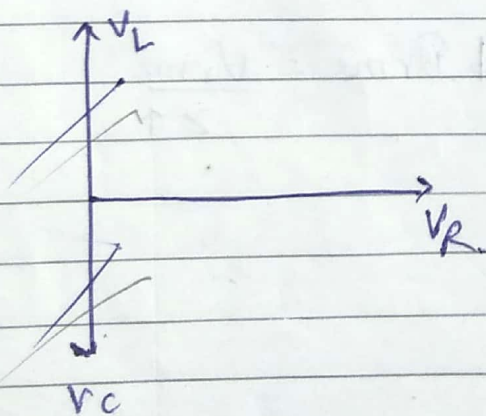

$$X_L - X_C$$

$$Z = R = 50 \Omega$$



$$I_{rms} = \frac{V_{rms}}{Z} = \frac{100}{50} = 2A$$

Series voltage
Parallel current

Parallel \Rightarrow Voltage same
Series \Rightarrow Current same

* Parallel LCR:

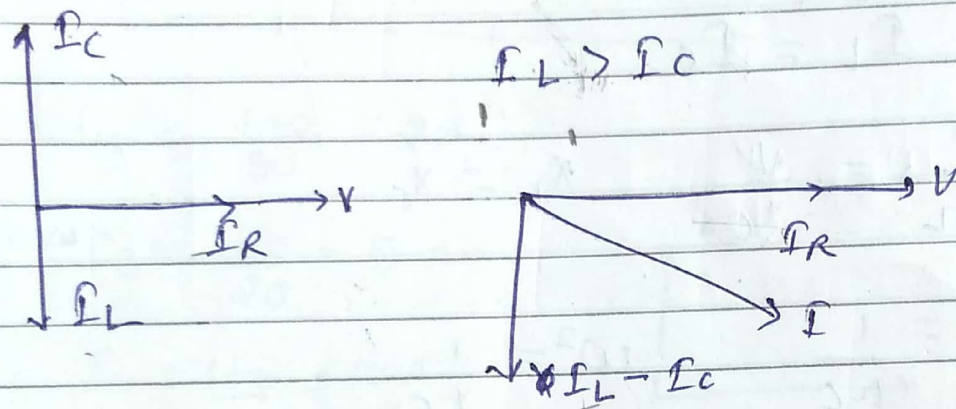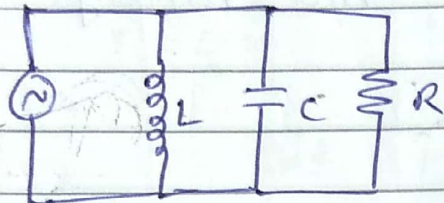In parallel LCR circuit
Phases diagram.
Voltage same. I diff



$$I = \sqrt{I_R^2 + (I_L - I_C)^2}$$

$$I = \sqrt{\left(\frac{V}{R}\right)^2 + \left(\frac{V}{X_L} - \frac{V}{X_C}\right)^2}$$

$$I = \frac{V}{N} \sqrt{\frac{1}{R^2} + \left(\frac{1}{X_L} - \frac{1}{X_C}\right)^2}$$

$$\frac{I}{V} = \frac{1}{N} \sqrt{\frac{1}{R^2} + \left(\frac{1}{X_L} - \frac{1}{X_C}\right)^2}$$

$$\frac{1}{Z} = \frac{1}{N} \sqrt{\frac{1}{R^2} + \left(\frac{1}{X_L} - \frac{1}{X_C}\right)^2}$$

$$Z = R^2 + (X_L - X_C)^2$$

Series LCR:

$V = IR$
 $\frac{V}{I} = Z$
 $\frac{V}{I} = Z \text{ impedance}$

~~R~~ R

In Resonance Current and Voltage will be in same phase.

$$R = \frac{1}{C}$$

$$I_L = I_C$$

$$\frac{V}{X_L} = \frac{V}{X_C}$$

$$X_L = X_C$$


$$\omega = 2\pi f$$

$$\omega L = \frac{1}{\omega C}$$


$$\omega^2 = \frac{1}{LC}$$

$$\omega = \frac{1}{\sqrt{LC}}$$

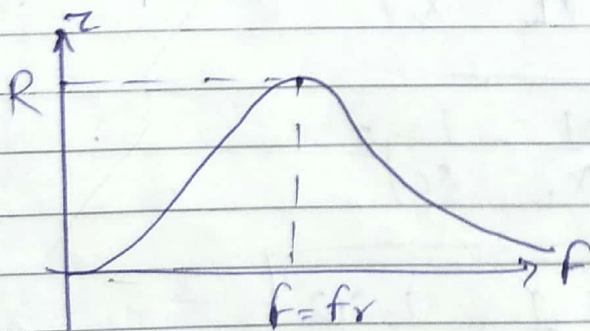- (i) $f = 0$, $Z = 0$
- (ii) $f = \infty$, $Z = 0$
- (iii) $f = f_r$, $X_L = X_C$, $Z_{max} = R$




[Current same]

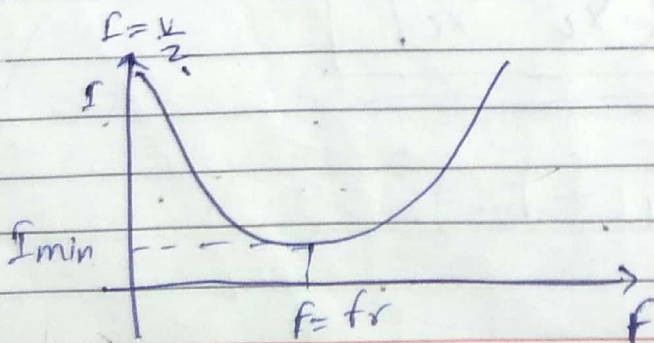

$$B = I^2 \neq P^2$$

Q3

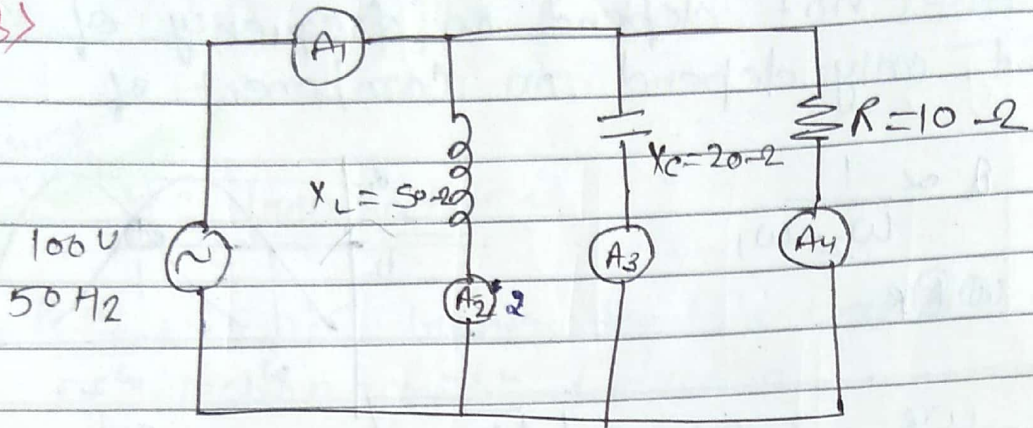

$$Z = \sqrt{\frac{1}{100} + \left(\frac{1}{50} - \frac{1}{20}\right)^2}$$

$$Z = \sqrt{\frac{1}{100} + \left(\frac{2-5}{100}\right)^2}$$


$$Z = \sqrt{\frac{1}{100} + \left(\frac{-3}{100}\right)^2}$$

$$Z = \frac{\sqrt{10}}{10}$$

$$I_2 = \frac{100}{50} = 2A$$

$$I_3 = \frac{100}{20} = 5A$$

$$I_4 = \frac{100}{10} = 10A$$

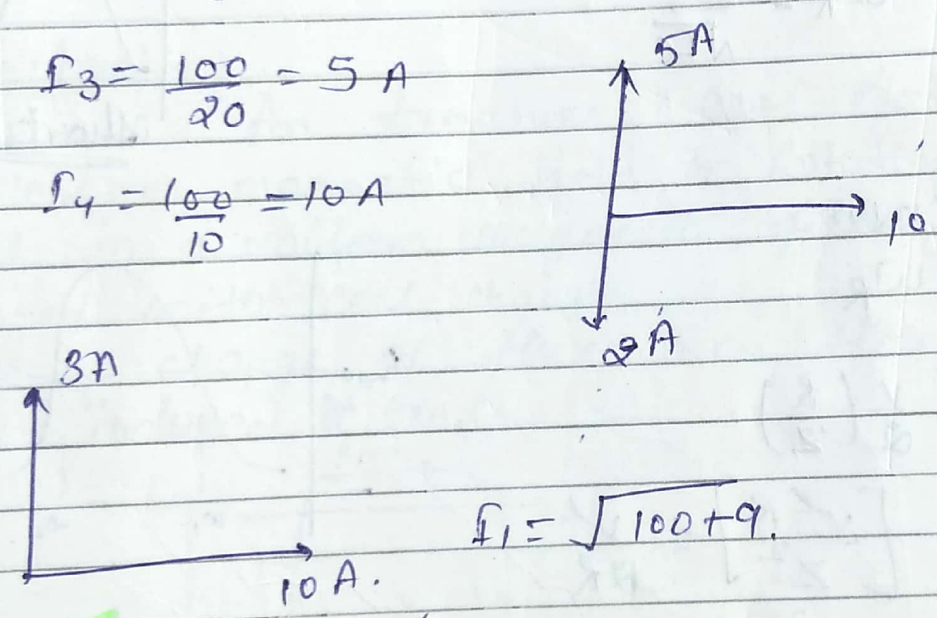

$$I_1 = \sqrt{100 + 9}$$

Quality factor: (Q-factor)

It is defined as ratio of Resonating frequency to that of Band width of the circuit


Band width

is defined as frequency of the source when power in the circuit is half of the maximum power of the circuit.

* Q-factor does not depend on frequency of source. It only depend on component of circuit


$$Q \propto \frac{1}{\omega_2 - \omega_1}$$

$$Q \propto \omega R$$

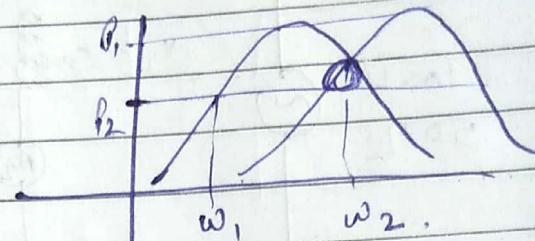

$$Q = \frac{\omega R}{\omega_2 - \omega_1} \quad \text{or} \quad \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$\omega R = \frac{1}{\sqrt{LC}}$$

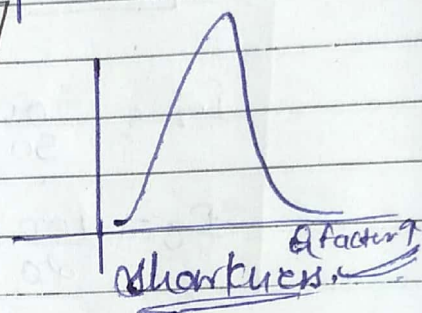

* $P = VI \cos \theta$
 $\omega_1, \omega_2 = \omega R$

$$P = V \frac{V}{Z} \left(\frac{R}{Z} \right)$$


$$= \left[\frac{V^2 R}{Z^2} \right] = \frac{V^2}{2R}$$

$$2R^2 = Z^2$$

$$2R = R^2 + (X_L - X_C)^2$$

$$(X_L - X_C)^2 = R^2$$

$$X_L - X_C = \pm R$$

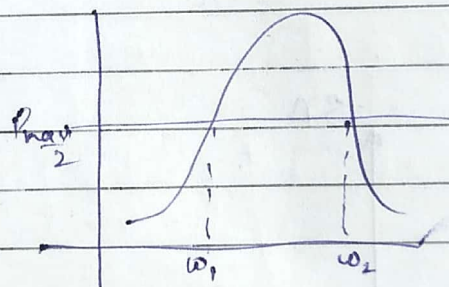

$$\omega_1 L - \frac{1}{\omega_1 C} = -R \quad \text{--- (1)}$$

$$\omega_2 L - \frac{1}{\omega_2 C} = +R \quad \text{--- (2)}$$

eqn. (2) - (1)

$$\frac{1}{\sqrt{LC}}$$

$$(\omega_2 - \omega_1) L = \left[\frac{1}{\omega_2 C} - \frac{1}{\omega_1 C} \right] = 2R$$

$$[\omega_2 - \omega_1] = \frac{R}{L}$$

Bandwidth.

Meins.

* AC Generator:


* Principle: AC generator is Based on Principle of Electromagnetic Induction.

$$E = \frac{d\phi}{dt}$$

* Construction:

An Armature coil placed inside a uniform magnetic field on rotating Armature coil in a uniform magnetic field flux (ϕ) linked with coil change.

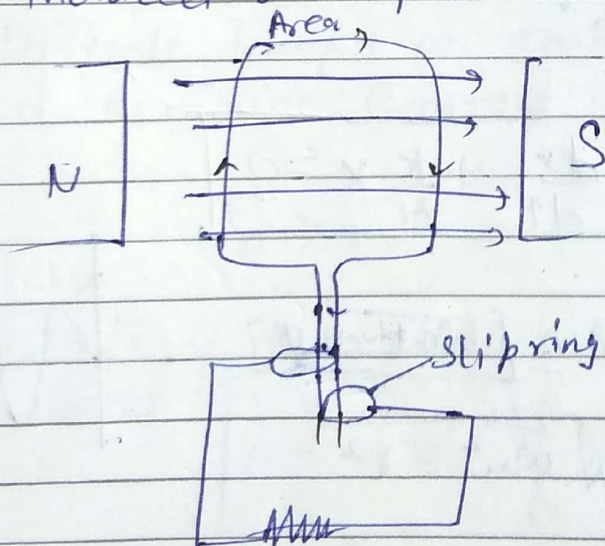Rate of change of flux w.r.t time is known as induced ϕ Emf.



$$\phi = NBA \cos \theta$$

$$e = \underline{NBA \omega \sin \theta}$$


$$e = \underline{E_0 \sin(\omega t)}$$

$V_{\text{viscous force}} = b \pi r b v$

AC Slip ring

DC Split ring

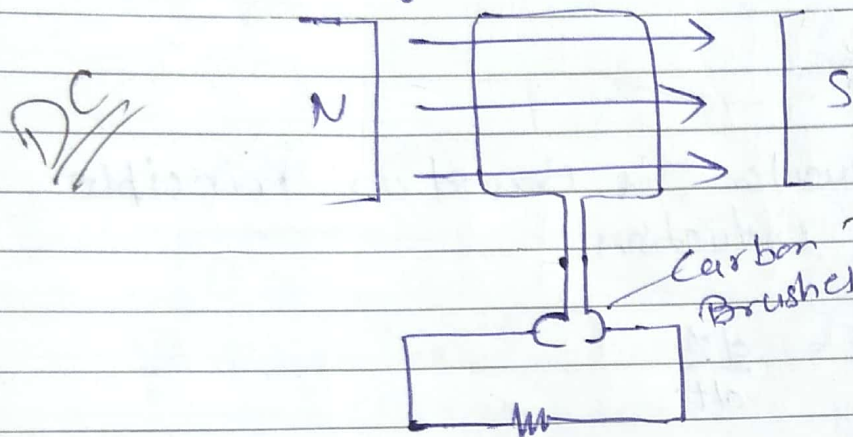* In DC generator instead of slip ring split ring with carbon brushes are used.



Difference in DC and AC only the ring

* Damped Oscillation

Not done for part 1

$ma = -kx - bv$

$a = -\frac{kx}{m}$

$v = \frac{b}{m}$


$\frac{d^2x}{dt^2} + \frac{k}{m}x + \frac{b}{m}v = 0$

$\frac{d^2x}{dt^2} + \frac{b}{m} \frac{dx}{dt} + \frac{k}{m}x = 0$

$y = A_0 e^{-\gamma t} \sin[\omega_D t + \phi]$

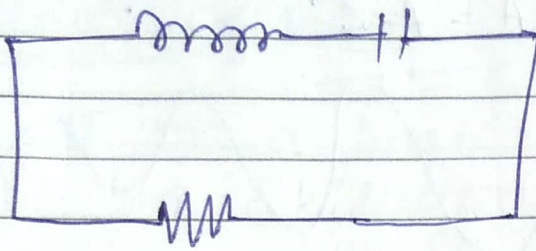where $\omega_D = \sqrt{\omega_N^2 - \gamma^2}$





$x \rightarrow q$
 R_{eq}

By K.V.L

$$-iR - L \frac{di}{dt} - \frac{q}{C} = 0$$

Time Constant


$$\frac{d^2q}{dt^2} + \frac{R}{L} \frac{dq}{dt} + \frac{q}{LC} = 0$$

$$\gamma = \frac{R}{2L}$$

$$q = Q_0 e^{-\gamma t} \sin(\omega_0 t + \phi)$$

Damping Coefficient = γ

* Important ~~Key~~ Key Points:

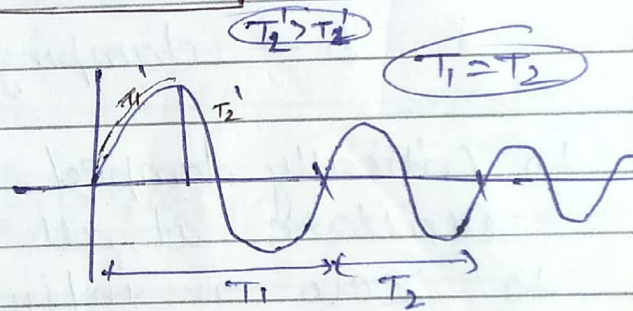

(1) Amplitude keeps on decreasing while time period remains constant.

$$T_2' > T_1'$$

(2) Amplitude of oscillation decreases exponentially with time

$$A = A_0 e^{-\gamma t}$$


$$A \xrightarrow{t} kA_0$$

$$A \xrightarrow{nt} k^n A_0$$

over damped $\textcircled{1}$ Particle goes to rest in finite time.

critically damped $\textcircled{2}$ Same as over damped.

$\textcircled{3}$

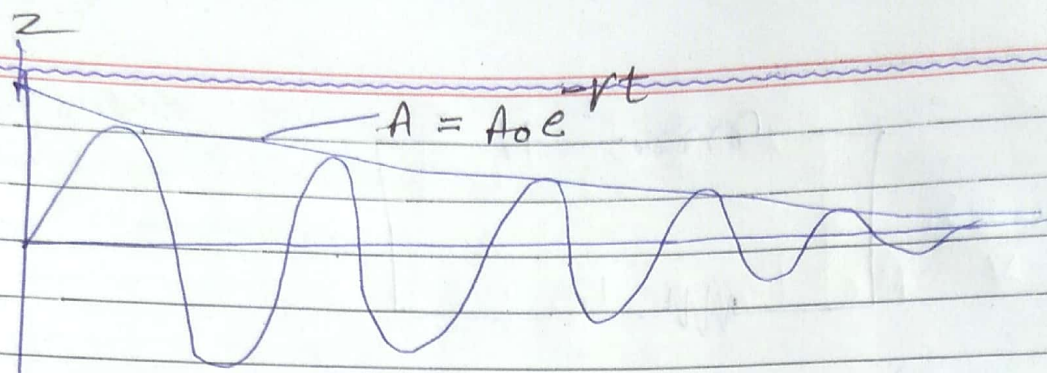


* Critically damped oscillation: ($\gamma = \omega_0$)

if when γ 's damping coefficient = ω_0

$$\gamma = \frac{b}{2M} \quad / \quad \gamma = \frac{R}{2L}$$

$b \rightarrow$ damping constant.

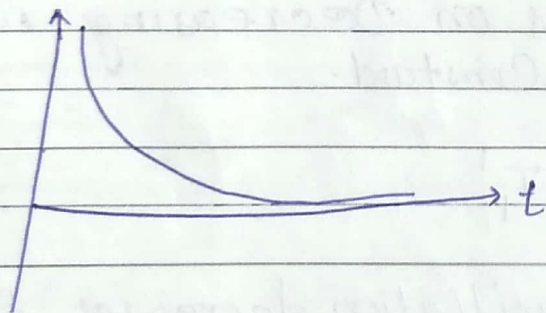In critically damped oscillation particle does not oscillate at all. Amplitude of particle decreases to zero in infinite time. ~~Amplitude~~



* Over damped condition:

$$\gamma > \omega_0$$

Some particle does not oscillate with time, but amplitude decays to zero in finite time.

But amplitude decreases to zero.

* forced oscillation:-

If external force is applied on a particle in damped oscillation then the oscillation is known as forced oscillation. In force oscillation an external force applied periodically varies periodically with a phase difference of $\pi/2$.

$$\frac{d^2x}{dt^2} + \frac{dx}{dt} + \omega_n^2 x = \frac{f_0}{M} \cos \omega t.$$

RLC: $\frac{d^2Q}{dt^2} + \frac{dQ}{dt} + \omega_0^2 Q = V_0 \cos \omega t.$

Amplitude $\Rightarrow A \Rightarrow \frac{f}{m(\omega^2 - \omega_0^2) + 4\omega_0^2 r^2}$

Imp. \downarrow

Imp. Que: A particle oscillates in a space such that its amplitude decreases with time exponentially. In 1 second amplitude of particle becomes 90% of its initial value. Find the Amplitude after 6 sec of motion.

$$A = A_0 e^{-\gamma t}$$

damping coefficient $\gamma = \frac{b}{2m}$

$A \xrightarrow{2 \text{ sec}} 0.9 A_0$

$A \xrightarrow{6 \text{ sec}} (0.9)^3 A_0 = 0.729 A_0.$