

SBG STUDY

09/06/17

Chapter-

Current Electricity

* Electric current = (i, I) Ampere (A)

state of flow of charge

$$i = \frac{q}{t} = \frac{dq}{dt} \rightarrow \text{instantaneous}$$

$$i = \frac{\Delta q}{\Delta t}$$

It is neither scalar nor vector.

Que: charge flowing through a wire is given by $q = \alpha t - \beta t^2$ Coulomb. Find the current through wire:

Ans: $i = \frac{dq}{dt}$ $i = \alpha - 2\beta t$

ii) Current is increases in the ~~direction of~~ wire.
Ans: false

iii) Magnitude of current first decreases ~~increases~~ then increases.

Ans: True.

Que: Current flowing in a conducting wire is $I = \alpha t$ Amp. find total charge through the wire after time t_0 .

Ans:

$$f = \frac{dq}{dt}$$

$$\int dq = \int i dt$$

$$I = \alpha t \text{ Amp.}$$

$$\frac{dq}{dt} = \alpha t$$

$$\int dq = \int_0^{t_0} \alpha t dt$$

$$q = \frac{\alpha t_0^2}{2}$$


ii) Find average current in t_0 time.

$$I_{\text{avg.}} = \frac{q_{\text{total}}}{\text{total time}} = \frac{\frac{\alpha t_0^2}{2}}{t_0}$$

$\frac{\text{Total Charge}}{\text{Total time}}$

$$= \frac{\alpha t_0}{2}$$

* Current in conductors

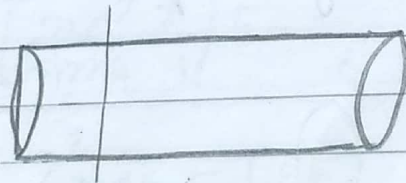

In every conductor free electrons are in random motion due to thermal energy. These electrons collide each other and also to the atoms of conductor. After ~~everywhere~~ collision their direction change. Hence their average displacement is zero and on any section the no. of electrons crossing in one direction is equals to no. of electrons crossing in other direction. Hence net flow of charge at any cross section is zero.

That's when electric current in the absence of voltage sources zero.

* Relaxation time : (τ)

Time interval b/w two consecutive collisions called relaxation time.


$$\tau \approx 10^{-14} \text{ sec.}$$

* Free path or mean free path :

It is the average distance travelled by electron b/w two consecutive collisions.

$$\lambda_{\text{avg}} = \frac{\lambda_1 + \lambda_2 + \lambda_3 + \dots + \lambda_n}{n}$$

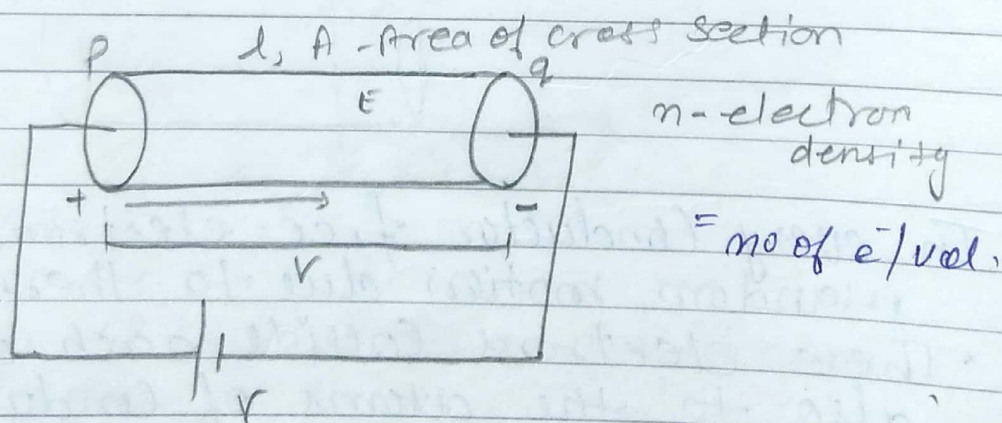* ON @ increasing temp. Relaxation time decreases



Electric field : $\frac{V}{l}$

$$F_e = eE$$

($F = ma$)

$$a = \frac{eE}{m}$$

$$v_d = a\tau$$

Drift velocity

$$V_d = \frac{eE\tau}{m}$$

$$a = \frac{eE}{m}$$

$$V_d = a\tau = \frac{eE\tau}{m}$$

drift velocity

$$\text{drift speed: } v = \frac{j}{ne}$$

Total no. of electrons = nAl
total charge $q = neAl$

$$i = \frac{q}{t} = neA\left(\frac{l}{t}\right)$$

$$I = neAV_d$$

drift velocity

$$I = neA \frac{eE\tau}{m} l$$

$$I = \left(\frac{ne^2\tau}{m}\right) AE$$

$$\frac{I}{A} = j \text{ (current density)}$$

$$\frac{I}{A} = \left(\frac{ne^2\tau}{m}\right) E$$

\downarrow

$$j = \left(\frac{ne^2\tau}{m}\right) E$$

$$\frac{ne^2\tau}{m} = \sigma$$

Conductivity of wire

C. density $j = \sigma E$

$$j = \frac{I}{A} = \frac{m}{ne^2\tau} \sigma E$$

$$I = neAV_d$$

$$I = neA \frac{eE\tau}{m} l$$

$$I = \left(\frac{ne^2\tau}{m}\right) A \frac{V}{l} \quad \therefore I = \sigma \frac{A}{l} V$$


How? $J \cdot A$

$$V = \frac{l}{\sigma A} \cdot I$$

$$V = \int \frac{l}{A} I$$

$$R = \int \frac{l}{A}$$

$$V = IR \rightarrow \text{Ohm's Law}$$

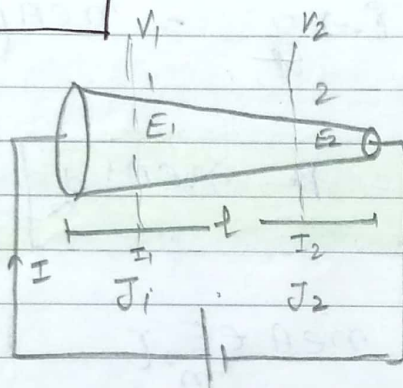

a) $I_1 = I_2$

b) $V_1 < V_2$

c) $J_1 < J_2$

d) $E_1 < E_2$

$V = IR$
 $R = \frac{l}{\sigma A}$

$V = IR$

direction of current is opposite to the direction of flow of electron or in the direction of charge.

* Current density (j)

$$j = \frac{I}{A} \quad \text{A/m}^2$$


j is a vector quantity

* Its direction is in the direction of current.

$$I = \vec{j} \cdot \vec{A}$$

10/06/17

Ex!

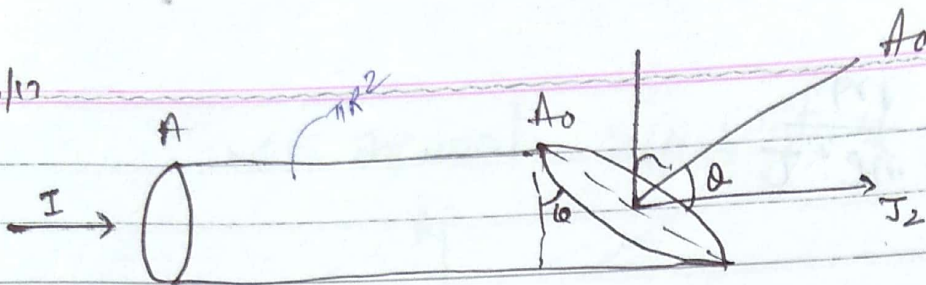

Find J_1 and J_2

$$J_1 = \frac{I}{A}$$

$$I = J_2 A_0 \cos \theta$$


$$J_2 = \frac{I}{A_0 \cos \theta}$$

variable

✓ Que: Current in a conducting wire of radius R is flowing such that current density in the wire is

a) $J_0 \text{ A/m}^2$

b) $J_0 \frac{r}{R} \text{ A/m}^2$

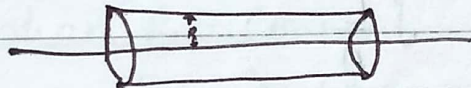

Find net current flowing through the wire in both cases.


Ans! a) $I = JA = J_0 \pi R^2$

b)

$$dA = 2\pi r dr$$


$$dI = J_0 \frac{r}{R} dA = J_0 \frac{2\pi r^2}{R} dr$$
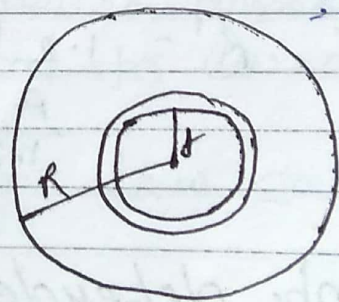
$$I = J_0 \frac{2\pi}{R} \int_0^R r^2 dr$$



$$\frac{I}{A} = J_0$$

* Resistance of a wire (resistor):

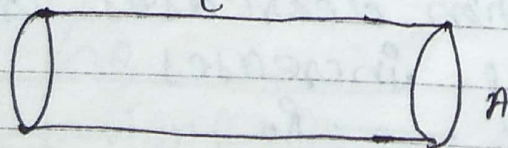

$$R = \frac{V}{I}$$

$$R = \frac{\rho l}{A} \text{ ohm } (\Omega) = \frac{\text{Volt}}{A}$$

$$f = \frac{m}{me^2 \tau}$$

Ques: Resistance of a cylindrical wire is R_0 if its length is doubled and new Resistance.

Ans: $\Delta A = \text{Constant}$

$$R_0 = \int \frac{l}{A} \quad R = \int \frac{l'}{A'} = \int \frac{2l}{A/2}$$

$$R = \underline{4R_0}$$

(ii) If wire is stretch by 20% find % change in Resistance.

Ans: $R = \int \frac{L}{A}$

$$l' = 1.2l$$

$$A' = \frac{A}{1.2}$$

$$R' = \frac{1.2l}{\frac{A}{1.2}}$$

$$R' = 1.44 R$$

$$\frac{20\% \cdot l}{A/1.2}$$

$$= \frac{4 \times 20}{100} = 8\%$$

$$\frac{20\% \cdot l}{\frac{100}{20}}$$

* Temp. dependence on Resistance:

When temp. is increase due to thermal energy collision b/w electrons become more frequent. Hence relaxation decreases and Resistivity and Resistance increases


$$0^\circ\text{C} \text{ --- } R_0$$

$$t^\circ\text{C} \text{ --- } R_t = R_0(1 + \alpha \Delta t)$$


$T \uparrow \rightarrow R \text{ and } \rho \uparrow$

$$V = IR$$

α = Thermal coefficient of Resistance

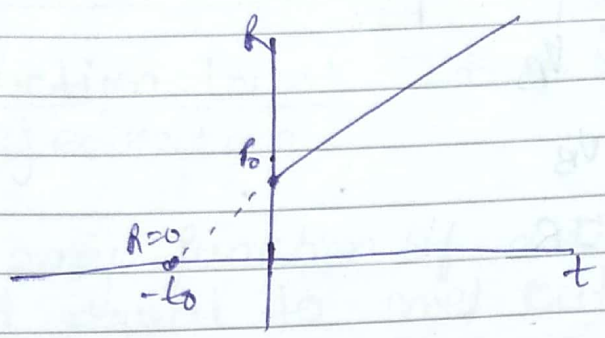


* Ohm's law :

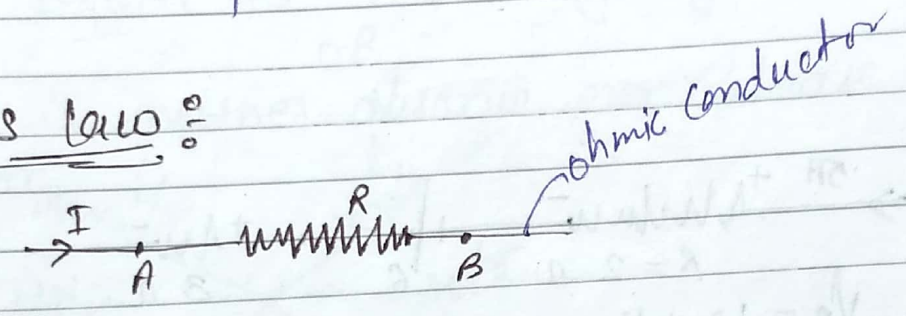

$V = IR$ when R - Const
 T - Const.
 Pot. diff


* When temp. and shape of a conductor are constant then Potential difference across the conductor is directly proportional to Current.

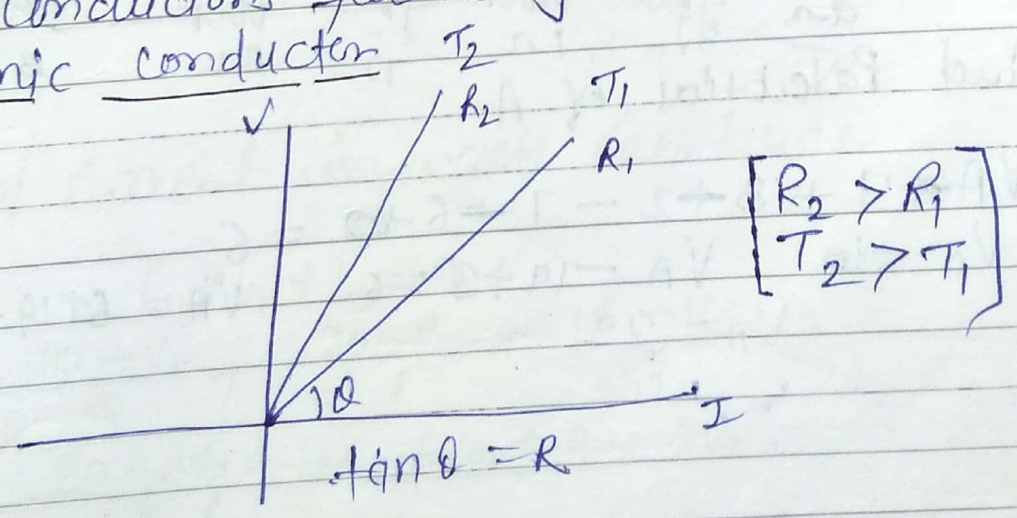* The Conductors following Ohm's law called ohmic conductor



$$\left[\begin{matrix} R_2 > R_1 \\ T_2 > T_1 \end{matrix} \right]$$

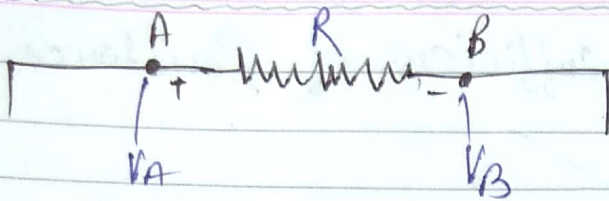$V = IR$
 $V = (R) I$
 slope = $\frac{m}{\text{unit}}$




$$V_A - IR = V_B$$

$$V_A - V_B = IR$$

$$V = IR$$

Que!

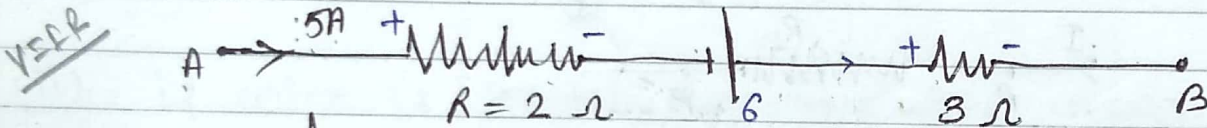

$$V_A = 10 \text{ volt.}$$

Find potential of B.

Ans: $V_A = 10 \text{ volt}$

$$V_A - 10 + 6 - 15 = V_B$$

$$V_B = -9 \text{ Volt}$$


$$V_A - V_B = IR$$

$$10 - V_B = 15 \times 6$$

$$-V_B = 30 - 10 = 20$$

$$V_B = -20$$

Que!

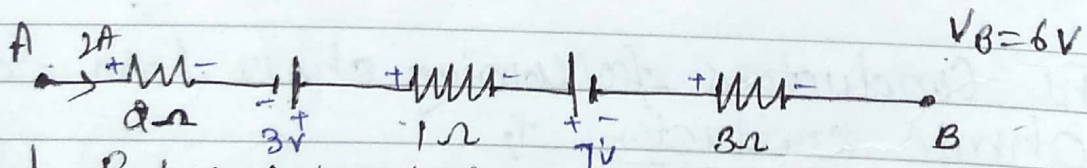

Find Potential of A

$$V_A - 4 + 3 + 2 - 7 + 6 = 6$$

$$V_A - 19 + 3 = 6 \quad V_A = 6 + 19 - 3$$


$$V_A = 22$$

* Kirchoff's law!

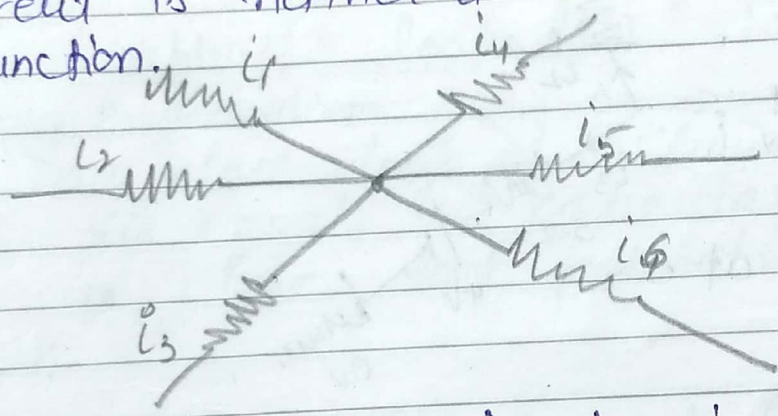(1) Junction law: It is based on charge conservation.


At any junction of a circuit net incoming current equal to net outgoing current.

OR
Current is neither absorbed nor released at the junction.



$$i_1 + i_2 + i_3 = i_4 + i_5 + i_6$$

Ques:

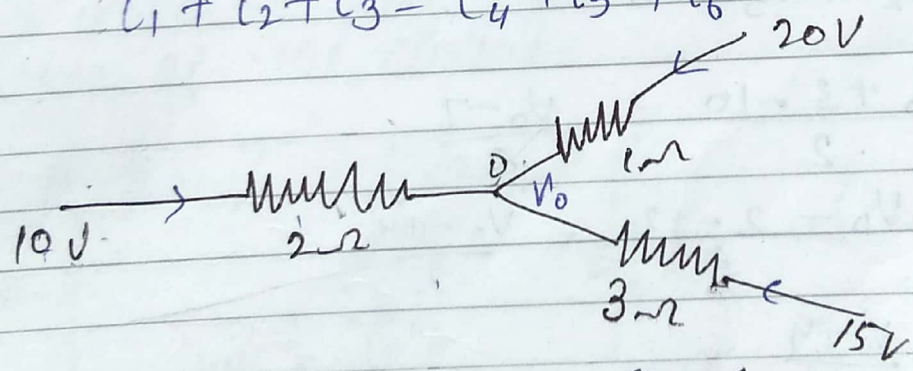

let $\sigma = V$

find current in each resistance.

Ans:

$$i_1 + i_2 + i_3 = 0$$

$$\frac{10 - V_0}{2} + \frac{20 - V_0}{1} + \frac{15 - V_0}{3} = 0$$

$$\frac{30 - 3V_0 + 120 - 6V_0 + 30 - 2V_0}{6} = 0$$

$$-11V_0 + 180 = 0$$

$$+11V_0 = +180 \quad V_0 = \frac{180}{11} \text{ Volt.}$$


$$V_0 = \frac{180}{11} \text{ Volt}$$

H.W. J.M.
 8-2 Q. 1, 5, 6, 9
 Rora.

$$i_1 = \frac{10 - \frac{180}{11}}{2} = \frac{110 - 180}{11 \times 2} = -\frac{70}{22} \text{ A}$$

$$i_2 = \frac{20 - \frac{180}{11}}{2} = \frac{220 - 180}{11} = \frac{40}{11}$$
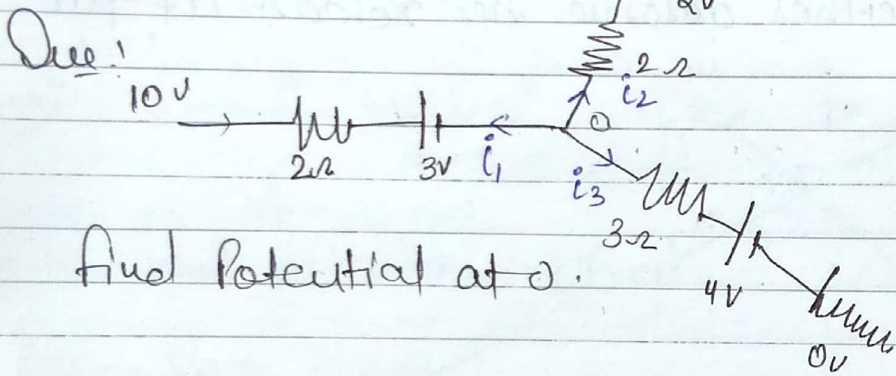
$$i_3 = \frac{15 - \frac{180}{11}}{3} = \frac{165 - 180}{33} = -\frac{15}{33}$$



$$i_1 + i_2 + i_3 = 0$$

$$i_1 = \frac{V_0 + 3 - 10}{2} = \frac{V_0 - 7}{2}$$

$$i_2 = \frac{V_0 - 2 - 12}{2} = \frac{V_0 - 14}{2}$$

$$i_3 = \frac{V_0 - 4}{3}$$

$$\frac{V_0 - 7}{2} + \frac{V_0 - 14}{2} + \frac{V_0 - 4}{3} = 0$$

$$\frac{3V_0 - 21 + 3V_0 - 42 + 2V_0 - 8}{6} = 0$$

$$3V_0 - 21 + 3V_0 - 42 + 2V_0 - 8 = 0$$

$$8V_0 = 71$$

$$V_1 = \frac{71}{8} \text{ Volt.}$$

$$i_1 = \frac{7/8 - 7}{2}$$

$$i_2 =$$


$$i_3 =$$

2) Kirchhoff's Voltage Law

or Kirchhoff's loop law: It is based on energy conservation.

* In any close loop of a circuit net potential drop is equals to potential gained or in a close loop potential difference is zero.

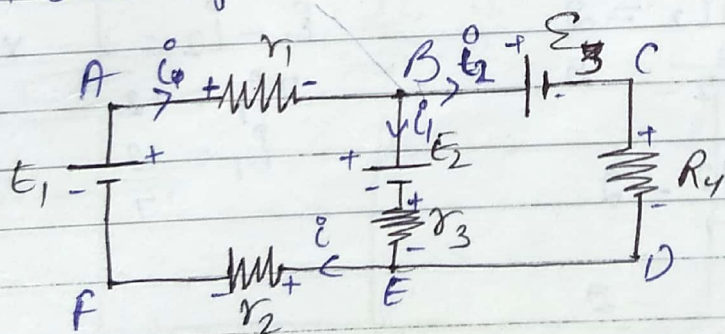a It is used to find current in different branches of the circuit.



$$i = i_1 + i_2 \quad \text{--- (i)}$$


Apply K.V.L in loop ABEFA

$$-i r_1, -E_2, -i r_3 - i r_2 + E_1 = 0$$

loop BCDEB

$$-E_3 - i_2 R_4 + i_1 R_3 + E_2 = 0$$

Race 13
 S:1 = 7Ω
 S-2 ⇒ 1, 2, 5, 6, 9

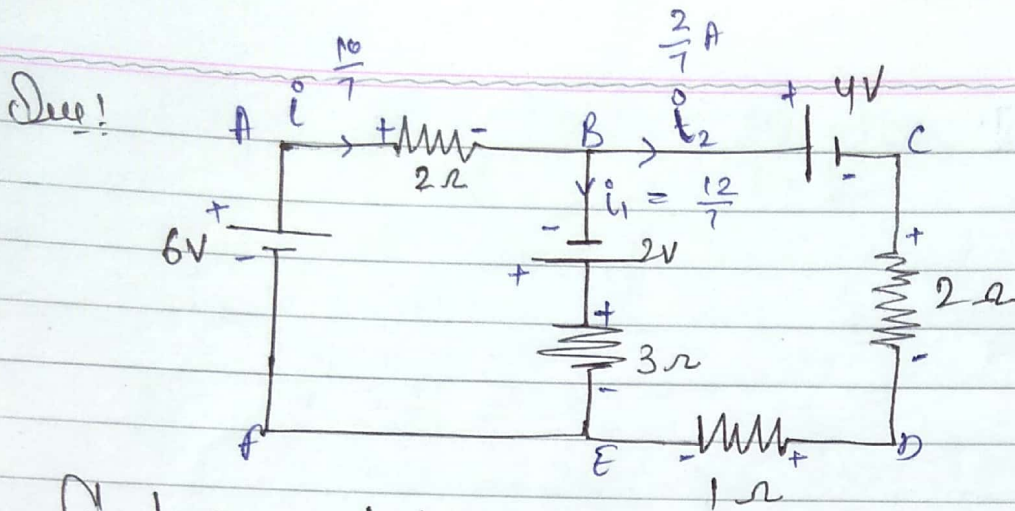

$$I = I_1 + I_2 \quad \text{--- (1)}$$

Find current in each resistor

Sol! In loop AB EFA

$$-2i + 2 - 3i_1 + 6 = 0 \Rightarrow -2(i + i_2) + 2 - 3i_1 + 6 = 0$$

$$\Rightarrow i - 2i - 3i_1 + 8 = 0 \quad \text{--- (i)} \quad \text{--- (ii)}$$

$$5i_1 + 2i_2 = 8 \quad \text{--- (1)}$$

In loop BC DEB.

$$-4 - 2i_2 = i_2 + 3i_1 - 2 = 0$$

$$-6 - 4i_2 + 3i_1 = 0 \quad \text{--- (ii)}$$

$$-3i_2 + 3i_1 - 6 = 0$$

$$3i_1 - 3i_2 = 6$$

$$i_1 - i_2 = 2$$

$$\frac{12}{7} - i_2 = 2$$

$$i_2 = \frac{12}{7} - 2$$

$$i_2 = \frac{-2}{7}$$


$$i_1 - i_2 = 2 \quad \times 2$$

$$7i_1 = 12$$

$$i_1 = \frac{12}{7}$$

* Alternate method!

Junction (node) Method!

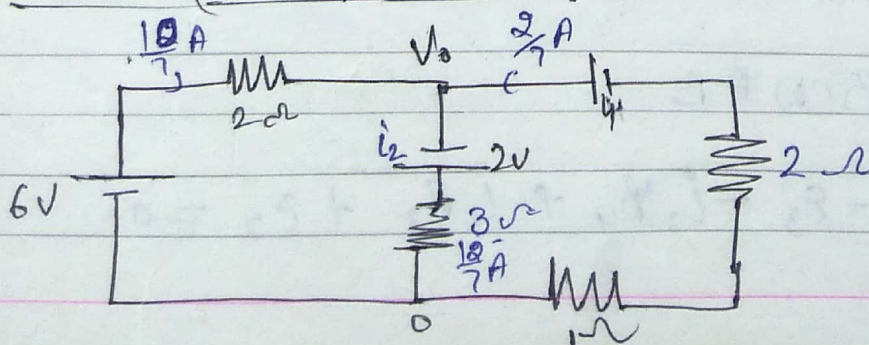

$$i_1 + i_2 + i_3$$

$$\frac{V_0 - 6}{2} + \frac{V_0 + 2}{3} + \frac{V_0 - 4}{3} = 0$$

$$\frac{3V_0 - 18 - 2V_0 + 4 + 2V_0 - 8}{6} = 0$$

$$3V_0 - 18 - 2V_0 + 4 + 2V_0 - 8 = 0$$


$$7V_0 - 22 = 0$$

$$V_0 = \frac{22}{7}$$

$$i_1 = \frac{V_0 - 6}{2} = \frac{\frac{22}{7} - 6}{2} = -\frac{\frac{20}{7}}{2} = -\frac{10}{7} \text{ A}$$

$$i_2 = \frac{V_0 + 2}{3} = \frac{\frac{22}{7} + 2}{3} = \frac{\frac{36}{7}}{3} = \frac{12}{7} \text{ A}$$
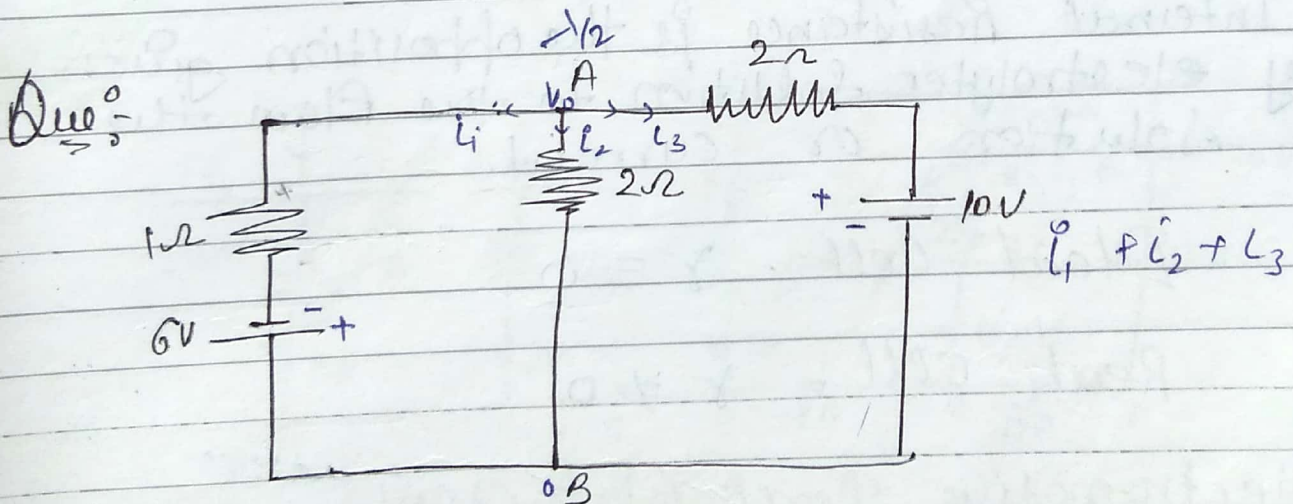
$$i_3 = \frac{\frac{22}{7} - 4}{3} = \frac{\frac{50}{7} - 8}{3} = -\frac{2}{7} \text{ A}$$



find current in AB.


$$\frac{V+6}{1} + \frac{V}{2} + \frac{V-10}{2} = 2V+12+V+V-10=0$$

$$4V+2=0$$

$$V = -\frac{1}{2}$$

$$i_2 = -\frac{10}{4} \text{ A} \quad (\text{from B to A}) \quad \text{Current}$$
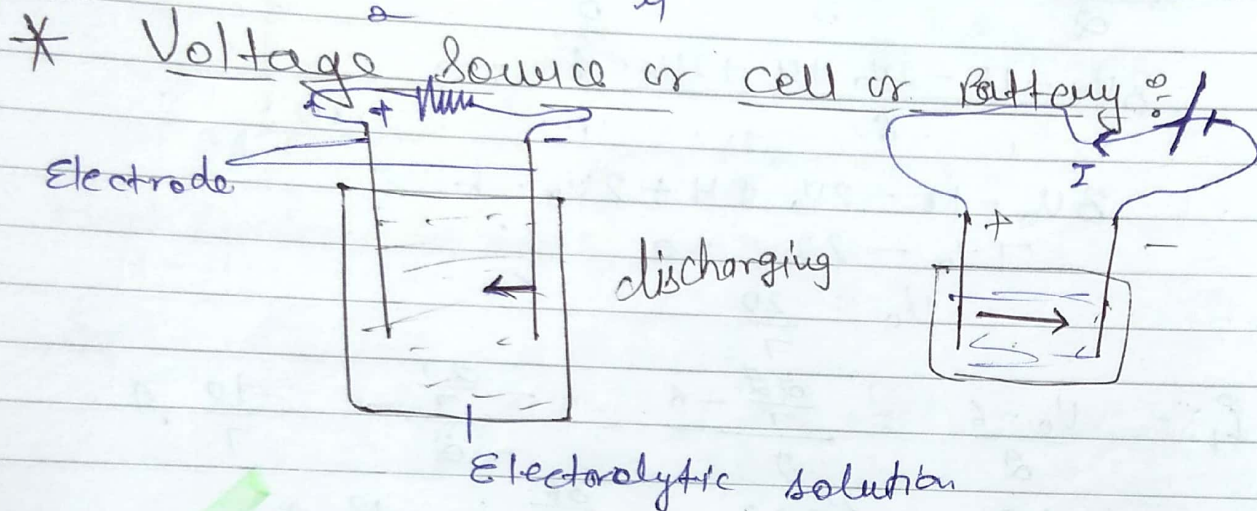
$$i_3 = \frac{-\frac{10}{2} - 10}{2} = -\frac{21}{2}$$



* Internal Resistance of cell (r)


Internal Resistance is the opposition given by electrolyte solution to the flow of the solution or current.

Ideal Cell - $r = 0$

Real cell = $r \neq 0$

* Electromotive force (E.M.F) (E) not force
 It is work done by the battery to move a unit charge along the circuit.
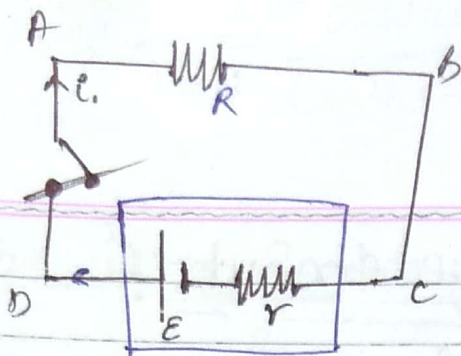
$$EMF = \frac{W_0}{q} \quad \text{J/C} = \text{Volt}$$



\rightarrow --- dis
 \leftarrow --- ch

$$-iR - ir + E = 0$$

$$i = \frac{E}{R + r}$$


Potential difference across terminal of battery:

$$V = E - ir$$

discharge.


$$V = E \text{ if } i = 0$$

$$V = E + ir \text{ - charge}$$

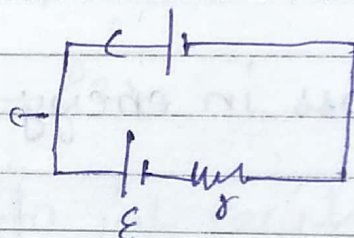

Ideal cell = $V = E$

Que:

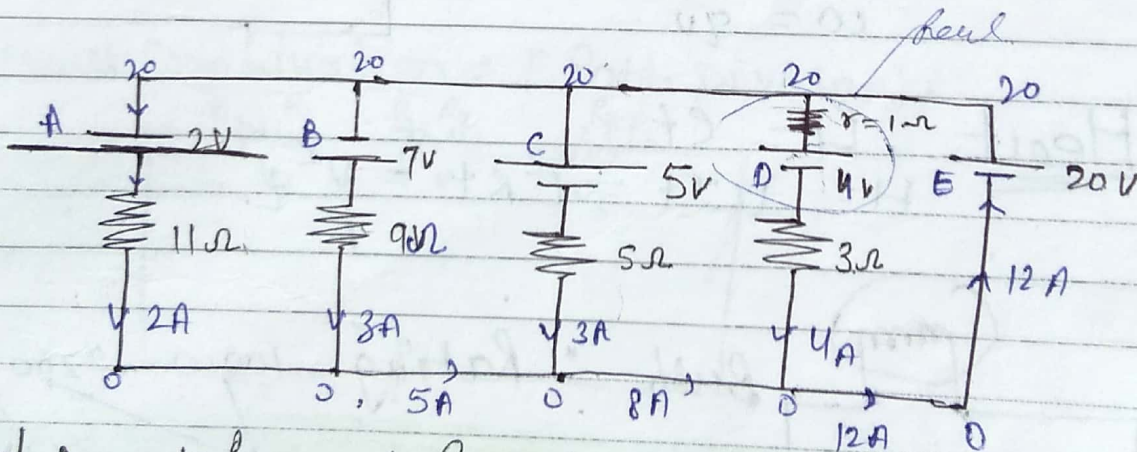

(i) Find current in each branch.

A, B, F discharge

C, D discharge-charge

(ii) Find Potential difference in battery D.

$$V = E + ir$$

$$= 4 + 4 = 8 \text{ Volt.}$$

Current $H = I^2 R t$ \Rightarrow Race $\div 13$
 $\frac{0-1}{0-1} \Rightarrow 1, 2, 3, 4$
 $\frac{0-1}{0-1} \Rightarrow 1, 2, 3, 4, 5$

$$H = I^2 R t$$

* Power of Circuit elements


$$H = I^2 R t$$

$$\frac{H}{t} = I^2 R = P$$

When current flow throo ~~the~~ conducting wire electrical energy is converted in Heat.

Heat produced Per unit time called Power.

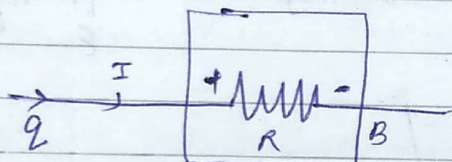Loss in energy takes place due to collisions of e^- .



$$P = \frac{W}{t} = \frac{qV}{t}$$

$$V = IR$$


$$W = qV$$

$$\text{Power } P = VI = I^2 R = \frac{V^2}{R}$$

Heat

$$H = Et$$

$$H = VIt = I^2 R t = \frac{V^2}{R} t$$

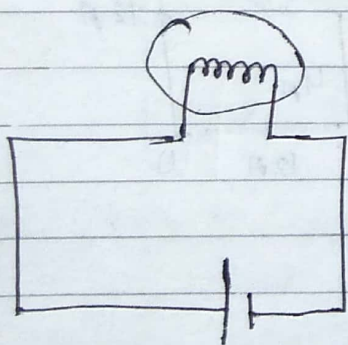

Bulb

Rating - 100W

200V bulb

max value that can work


$$P = \frac{V^2}{R}$$

$$R = \frac{V^2}{P}$$

Series C. \Rightarrow Potential diff. \rightarrow different.
 Current \rightarrow same

Series Potential Divider

* Power in a Battery

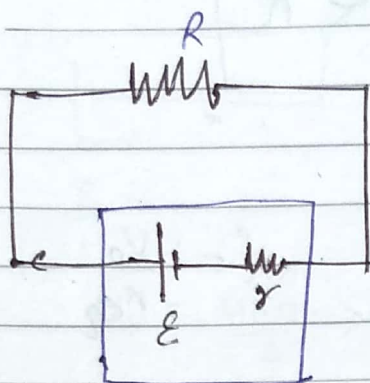

$$I = \frac{E}{R+r}$$

Pot. diff across battery
 $V = E - Ir$


$$\text{Power in battery} = VI = EI - I^2r$$

Power delivered by battery to the external circuit $EI - I^2r$.

Power loss in the battery due to int. resistance $= I^2r$.

* Combination of Resistors:

1) Series combination: (Pot. Divider).

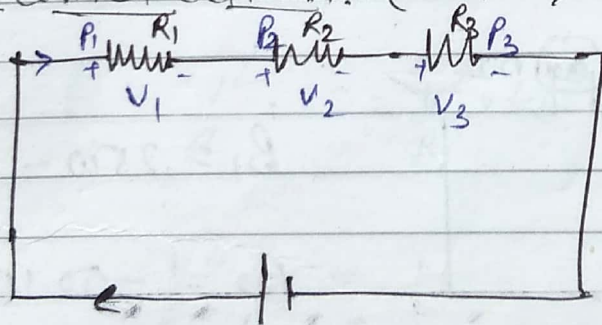

* Current in each resistor is same but potential is different.

$$-V_1 - V_2 - V_3 + V_0 = 0$$

$$V_1 + V_2 + V_3 = V_0$$

$$\begin{aligned} V_1 &= IR_1 \\ V_2 &= IR_2 \\ V_3 &= IR_3 \end{aligned}$$



$$V \propto R$$

$$\frac{V_1}{V_2} = \frac{R_1}{R_2}$$

$$P_1 = I^2 R_1$$

$$P_2 = I^2 R_2$$

$$P_3 = I^2 R_3$$

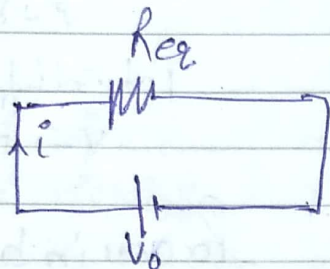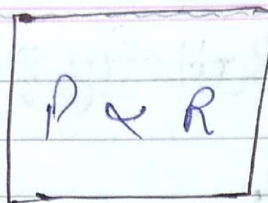


$$i = \frac{V_0}{R_{eq}}$$

$$R_{eq} = R_1 + R_2 + R_3 + \dots$$

Que:

series
filament

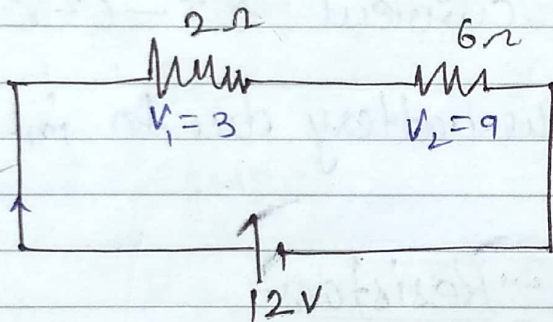


find current

$$i = \frac{12}{8} = 1.5A$$

$$\frac{V_1}{V_2} = \frac{1}{3}$$

Que:

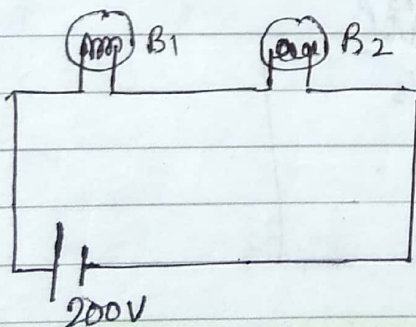

$$B_1 = 25W - 100V$$

$$B_2 = 50W - 100V$$

which bulb gets fewer.

Ans:

$$\frac{V^2}{R}$$

$$R_1 = \frac{(100)^2}{25} = 2R$$

$$R_2 = \frac{(100)^2}{50} = R$$

$$P = \frac{V^2}{R}$$

$$R = \frac{V^2}{P}$$


$$P = I^2 R$$

$$= \frac{V^2}{R^2} R = \frac{V^2}{R}$$

$$P = \frac{V^2}{R}$$

$$P = \frac{V^2}{R}$$

$$I = \frac{V}{R} : R = \frac{V}{I}$$

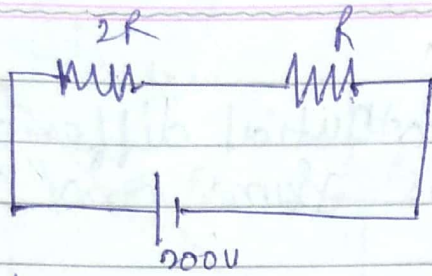

$$V \propto R$$

$$V = IR$$

↑
same

$$V = I \left(\frac{V}{R} + \frac{200}{2R} \right)$$

$$\frac{V_1}{V_2} = \frac{2}{1}$$

$$V_1 = \frac{400}{3} > 100V$$

get fused

$$V_2 = \frac{200}{3} < 100V.$$

$$\uparrow V = IR$$

Que: An electric heater boil some amount of water in 12 minute when connected to a Battery. Another heater boil same amount of water in 8 minute using same battery. How much time will it take to boil same amount of water using same Battery when both the wires connected in series

Ans

$$P = \frac{V^2}{R_1} = \frac{V^2}{R_1} \times t_1 = H$$

$$\frac{V^2}{R_2} t_2 = H.$$

$$\left(\frac{V^2}{R_1 + R_2} \right) t = H$$

$$t = \frac{H}{V^2} (R_1 + R_2)$$


$$t = \frac{H}{V^2} \times \frac{V^2}{H} (t_1 + t_2)$$

$$t = t_1 + t_2$$

Parallel \Rightarrow Pot. diff. ~~Resist~~ same
 Current — diff.

* Parallel Combination:

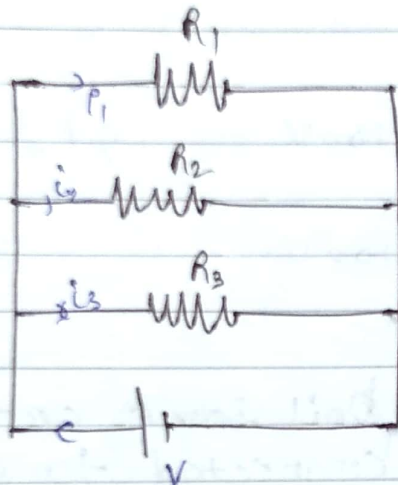In Parallel Comb. Potential difference across each Resistor is same and current is different.



$$i_1 = \frac{V}{R_1}$$


$$i_2 = \frac{V}{R_2}$$

$$i_3 = \frac{V}{R_3}$$

$$i^0 = i_1 + i_2 + i_3$$

$\frac{V}{i} = R$
 $i = \frac{V}{R}$

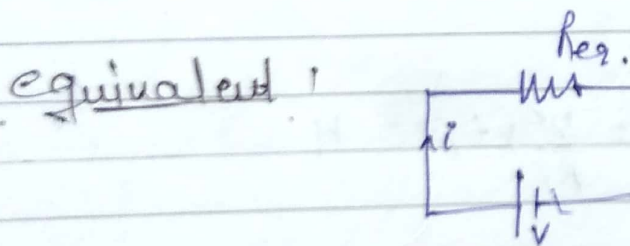
$$I \propto \frac{1}{R} = P = \frac{V^2}{R}$$



$$i^0 = \frac{V}{R_{eq}}$$

$$\frac{V}{R_{eq}} = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$

Ques:

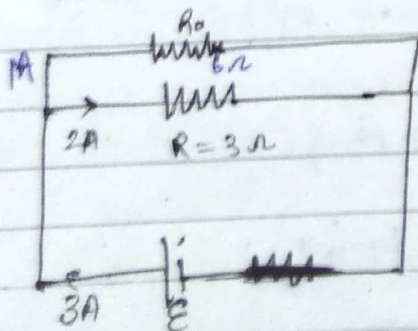

find R_0 and E

$$i^0 = \frac{E}{R} =$$

$$2 = \frac{E}{3}$$


$$1 \times R_0 = 2 \times 3$$

$$R_0 = 6 \Omega$$


$$E = 6$$

H.W: 8-1 = 5, 11, 13, 14, 16, 17, 18, 19
Race

A = Series
V = Parallel

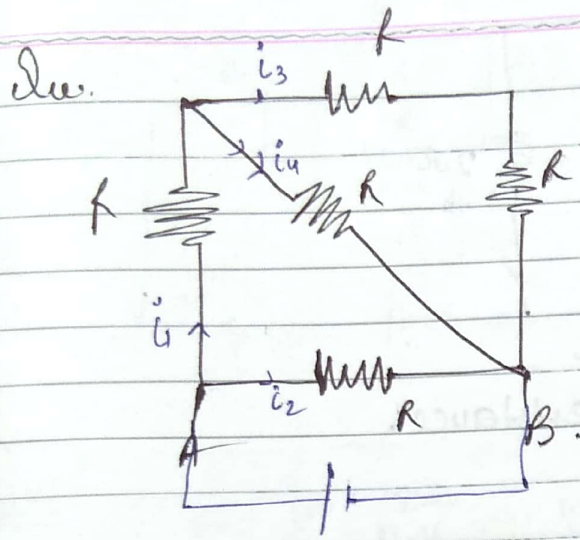

Find Req b/w A & B

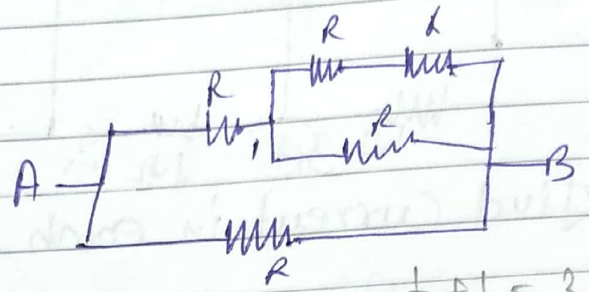


$$\frac{1}{2} + 1 = \frac{3}{2}$$

$$= \frac{2}{3} + 1 = \frac{5}{3}$$

$$\frac{1}{\frac{5}{3}} + 1 = \frac{8}{5}$$

$$= \frac{5}{8}$$

Que:

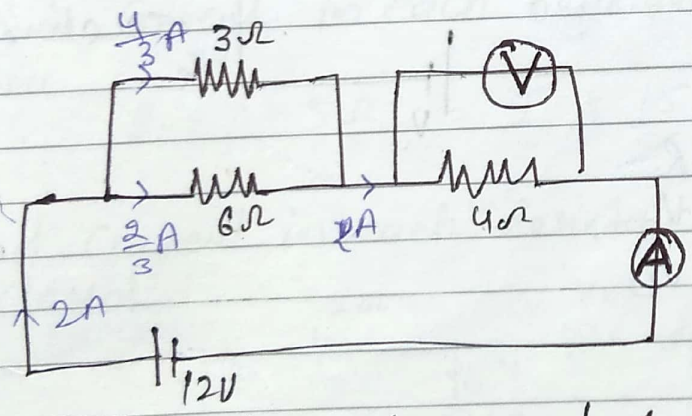


Find reading of A and V.

Ans:

$$A = 2A$$

$$V = 8$$
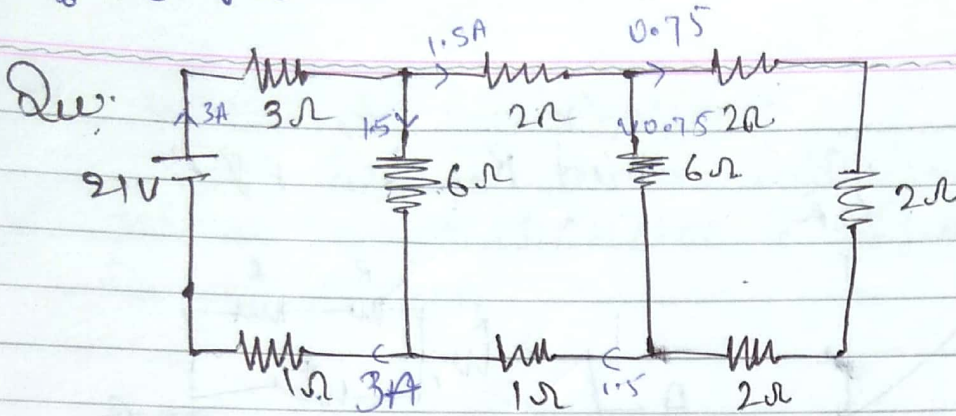
$$\frac{1}{6} + \frac{1}{6} = \frac{1}{R_{eq}}$$




Find current in each resistance.

$$R_{eq} = 7\Omega$$

$$R = 0$$

Qw:

Short Circuit

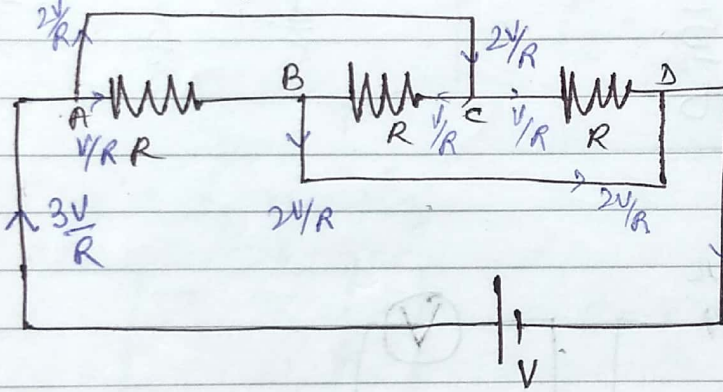

Find:

- (i) $R_{eq} = ?$
- (ii) Current in each resistance

$$V = IR$$


$$V_A = V_C$$

$$V_B = V_D$$

Short Circuit: When two points are connected by a wire of negligible resistance potential of both the point becomes equal and they are called short circuit.

Method of equipotential point?

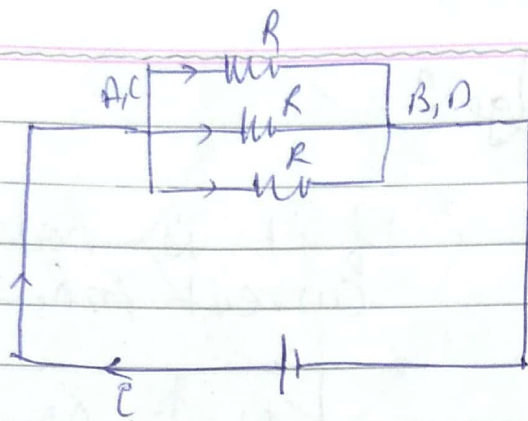
In any circuit all the points having same potential can be considered as a single point.



$$R_{eq} = \frac{R}{3}$$

$$I = \frac{3V}{R}$$


Que 0

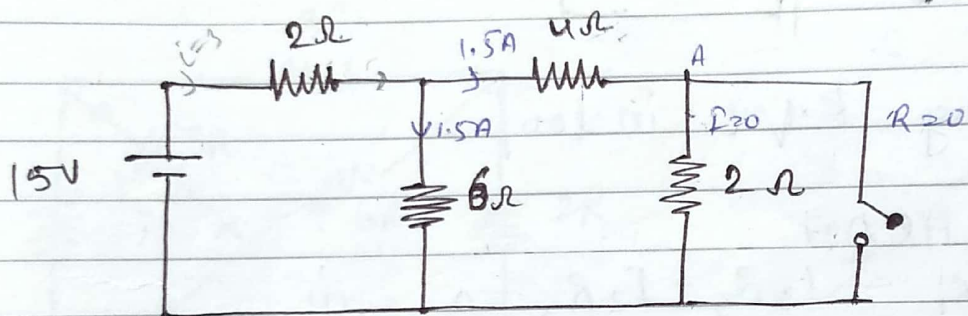

i) Find Current in each resistance when switch is open

Ans $R_{eq} = 5\Omega \Rightarrow I = \frac{15}{5} = 3A$

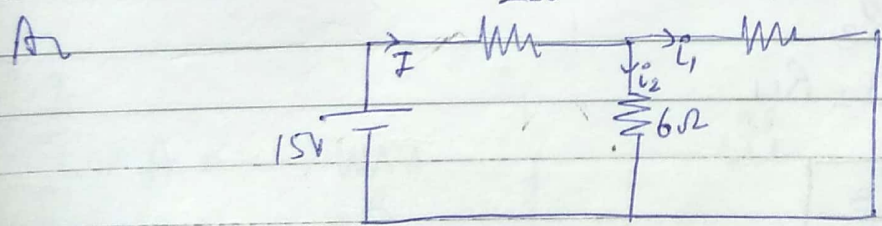ii) Find Current in each Resistance when switch is closed.




$$I = \frac{15}{R_{eq}} \quad \frac{I_1}{I_2} = \frac{3}{2}$$

$$I_1 + I_2 = I$$

~~Imp.~~

Wheatstone Bridge

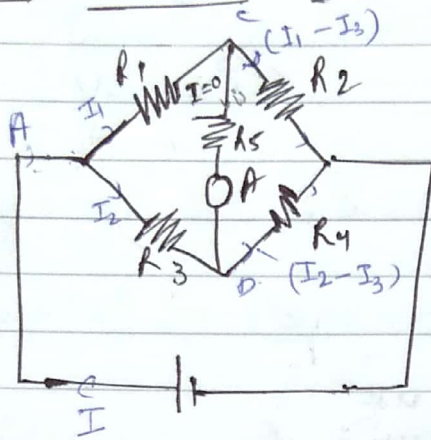

If it is balanced
current in $R_5 = 0$

$$\frac{R_1}{R_2} = \frac{R_3}{R_4}$$

Applying K.V.L in loop

ACDA

$$-I_1 R_1 - I_3 R_5 + I_2 R_3 = 0 \quad \text{--- (1)}$$

loop CBDC

$$(I_1 - I_3) R_2 + (I_2 + I_3) R_4 + I_3 R_5 = 0 \quad \text{--- (2)}$$

If W.S.B is balanced


$$I_3 = 0$$

$$I_1 R_1 = I_2 R_3$$

$$I_1 R_2 = I_2 R_4$$

$$\frac{R_1}{R_2} = \frac{R_3}{R_4}$$


Que:

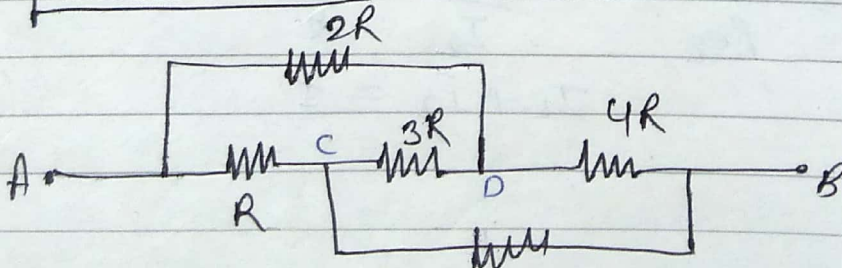

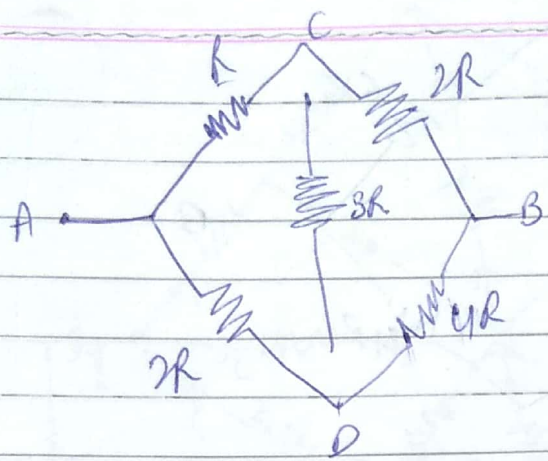i) Req b/w A and B.



$\frac{3R \cdot 1R}{3R + 1R} + \frac{2R \cdot 4R}{2R + 4R}$
 $\frac{3R}{4} + \frac{8R}{6}$
 $\frac{9R}{4} + \frac{4R}{3}$
 $\frac{27R + 16R}{12}$
 $\frac{43R}{12}$

H.C.V. = P-187 Rec.
 Solved ex: 1-7, 9-17,
 EX: 4, 24, 28, 32, 33, 34.



$R_{eq} = 2R$

Ex:

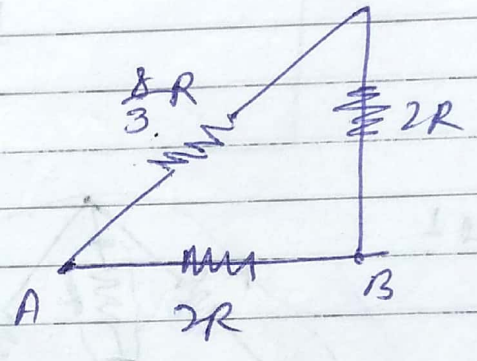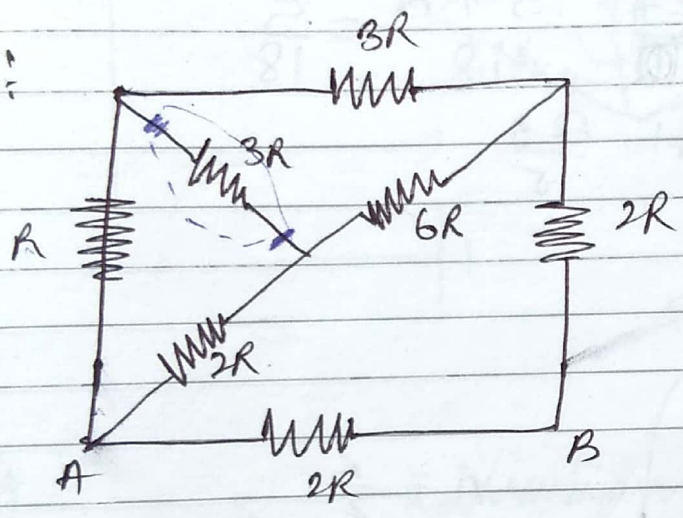


$\frac{14R}{3}$

$\frac{3}{14R} + \frac{1}{2R}$

$\frac{14R}{10} = \frac{7R}{5}$


$\frac{3+7}{14R}$

Q.2

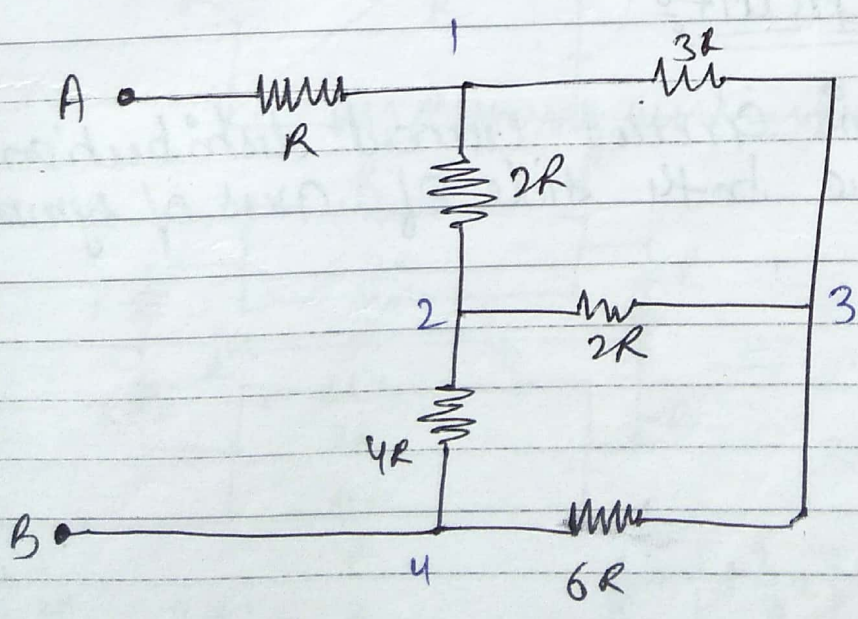

$$\frac{1}{4} + \frac{1}{6}$$


$$\frac{1+}{9}$$

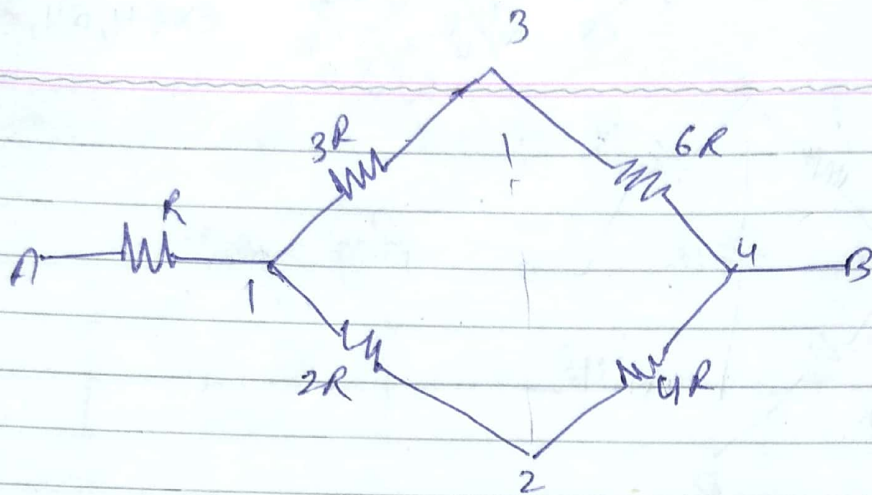

$$\frac{1}{6} + \frac{1}{9} = \frac{3+2}{18} = \frac{5}{18}$$

$$\frac{18}{5} + 1 = \frac{23}{5}$$

Ques 1

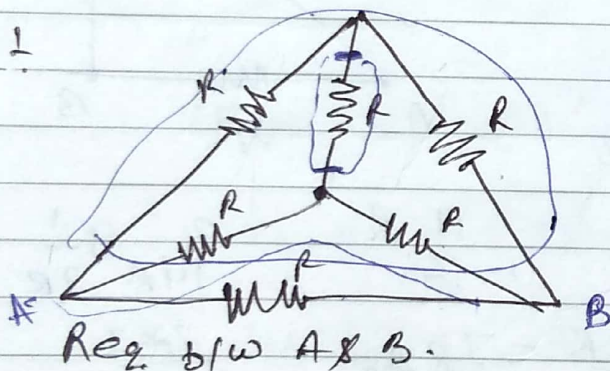


$$R_{eq} = \frac{R}{2}$$

* Symmetric Circuit:


In a symmetric circuit current distribution is same on the both side of axis of symmetric.

Ex-1

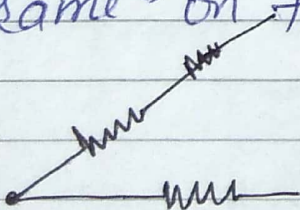


~~Ques~~ \times


Ex:

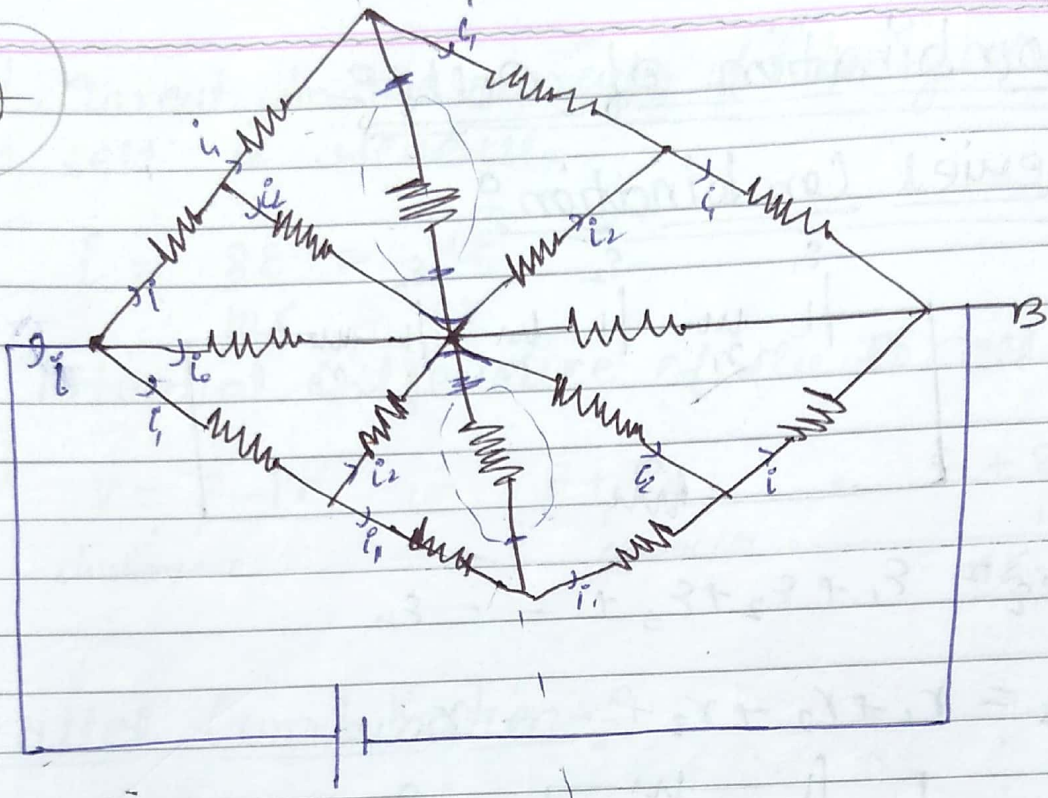

Ques:

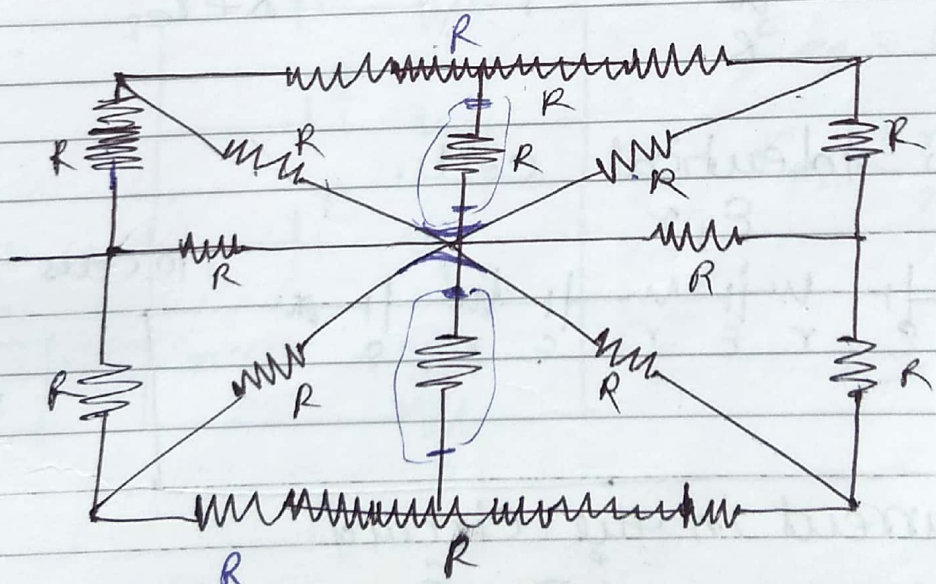

$$\frac{4R}{3} \quad 2R$$

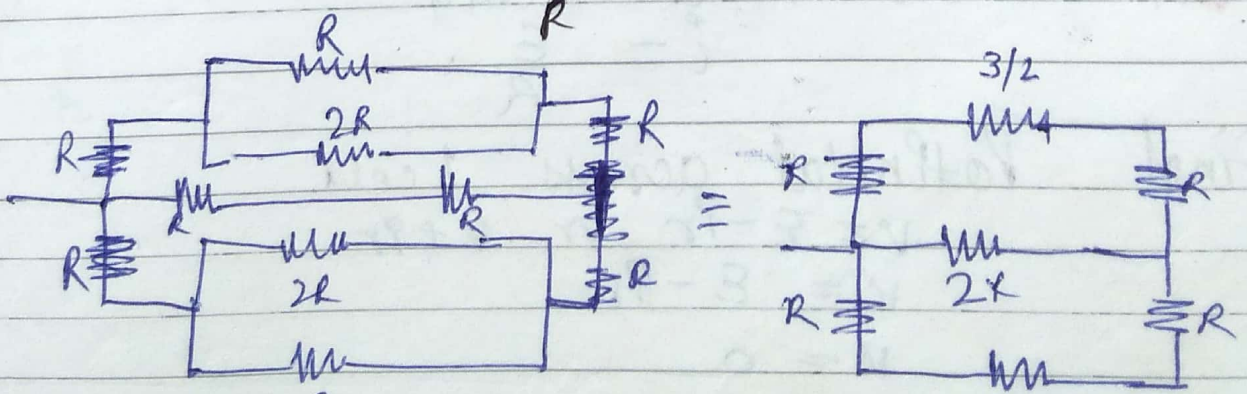

$$\frac{1}{R} + \frac{1}{2R} =$$


$$\frac{2+1}{2} = \frac{3}{2}$$

$$\frac{1}{\frac{1}{R} + \frac{1}{2R} + \frac{1}{\frac{1}{R} + \frac{1}{2R}}} = \frac{3+2+3}{3} = \frac{8}{3}$$

$$= \frac{9}{8} \Omega$$


* Combination of Cells

1) Series Combination

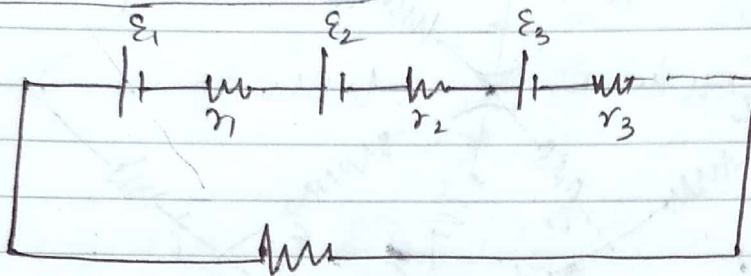


$$\mathcal{E}_{eq} = \mathcal{E}_1 + \mathcal{E}_2 + \mathcal{E}_3 + \dots + \mathcal{E}_n$$
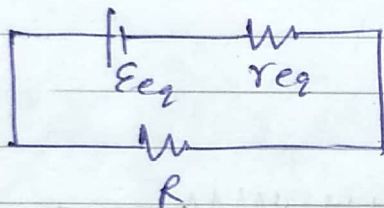
$$r_{eq} = r_1 + r_2 + r_3 + \dots + r_n$$



$$I = \frac{\mathcal{E}_{eq}}{R + r_{eq}}$$

Qw: 10 identical cells.

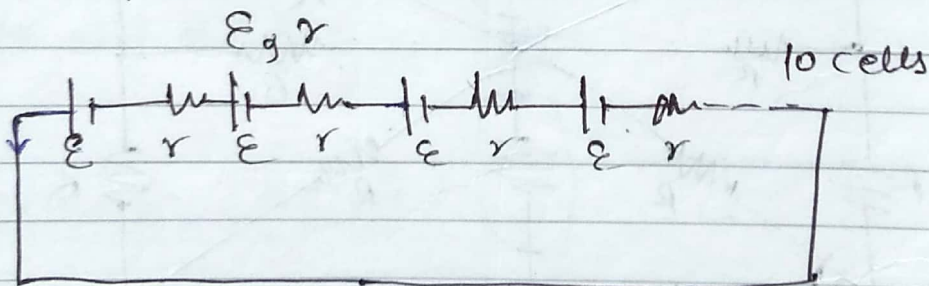

i) Find current in the circuit

$$I = \frac{\mathcal{E}}{R}$$

ii) Find potential across 1 cell.

$$V = \mathcal{E} - Ir \quad \text{or} \quad \mathcal{E} + Ir$$

$$V = \mathcal{E} - Ir$$

$$V = 0$$

$$H.C.V = \sum \epsilon = 18, 24, 23, 25,$$

$$\sum \epsilon = 17, 18, 19, 23, 25, 27, 28, \dots = 31$$

$$41 - 45$$

iii) Find current in the circuit if polarity of one of the cell is reverse.

$$i = \frac{8\epsilon}{10r} = \frac{4\epsilon}{5r}$$


Find Potential Difference of the cell.

$$V = \epsilon - ir \quad \text{or} \quad \epsilon + ir = \epsilon + \frac{8\epsilon}{10} = 9\epsilon$$

discharge \rightarrow change \rightarrow

* 2) Parallel Combination

(1) Identical Cells

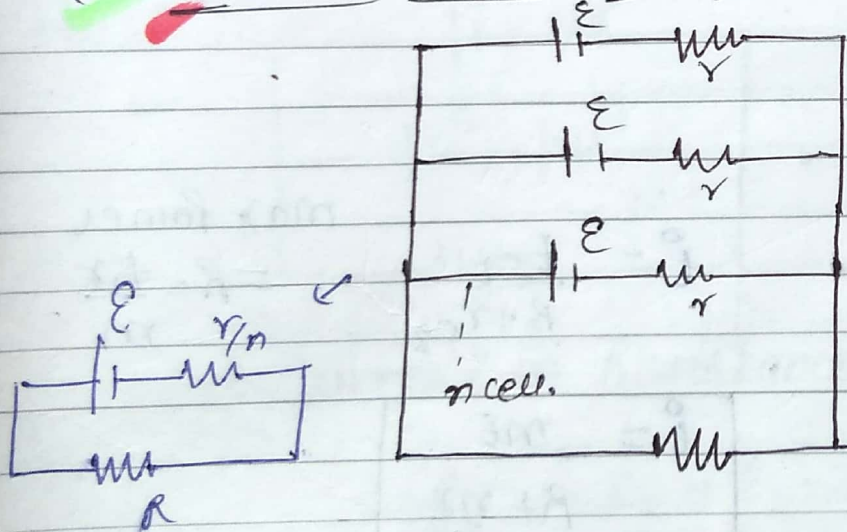


$$E_{eq} = \epsilon$$

$$r_{eq} = \frac{r}{n}$$

$$i = \frac{\epsilon}{R + \frac{r}{n}}$$


* Mixed Combination!

Identical cells!

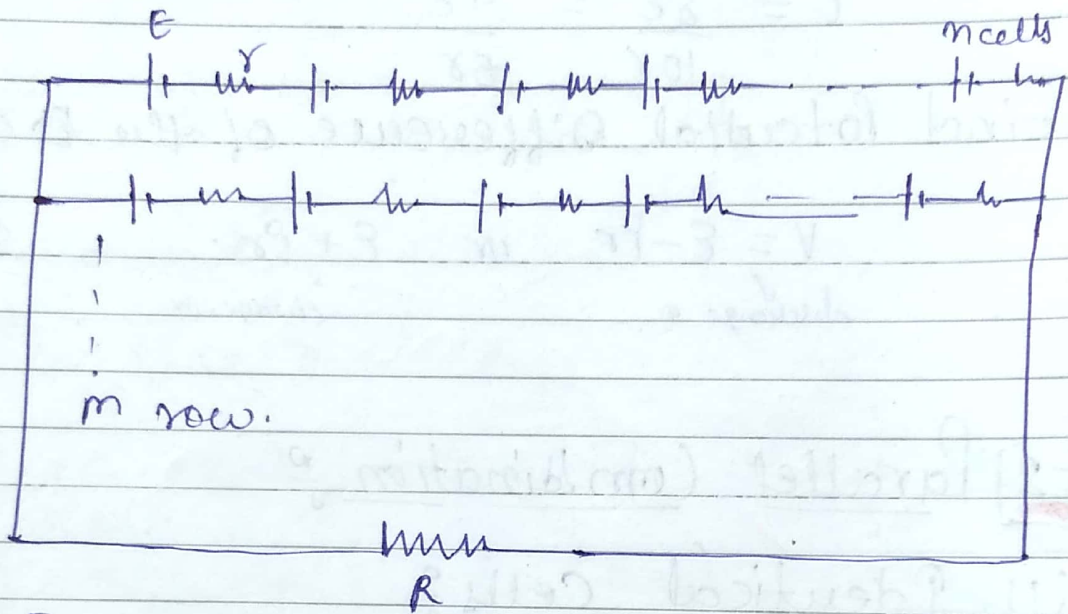

$$E_{eq} = nE$$

$$r_{eq} = \frac{nr}{m}$$

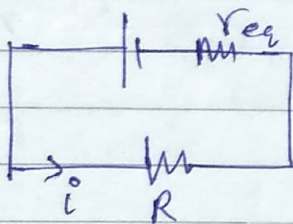


$$i = \frac{E_{eq}}{R + r_{eq}}$$

max power
 $= R = \frac{nr}{m}$

$$i = \frac{nE}{R + \frac{nr}{m}}$$

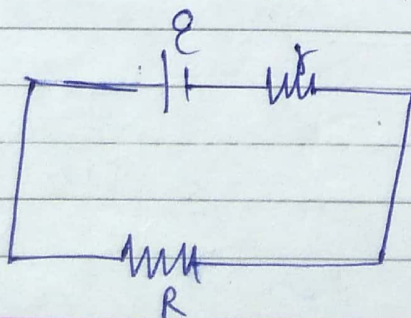* Maximum Power transfer ~~power~~ theorem



$$i = \frac{E}{R + r}$$

$$P_R = i^2 R$$

$$P_R = \frac{E^2 R}{(R + r)^2}$$

MAX

for maximum power

$$\frac{dP}{dR} = 0$$

$$= \frac{\epsilon^2 [(R+r)^2 - 2R(R+r)]}{(R+r)^4} = 0$$



$$(R+r)^2 - 2R(R+r) = 0$$

$$R+r - 2R = 0$$

$$R = r$$

$$P_{\max} = \frac{\epsilon^2}{4R} = \frac{\epsilon^2}{4r}$$

Que:

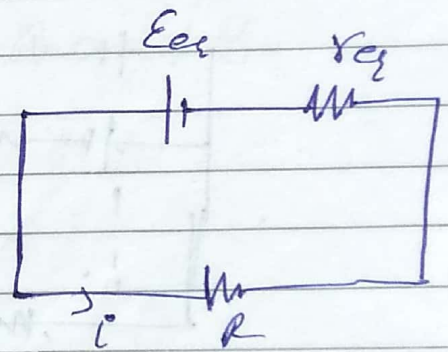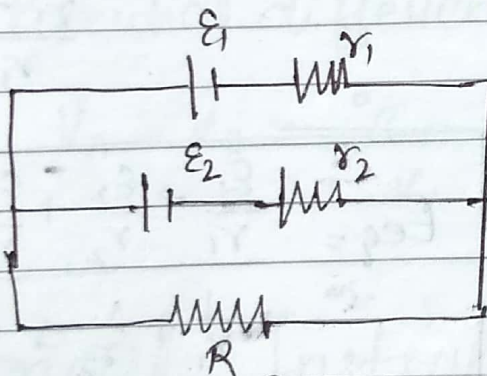

find current in Resistance in R.

Ans:

$$-iR - i_2 r_2 + \epsilon_2 = 0$$

$$iR + i_2 r_2 = \epsilon_2 \times r_1$$

$$iR + i_1 r_1 = \epsilon_1 \times r_2$$

$$iR(r_1 + r_2) + (i_1 + i_2)(r_1 r_2) = \epsilon_1 r_2 + \epsilon_2 r_1$$

$$P(R(r_1 + r_2) + r_1 r_2) = \epsilon_1 r_2 + \epsilon_2 r_1$$

$$i = \frac{E_1 r_2 + E_2 r_1}{R(r_1 + r_2) + r_1 r_2}$$


$$i = \frac{\frac{E_1 r_2 + E_2 r_1}{r_1 + r_2}}{R + \frac{r_1 r_2}{r_1 + r_2}}$$

$$E_{eq} = \frac{E_1 r_2 + E_2 r_1}{r_1 + r_2} \quad E_{eq} = \frac{E_1 r_1 + E_2 r_2}{r_1 + r_2}$$

$$r_{eq} = \frac{r_1 r_2}{r_1 + r_2}$$

$$E_{eq} = \frac{E_1 r_2 + E_2 r_1}{\frac{r_1 r_2}{r_1 + r_2}}$$


clear

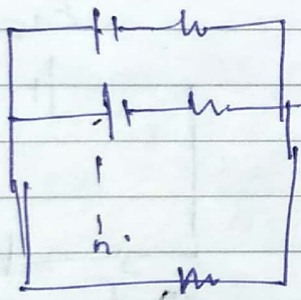

$$E_{eq} = \frac{\frac{E_1}{r_1} + \frac{E_2}{r_2} + \frac{E_3}{r_3} + \dots}{\frac{1}{r_1} + \frac{1}{r_2} + \frac{1}{r_3} + \dots}$$

Impedance

Ques:

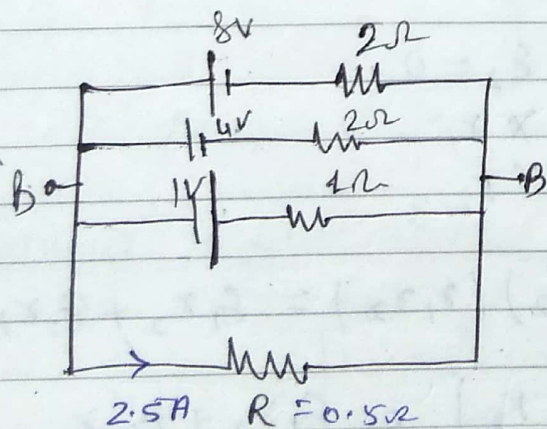

$$\frac{1}{\frac{1}{2} + \frac{1}{2} + 1} = \frac{1 + 2}{2} = \frac{3}{2}$$

(i) Find R. Show that power in it is maximum


$$\frac{1}{R_{eq}} = \frac{1}{2} + \frac{1}{2} + 1$$

$$R_{eq} = \frac{1}{2} = 0.5 \Omega$$

ii) Find current in R.

$$I = \frac{V}{R}$$

$$E_{eq} = \frac{4 + 2 - 1}{2} = 2.5 V$$

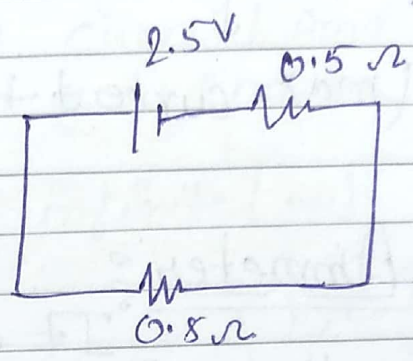


$$I = 2.5 A$$

viii) Find Potential difference b/w A and B.

$$V_A - V_B = iR = 1.25 V$$

* Electrical Instruments :

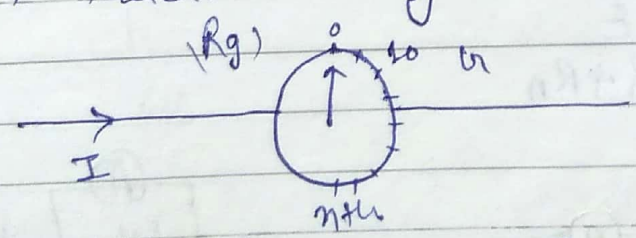1. Galvanometer : It detects the presence of current in any branch of the circuit. It can tolerate only small current.



$$\text{Current Sensitivity} = \frac{\text{Current}}{\text{deflection/division}} = I_0$$

$n = \text{no. of division.}$

full scale deflection current $I_g = n I_0 (\approx \text{mA})$



(max. current that galvanometer can tolerate)


2) Ammeter



It can measure any amount of current in the circuit because its range can be increased.

Ammeter is always applied in series combination


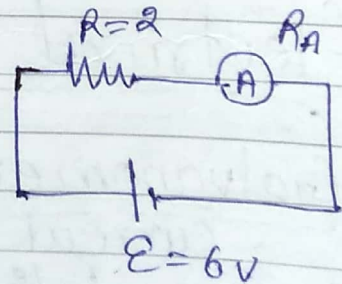
* Its resistance should be very small for ideal ammeter resistance should be zero. So that presence of ammeter does not affect the magnitude of current.



$$i = \frac{E}{R}$$

$$i_1 = \frac{E}{R + R_A}$$

Ques

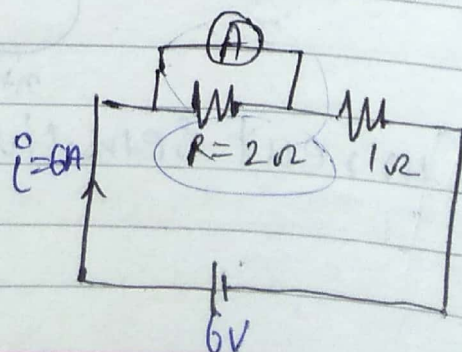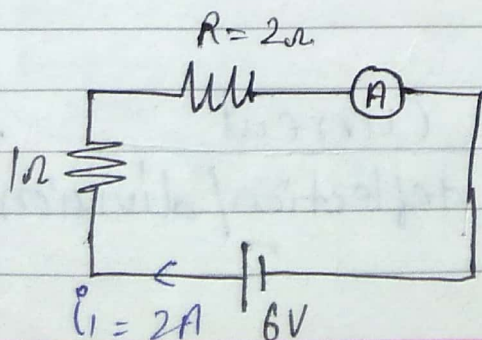

H.W: 8-1 > upto 20 Ques. 45 Ques left.


0-1: upto 46 Ques.

0-2: 1, 2, -8 Ques. 10, 11, 12

3) Voltmeter: It major Potential difference b/w any two points. It is always applied in Paralleled combination so #

Its resistance should be very high. So that due to presence of voltmeter current and Potential difference do not gets change.

Resistance of Voltmeter is infinite (∞).

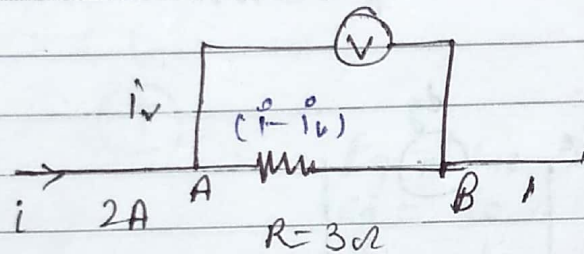



$R_v \uparrow$ $R_{nd} \downarrow$

$$V_A - V_B = IR$$

$$V_A - V_B = (i - i_v)R$$


$$\text{Ideal voltmeter} = R \approx \infty$$

Ex: find reading of Volt meter

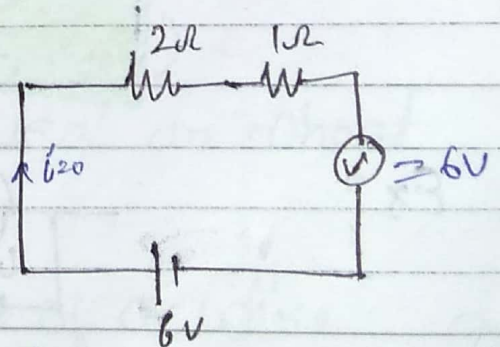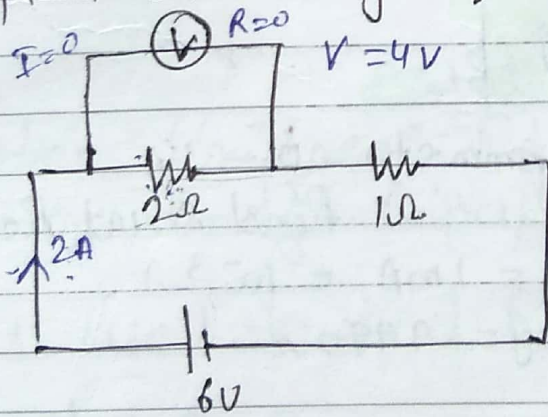

$$i = \frac{6}{2+1+R_v} = 0$$


* Conversion of Galvano meter into Ammeter

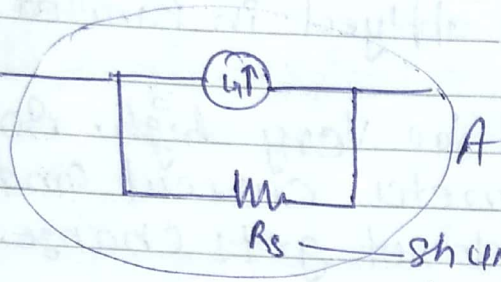

Range 0 - I_0 Amp

R_s - shunt resistance
 \rightarrow low resistance

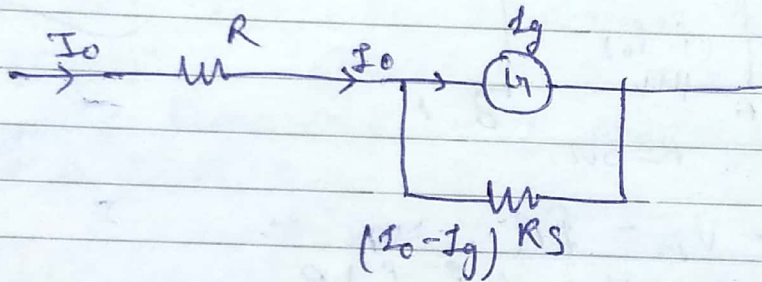I_g - full scale deflection current \approx mA




$$\frac{1}{R_A} = \frac{1}{R_g} + \frac{1}{R_s}$$

$$I_g R_g = (I_0 - I_g) R_s$$

$$R_s = \frac{I_g R_g}{I_0 - I_g}$$

Ex^o

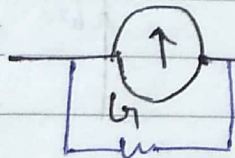

Ammeter 0 - 1 A

find shunt Resistance

$$I_g = 1 \text{ mA} = 10^{-3} \text{ A}$$

$$R_g = 9990 \Omega$$

$$= \frac{10^{-3} \times 9990}{1 - 0.001} \text{ A}$$

$$= \frac{10^{-3} \times 9990}{.999} = 10 \Omega$$

Ammeter 0 - 100 A

$$R_s = \frac{10^{-3} \times 9990}{10^2 - 10^{-3}}$$


$$R_s = 9990 \times 10^{-5}$$

$$= 0.099 \Omega$$

$$= 0.1 \Omega$$

50/150

② Conversion of galvanometer into Voltmeter

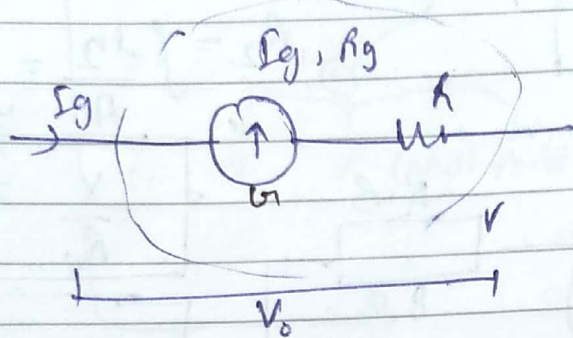


Voltmeter 0 - V_0

$$I_g R_g + I_g R = V_0$$

$$R = \frac{V_0}{I_g} - R_g$$

Que!

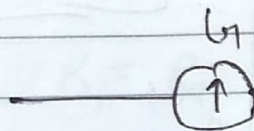

$I_g = 1 \text{ mA}$
 $R_g = 50 \Omega$
 Voltmeter = 0 - 3V
 Find R.

$$I_g R = V_0 - I_g R_g$$

$$I_g (R - R_g) = V_0$$

$$I_g = \frac{V_0}{R - R_g}$$

$$R = \frac{V_0}{I_g} - R_g$$


$$R = \frac{3\text{V}}{10^{-3}} - 50 = 2950$$

(slide wire Bridge)

* Meter Bridge = It is based on wheat stone bridge principle.

It is used to find Resistance of a wire

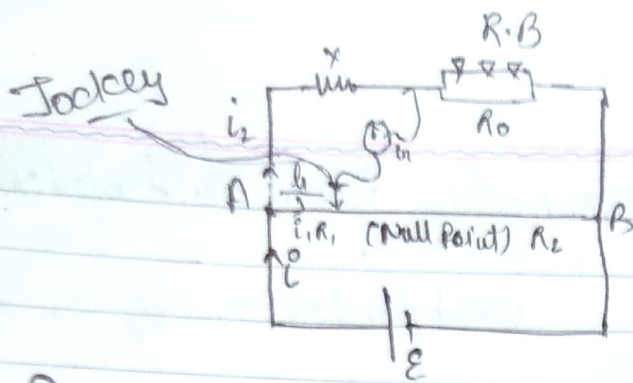It is based Its working is based on Null point method.



$$L_{AB} = 1m = 100cm$$

$$R_{AB} = \int \frac{d}{A} = R_0$$


$$R_1 = \int \frac{d_1}{A} \quad , \quad l$$

$$R_2 = \int \frac{d_2}{A} = \int \frac{100-l}{A}$$

$$\frac{x}{R_0} = \frac{R_1}{R_2}$$


$$\frac{x}{R_0} = \frac{l}{100-l}$$

Q.1

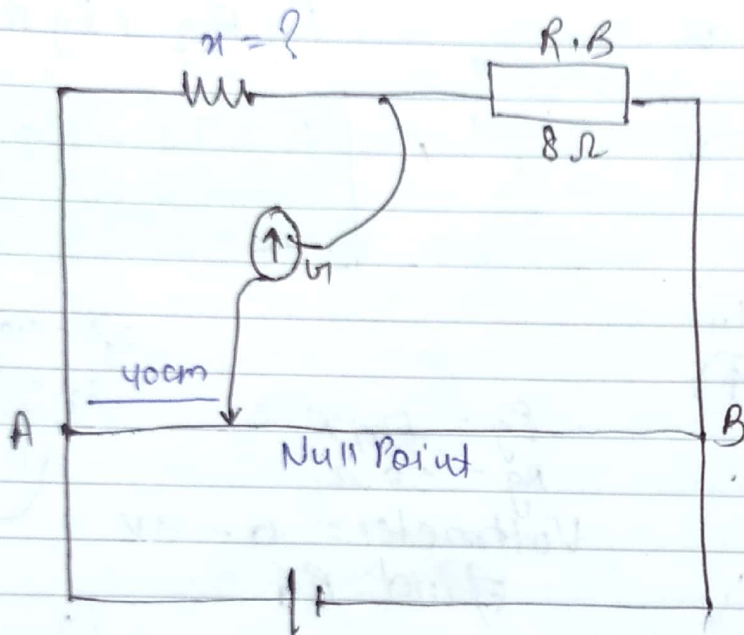

$$= \frac{x}{8} = \frac{16}{\frac{64}{3}} = \frac{16}{3}$$

Q.2

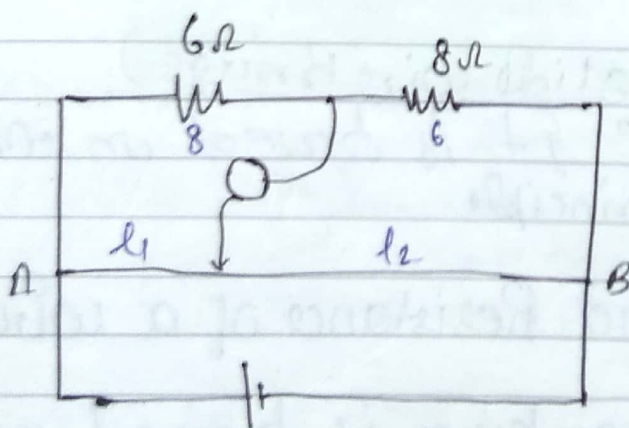

Find shift in the position of Null Point if resistances are interchange.

Ans:

$$\frac{6}{8} = \frac{l_1}{100-l_1}$$

$$l_1 = \frac{300}{7}$$

$$\frac{8}{6} = \frac{l_2}{100-l_2}$$


$$l_2 = \frac{400}{7}$$

$$\text{null point shift} = l_2 - l_1 = \frac{400}{7} - \frac{300}{7} = \frac{100}{7} \text{ cm}$$

$$R_{eq} =$$

C + R


Ques 0

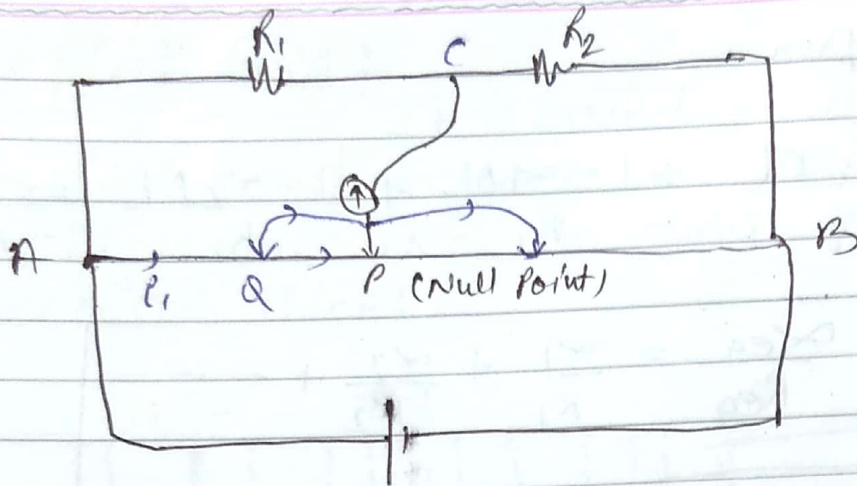

Null point at jockey at left

Q-17

$$R = R_0 (1 + \alpha \Delta t)$$

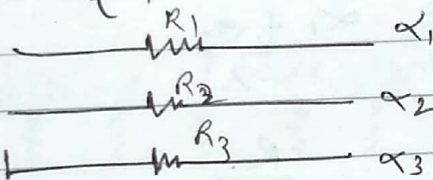

$$R_{eq} = R_1 + R_2 + R_3$$

$$R_{eq}(1 + \alpha_{eq} \Delta t) = R_1(1 + \alpha_{eq1} \Delta t) + R_2(1 + \alpha_{eq2} \Delta t) + R_3(1 + \alpha_{eq3} \Delta t)$$

$$R_{eq} \alpha_{eq} \Delta t = R_1 \alpha_{eq1} \Delta t + R_2 \alpha_{eq2} \Delta t + R_3 \alpha_{eq3} \Delta t$$

$$\alpha_{eq} = \frac{R_1 \alpha_1 + R_2 \alpha_2 + R_3 \alpha_3}{R_1 + R_2 + R_3}$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$

$$\frac{1}{R_{eq}(1 + \alpha_{eq} \Delta t)} = \frac{1}{R_1(1 + \alpha_1 \Delta t)} + \frac{1}{R_2(1 + \alpha_2 \Delta t)} + \frac{1}{R_3(1 + \alpha_3 \Delta t)}$$

$$= \frac{(1 + \alpha_{eq} \Delta t)^{-1}}{R_{eq}} = \frac{(1 + \alpha_1 \Delta t)^{-1}}{R_1} + \frac{(1 + \alpha_2 \Delta t)^{-1}}{R_2}$$

Binomial approx:


$$\frac{1 - \alpha_{eq} \Delta t}{R_{eq}} = \frac{1 - \alpha_1 \Delta t}{R_1} + \frac{1 - \alpha_2 \Delta t}{R_2} + \frac{1 - \alpha_3 \Delta t}{R_3} + \dots$$

$$\frac{\alpha_{eq}}{R_{eq}} = \frac{\alpha_1}{R_1} + \frac{\alpha_2}{R_2} + \dots$$

$$\frac{\alpha_{eq}}{R/2} = \frac{\alpha_1}{R} + \frac{\alpha_2}{R}$$

$$\alpha_{eq} = \frac{\alpha_1 + \alpha_2}{2}$$

Note:

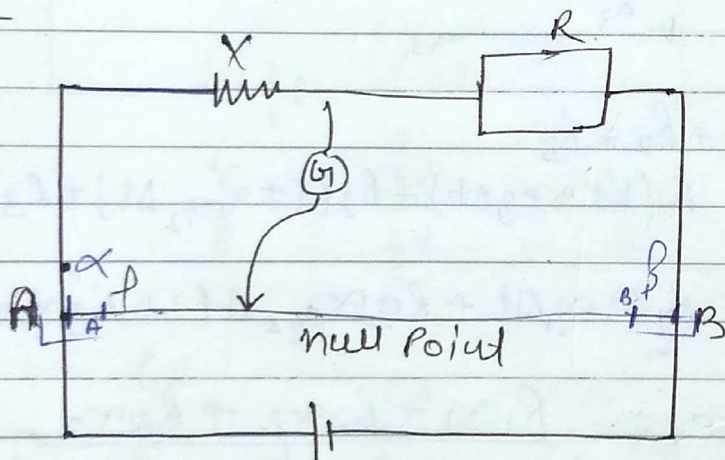



$$\frac{x}{R} = \frac{l}{100 - l}$$

If meter bridge is most sensitive or meter bridge gives accurate reading when null point is obtained at the mid point of wire AB.

* Ends correction $\frac{x}{R} = \frac{l + \alpha}{100 - l + \beta}$

* Post office Box :-

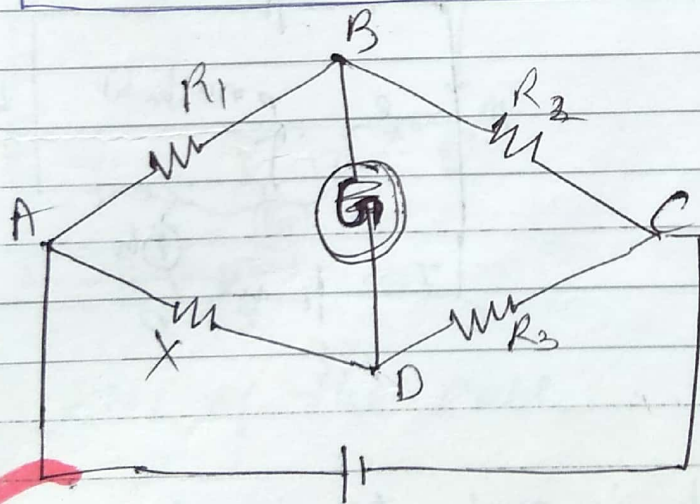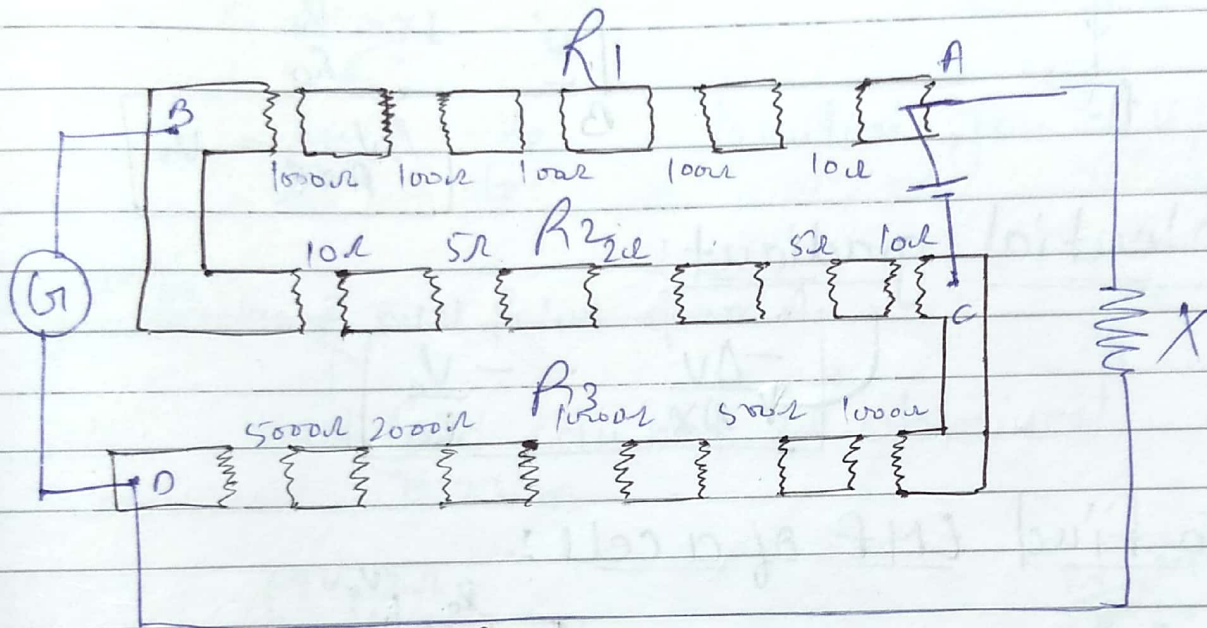It is based on wheat stone bridge. It is used to measure Resistance of a wire. It is also used to find any breakage in electrical lines




$$\frac{R_1}{n} = \frac{R_2}{R_3}$$

* Potentiometer :- It is used to find Potential difference b/w any two points. It is also used to measure and compared EMF and Internal Resistance of the cells. It is better device than Voltmeter

H.W: 0-2 ⇒ Q(9,13) left 11 Que.
 J-M: 1 to 10 Que

It is based on null point method.

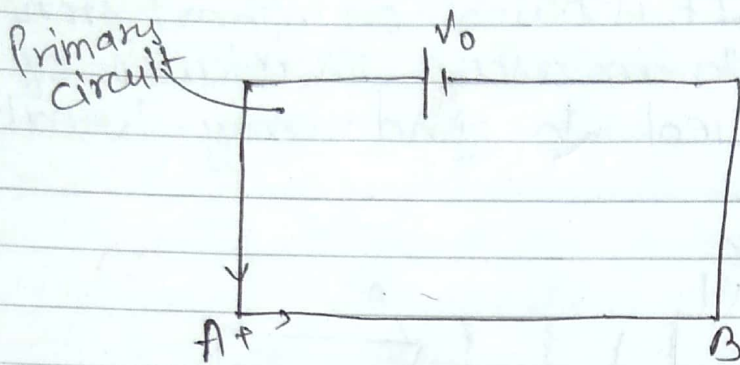

$$L_{AB} = L_0$$

$$R_0 = \frac{\rho L_0}{A}$$

$$i = \frac{V_0}{R_0}$$

$$\Delta V_{A \rightarrow B} = V_0$$

Potential gradient!


$$\frac{-\Delta V}{\Delta X} = -\frac{V_0}{L_0}$$

pot. grad

1) To find EMF of a cell:

$$E = \Delta V_{A \rightarrow P}$$


$$E = \frac{V_0 \rho}{L_0 A}$$

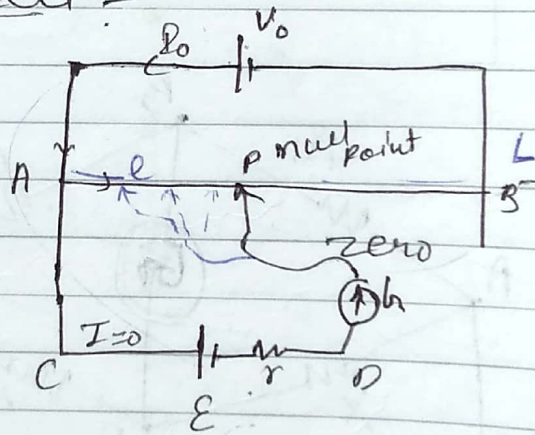

* If $E > V_{AB}$ \Rightarrow

then null point is not obtained.

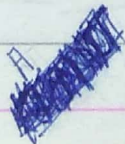2) If cell is connected opposite to primary cell,



$$\frac{24}{200}$$


$$\frac{24}{200}$$

$$\frac{150}{200}$$

$$\frac{V_0}{l_0} = \frac{24}{200}$$

$$\frac{1}{10} = 0.1$$

Que

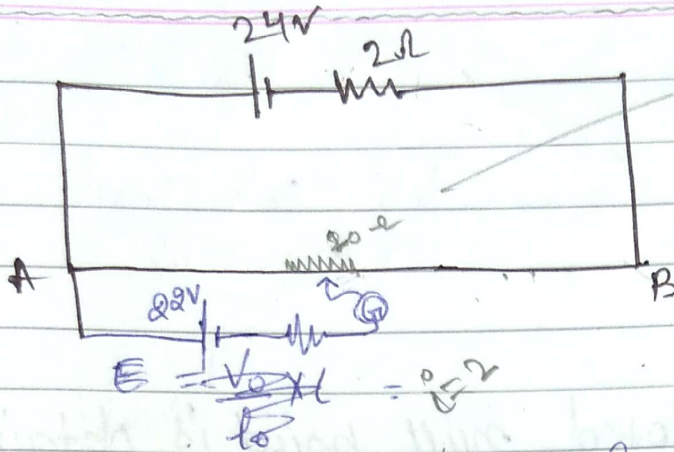

$$L_{AB} = 200 \text{ cm.}$$

$$R_{AB} = 10 \Omega.$$

find potential gradient

$$V_B = iR = 20 \text{ Volt}$$

$$V = \frac{24}{10} = 2.4$$

Ans


$$\frac{-\Delta\phi}{\Delta x} = \frac{-V_0}{l_0}$$

Potential gra. 0.1 V/cm.

$$= \frac{V_0}{l_0} = \frac{24}{200} = 0.1$$

find distance null point from A.

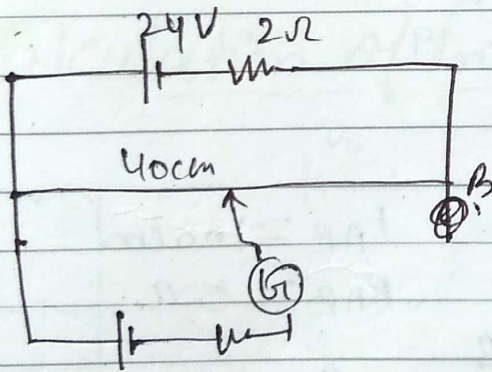Here null point can not be obtained because $E > V_{AB}$




$$\frac{24}{40} \times 20 = 12$$

find EMF of the cell = $E = \frac{V_0 \times l_0}{l}$

$$0.1 \times 40 = 4 \text{ V}$$

Que

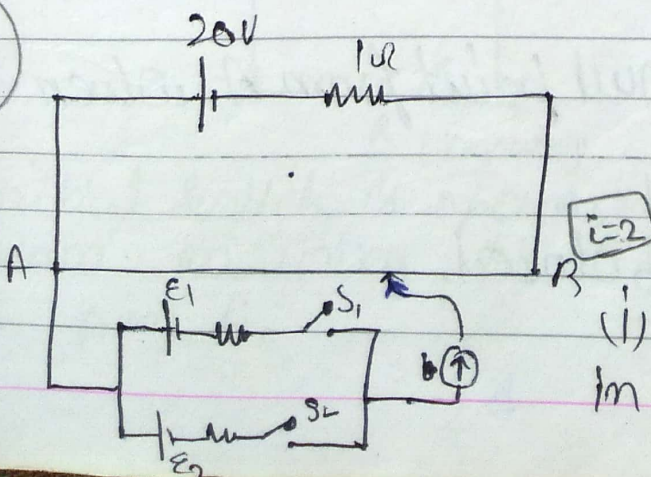

$$R_{AB} = 9 \Omega$$

$$L_{AB} = 100 \text{ cm.}$$

$$\frac{18}{100} = \frac{20}{10} = 2$$

(i) find potential gradient in potentiometer wire.

$$E = \frac{V_0}{l_0} \times l$$

$$I = 2A$$

$$V_0 = IR_0$$

$$= 18V$$

$$\frac{V_0}{l_0} = 0.18 \text{ V/cm}$$


When switch S_1 is closed null point is obtained at 30 cm from A. When only S_2 is closed null point is obtained 50 cm from A

find $\frac{E_1}{E_2}$?

Ans:
$$\frac{E_1}{E_2} = \frac{l_1}{l_2} = \frac{3}{5}$$

$$E_1 = 5.4 = 0.18 \times 30 = 5.4$$

$$E_2 = 9 = 0.18 \times 50 = 9$$

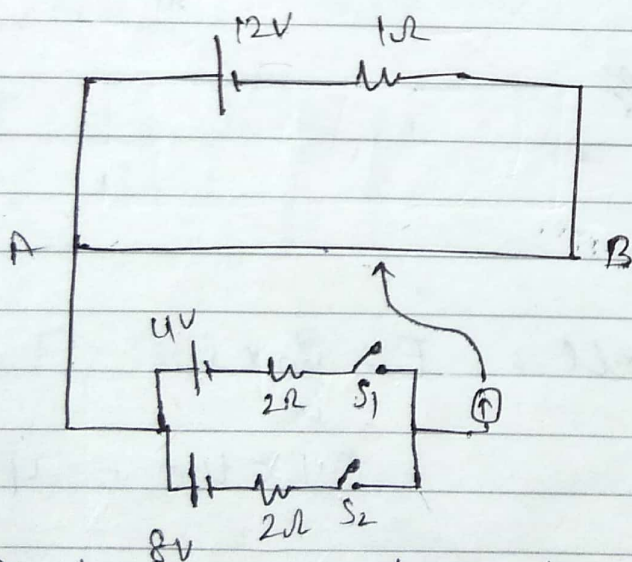

$$L_{AB} = 100 \text{ cm}$$

$$R_{AB} = 5 \Omega$$

$$I = 2A \quad \checkmark$$

$$\frac{V_0}{l_0} = \frac{7}{100} = 0.07$$

- (1) Find distance of null point from A when
 - (i) only S_1 is closed 40
 - (ii) only S_2 is closed 80
 - (iii) S_1 and S_2 are closed. 60

$$P = 2A \quad \checkmark$$

 ϵ_2

$$V_{AB} = V_0 = 10V \quad \checkmark$$

$$L_0 = 100 \text{ cm}$$

$$\epsilon = \left(\frac{V_0}{L_0} \right) l$$

$$u = \frac{10}{100} \times l_1$$

$$l_1 = 40 \text{ cm}$$


$$s = \frac{10}{100} \times l_2$$

$$l_2 = 80 \text{ cm}$$

$$\rightarrow \epsilon_{eq} = \frac{2+4}{1}$$

$$\epsilon_{eq} = 6V$$

* Calculation of Internal Resistance :

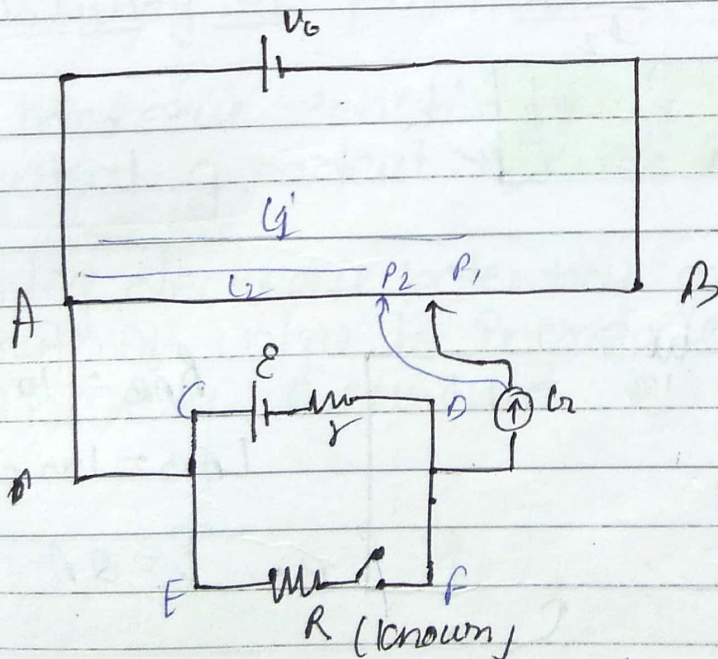

$$L_{AB} = L_0$$

$$V_{AB} = V_0$$

$$\text{Pot. grad.} = \frac{V_0}{L_0}$$

Initial switch is open and null point is obtained on wire AB let it is at dist. l_1 from A.

$$E = \frac{V_0}{l_0} l_1$$

(ii) Now switch is closed and again null point is obtained on wire AB. Let it is at distance l_2 from A.

Ans:

$$E = \frac{V_0}{l_0} l_1 \quad \text{--- (i)}$$

$$I = \frac{E}{R+r}$$

$$IR = \left(\frac{V_0}{l_0} \right) l_2 \quad \text{--- (ii)}$$


$$\frac{E}{IR} = \frac{l_1}{l_2}$$

$$\frac{R+r}{R} = \frac{l_1}{l_2}$$

$$R+r = \frac{l_1}{l_2} R$$

$$r = R \left(\frac{l_1}{l_2} - 1 \right)$$

Que:

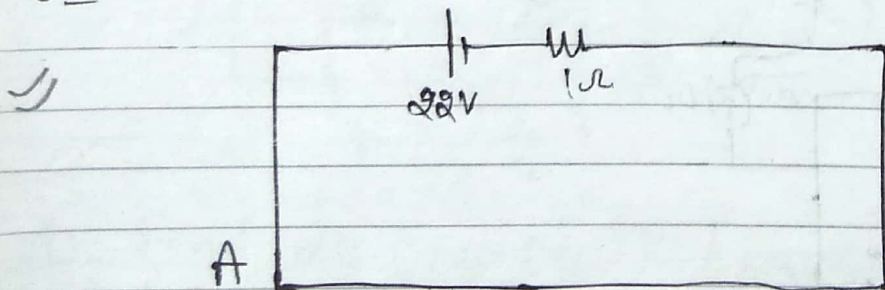

$$R_{AB} = 10 \Omega$$

$$L_{AB} = 100 \text{ cm}$$

$$I = 2 \text{ A}$$

$$R = 1 \Omega$$

(9) When only S_1 is closed, null point at 80 cm from A. When S_1 and S_2 are closed then null point at 40 cm from A find E_1 and R_1 .

Ans: $A = 2A$

$$\frac{V_0}{L_0} = \frac{20}{100} = 0.2$$

$$E_1 = \frac{V_0 \cdot l_1}{L_0}$$

$$= \frac{20}{100} \times 80 = 16V$$

$$r_1 = R \left(\frac{l_1}{L_0} - 1 \right)$$


$$= R \left(\frac{80}{100} - 1 \right) =$$

* Sensitivity of potentiometer


* To increase sensitivity of potentiometer potential gradient is decreased.

* To decrease potential gradient either length of wire is increase or current in primary circuit is decrease.
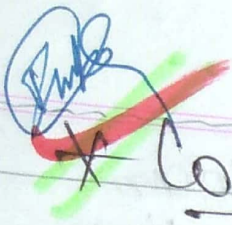
$$\uparrow \quad \quad \quad = \frac{V_0}{L_0}$$




Colour Code for Carbon Resistors

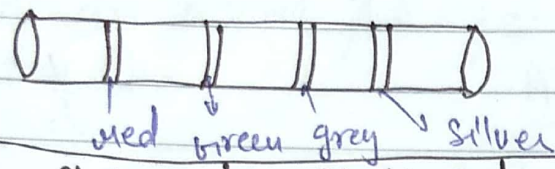

Colour	Strip A	Strip B	Strip C	Strip D Tolerance
Black	0	0	10^0	
Brown	1	1	10^1	
Red	2	2	10^2	
Orange	3	3	10^3	
Yellow	4	4	10^4	
Green	5	5	10^5	
Blue	6	6	10^6	
Violet	7	7	10^7	
Grey	8	8	10^8	
White	9	9	10^9	
Gold	-	-	10^{-1}	$\pm 5\%$
Silver	-	-	10^{-2}	$\pm 5\%$, $\pm 10\%$
No colour	-	-	-	$\pm 10\%$, $\pm 20\%$, $\pm 20\%$

B B Roy Great Britain very good watch of gold & silver

Q.1!

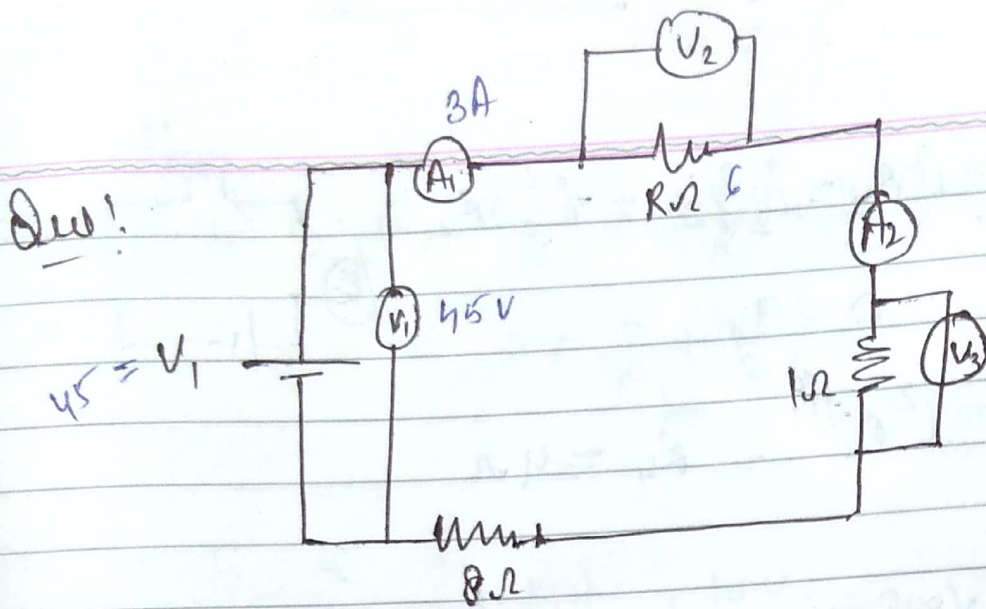

All are ideal.

$$V_1 + 45V = 27 + 3R$$

If reading of V_1 is 45V
& A_1 is 3A

find R .

Ans


$$i = \frac{45}{9 + R}$$

$$3 = \frac{45}{9 + R} = \frac{45}{9 + 3}$$

$$\begin{aligned} 27 + 3R &= 45 \\ 3R &= 45 - 27 \\ R &= \frac{18}{3} = 6\Omega \end{aligned}$$

$$R = 6\Omega$$

Q.2

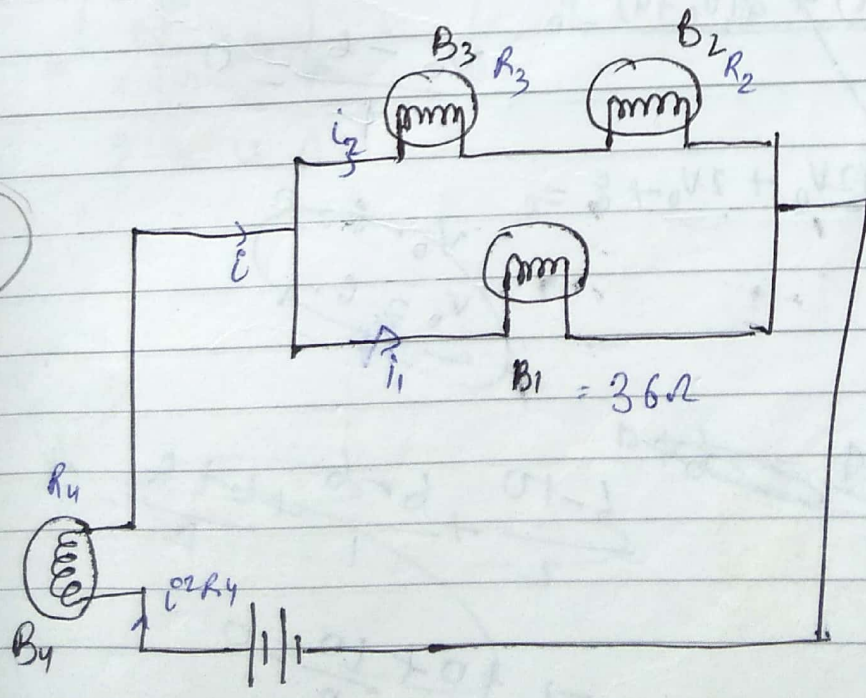


Power in each bulb is same and resistance of B_1 is 36Ω


∴ find resistance of B_2, B_3, B_4

Test syllabus upto - Voltmeter

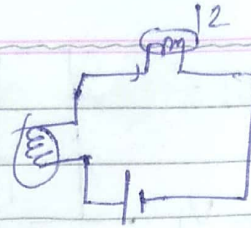B₁ $i_1^2 36 = i_2^2 R_1 = i_2^2 3 = i_2^2 R_2$
 $\frac{V^2}{9R} = \frac{2V^2}{36}$ $R = 9\Omega$



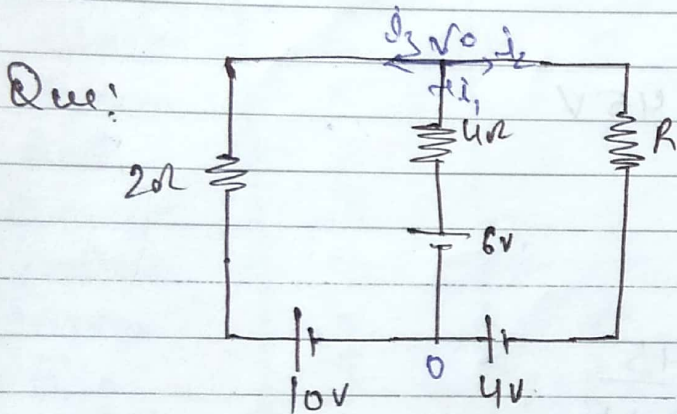$3i^2 R_1 = i^2 R_2 \Rightarrow R_1 = 4\Omega$



Find R so that current is 2A in 4Ω is 2e.u.

$\frac{V_0 - 10}{2} + \frac{V_0 - 6}{4} + \frac{V_0 + 4}{R} = 0$

$\frac{R(V_0 - 10) + 2R(V_0 - 6) + 2(V_0 + 4)}{2R} = 0$

$\frac{RV_0 - 10R + 2RV_0 - 12V_0 + 2V_0 + 8}{2R} = 0$

~~$\frac{V_0 - 10}{2} + \frac{V_0 - 6}{4} + \frac{V_0 + 4}{R} = 0$~~

~~$\frac{V_0 - 10}{2}$~~

~~$\frac{V_0 - 6}{4}$~~

~~$\frac{V_0 + 4}{R}$~~

~~$V_0 + 6$~~

$\frac{V_0 - 6}{4} = 0$

$V_0 = 2.6$

~~$\frac{V_0 + 4}{R} = 0$~~

~~$\frac{6-10}{2} + \frac{6-6}{4} + \frac{6+4}{R} = 0$~~

~~$-2 + 0 + \frac{10}{R} = 0$~~

$$V_0 - 10$$

$$\frac{V_0 - 6}{4} = 0$$

$$V_0 - 6 = 0$$

$$V_0 = 6$$

$$\frac{6+4}{R} = 0$$

$$V = IR$$

$$i_1 + i_2 + i_3 = 0, \quad \frac{V_0 - 6}{4} + \frac{V_0 + 4}{R} + \frac{V_0 - 10}{2} = 0$$

$$0 + \frac{10}{R} + \frac{-4}{2} = 0$$


$$\frac{10 - 2}{R} = \frac{2}{1}$$

$$\frac{10 - 2R}{R} = 0$$

$$10 - 2R = 0$$

$$R = \frac{10}{2} = 5$$


Sol:

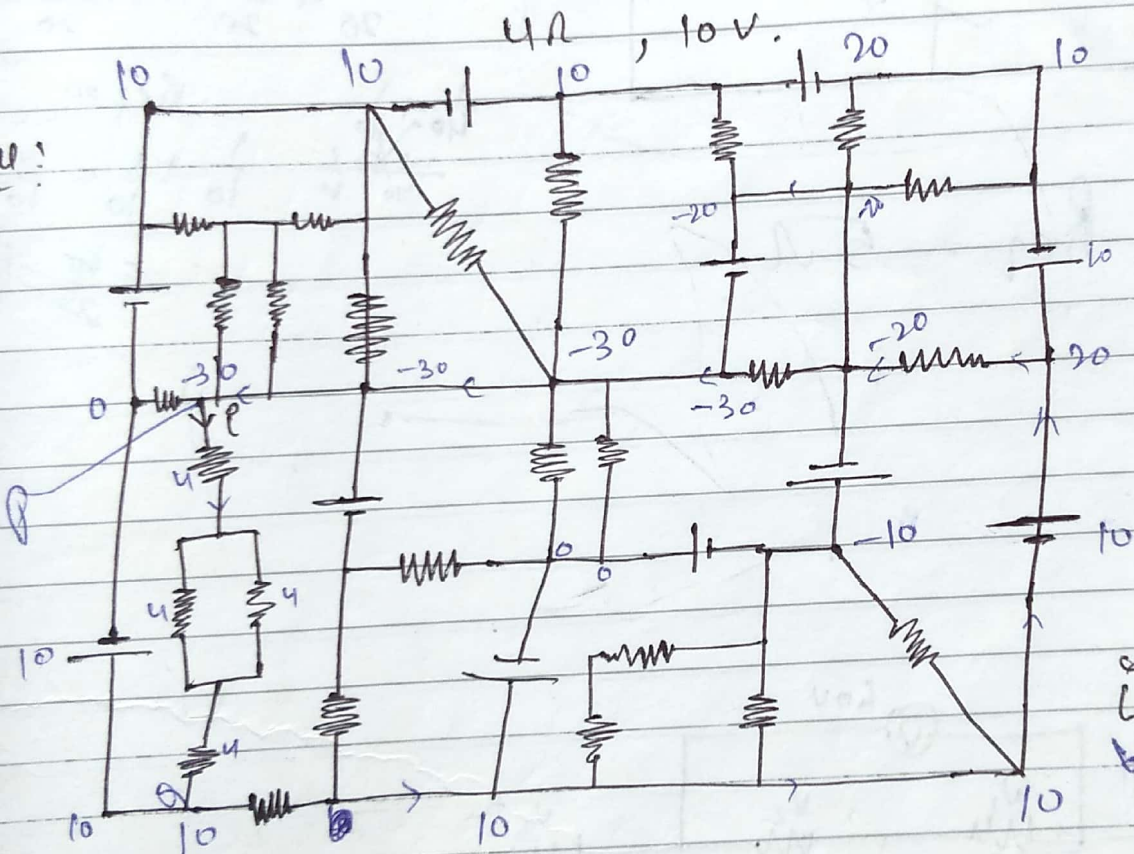

$$i = 4 \text{ A}$$

is
b/w P and Q

check
with
KVL

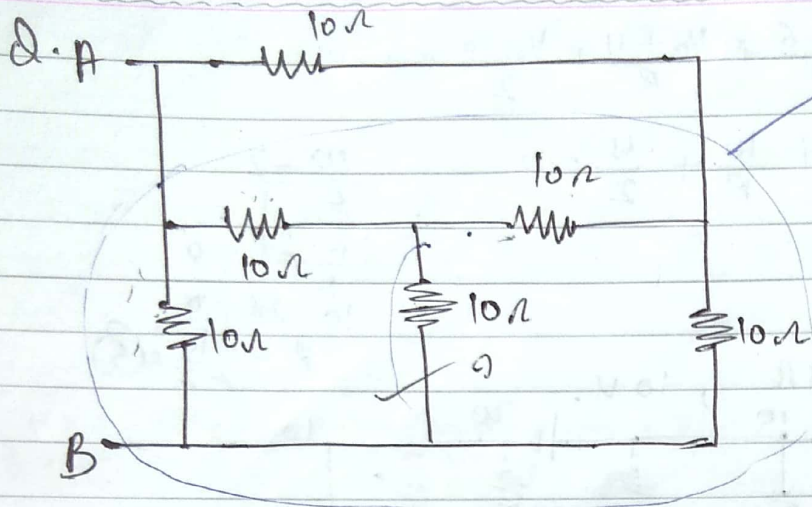

Wheatstone Bridge

Find Req.

$$\frac{1}{20} + \frac{1}{20} = \frac{2}{20} = \frac{1}{10}$$


$$\frac{1}{40} + \frac{1}{10} = \frac{1+4}{40} = \frac{5}{40} = \frac{1}{8}$$

Req =

$$\frac{1}{10} + \frac{1}{10} = \frac{2}{10} = \frac{1}{5}$$

$$= \frac{10}{2} = 5$$

Req = 5Ω

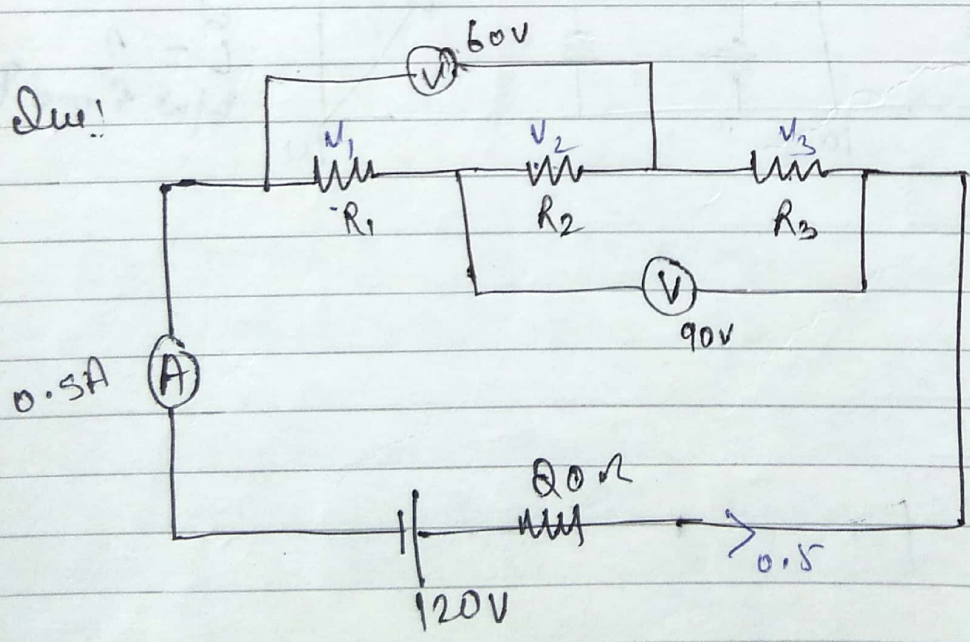

$$V_1 + V_2 = 60$$

$$V_2 + V_3 = 90$$

$$V_1 + V_2 + V_3 = 110$$

$$60 + V_3 = 110$$

$$V_3 = 50$$

J- Advanced.

$$V_1 + V_2 + V_3 = 110$$

$$V_1 = 20$$

$$V_2 = 40$$

$$V_3 = 50$$

$$R_{eq} = 80$$

~~R=80~~

$$V_1 + V_2 + V_3 = 110$$

$$V_1 = 110 - 90$$

$$V_1 = 20$$

$$\Rightarrow V_1 + V_2 = 60$$

$$V_2 = 60 - 20 = 40$$

$$40 + V_3 = 90$$

$$V_3 = 90 - 40 = 50$$

SBG STUDY