

Chapter = 1

Electricity

Assignment

Ques 1 - Is electric potential a scalar or vector quantity?

Ans - It is a scalar quantity because it has no direction.

Ques 2 Name the instrument that measure the electric current?

Ans - An Ammeter is used to measure the electric current.

Ques 3 Define the unit of electric current?

Ans - 1 Ampere = 1 Coulomb
1 Sec.

Ques 4 what is the resistance of air gap?

Ans - The Resistance of air gap is (∞) infinity.

Ques 5 How resistance change with increase of temp.?

Ans - Resistance \propto Temp.

when the electron move to get heat energy then the amount of moving electron is faster when resistance is high.

Ques 6 what constitutes the current?

Ans - It is the rate of moving electron per unit time.

Ques 7. How are Conventional & electronic current related?

Ans. In Conventional current to direction of moving current is opposite to electronic current.

Ques 8. What does an electric circuit mean?

Ans. It is a path in which electron flow from a voltage or current source.

Ques 9. What is the S.I. unit of Resistance?

Ans. Ohms (Ω).

Ques 10. What is measured by voltmeter?

Ans. It is used to measure electric potential difference b/w two points in an electric circuit.

Ques 11. Among Silver & copper which one is better conductor?

Ans. Silver is better because of its lower resistivity.

Ques 12. State the name of instrument which produces electric current?

Ans. Electrical Generator.

Ques 13. Name the physical quantity whose unit is joule Coulomb.

Ans. Electrical potential difference.

Ques 14. One ampere of current can also be represented by?

Ans. One Coulomb sec^{-1}

Ques 15. write the energy transformed into electric cell?

Ans. Chemical energy to electrical energy.

Ques 16. In Resistance box, the resistance are connected in?

Ans. It is connected in series.


Ques 17. Best conductor whose resistivity is?


Ans. Silver = 1.6×10^{-8} ohm meter.


Ques 18. Electron contained in one coulomb of electric charge is what?


Ans. 1.6×10^{-18}


Ques 19. write components of :

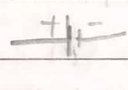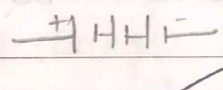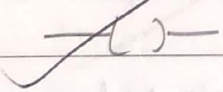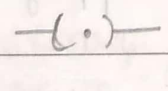
i) electric cell: 


ii) Battery: 


iii) open key: 


iv) closed key: 

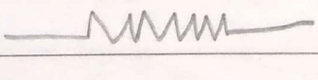
v) Resistance: 

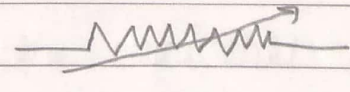
vi) Variable resistance: 

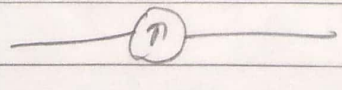vii) Galvometer: 

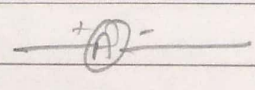viii) Ammeter: 

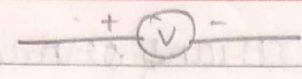ix Voltmeter 

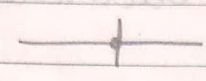x Joint wire 

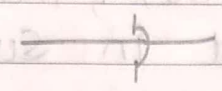xi Cross Crossing wire 

Benefits of Electricity.

- It is used in Home appliances.
- It is used in our daily working places like offices.
- we use it for AC, computer, fan, mobile etc.
- We also use it for heating.
- It is used on roads on street light.
- we use it in our school in many ways like projector, computer, AC etc.
- we use electricity in vehicle like, light, horn.
- It is also use in satellite and networking areas.
- we use electricity in factories and industries to prepare goods.
- we use it for supplying water.

Electricity = It is form of electrical energy. It is controllable & Convertent form of energy.
Ex - lightning of bulb etc.

electric charge.

* They are of three types

- (i) Electron - Negative
- (ii) Proton - Positive
- (iii) Neutron - neutral.

* Electron: It is defined as negative charge.

- (i) Magnitude of charge: $1.6 \times 10^{-19} \text{ C}$.
- (ii) Mass - ~~$1.6 \times 10^{-31} \text{ kg}$~~ $9.1 \times 10^{-31} \text{ kg}$.

* Proton: It is defined as positive charge.

- (i) Magnitude of charge: $1.6 \times 10^{-19} \text{ C}$.
- (ii) Mass - $1.673 \times 10^{-27} \text{ kg}$.

* Neutron - It is defined as neutral charge.


- (i) Magnitude of charge: 0 C .
- (ii) Mass: $1.672 \times 10^{-27} \text{ kg}$.

Property of charge:


All the charges in the universe contain two type of properties:-

1. Like
2. Unlike.

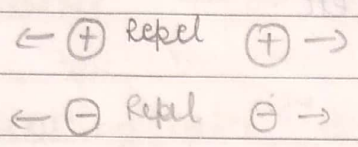i) Like - when same charges placed together, they will show repulsion property.



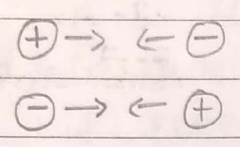(ii) unlike: when opposite charges place together they will show attraction property.




Electric Current: It is defined as the movement of electric charge flowing through a particular area per unit time.


★ Formula =
$$I = \frac{Q}{t}$$

Symbol Naming
I = Current
Q = Charge
t = time
Dimension = ~~M L T A~~
= [M L T A⁻¹ Kan]

3. S.I. Unit = "Ampere"


Measuring instrument for current :- Ammeter

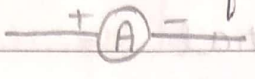* Symbol: 

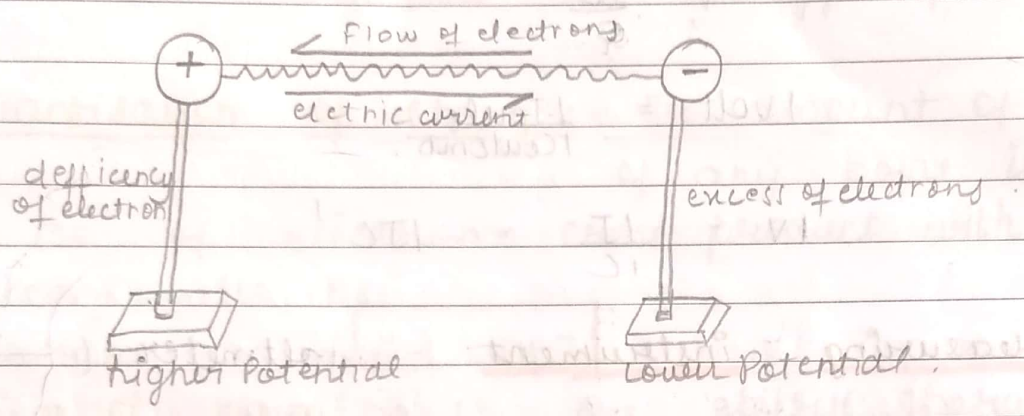

* In fig. Conventional current flows from A to B
Electronic current flows from B to A.

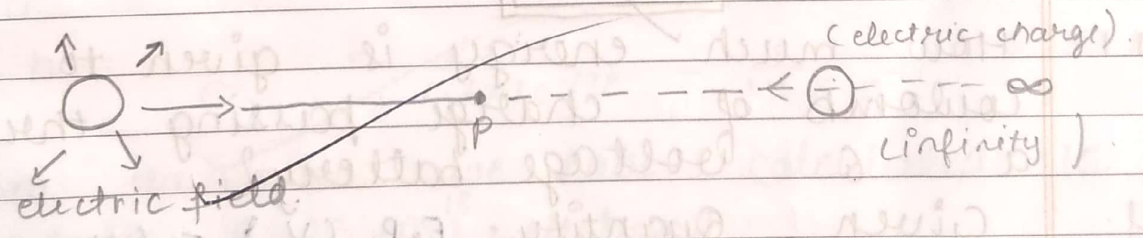Electric Potential :- The electric current of any point in electric field is defined as work done to bring a unit positive charge ∞ to a fixed point.



→ Formula of electric Potential.

Electric Potential (V) = $\frac{\text{work done}}{\text{Charge}} = \frac{W}{Q}$

$$V = \frac{W}{Q}$$

2. Symbol. 'V'
3. S.I. unit = 'Volt'

we know that

$$\text{Electric Potential} = \frac{\text{work}}{\text{Charge}}$$

$$V = \frac{W}{Q}$$

$$1 \text{ volt} = \frac{1 \text{ Joule}}{1 \text{ Coulomb}}$$

$$1 \text{ V} = \frac{1 \text{ J}}{1 \text{ C}} = 1 \text{ J C}^{-1}$$

Measuring instrument - voltmeter ($\text{---}^+\text{V}\text{---}$)

★ Electric Potential difference : The electric potential b/w two points in any electric circuit is defined as amount of work done in moving a unit charge from a point to another point

Formula

$$\frac{W_2 - W_1}{q}$$

Ques 1 How much energy is given to each Coulomb of charge passing through a 6 voltage battery?

Sol. Given Quantity: E.P. (V) = 6V
charge (Q) = 1C

Find = Energy = work

We know that

$$\text{Electric potential} = \frac{\text{work done}}{\text{charge}}$$

$$V = \frac{W}{Q}$$

$$\boxed{VQ = W}$$

$$\frac{6 \text{ V} \times 1 \text{ C}}{1 \text{ C}} = 6 \text{ J}$$

The work done on each coulomb is 6J. So, we can say that the energy require 6J.

Quantisation of charge :- The amount of charge of any point is equal to no. of electron cross product with single charge value $1e^-$

* Formula = $Q = ne^-$

Symbol naming :-
 Q = electric charge.
 n = no. of electron
 e^- = charge on electron.

S.I. Unit : $1 \text{ C} = 1 \text{ Coulomb.}$

Ques - Calculate the no. of e^- constituting 1C of charge.

Ans $1 \text{ C} = ne^-$
 $n = \frac{1 \text{ C}}{e^-} = \frac{1 \text{ C}}{1.6 \times 10^{-19} \text{ C}} = \frac{1}{1.6 \times 10^{-19}} = 6.25 \times 10^{18}$

From the above we have calculated 1C contain 6.25×10^{18} electrons.


Electric circuit :-

It is defined as the flowing of electric charge from one point to another point. we can say that charge is flowing +ve to -ve.

Types of Electric circuit :-

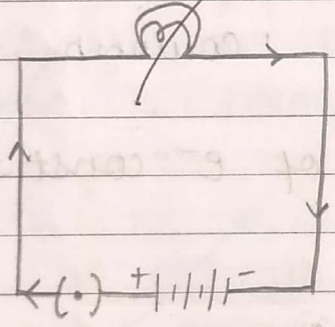
(a) Closed :-

The electric circuit in which electric charge will flow from one point to another without any breaking of electric potential difference b/w these source and instrument.




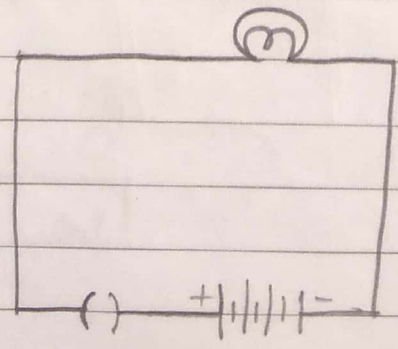(b) Open :-

Electric circuit in which electric charge will not flow from one point to another point due to breaking i.e. cutting of electric potential diff. b/w the source and instrument.




Circuit Diagram

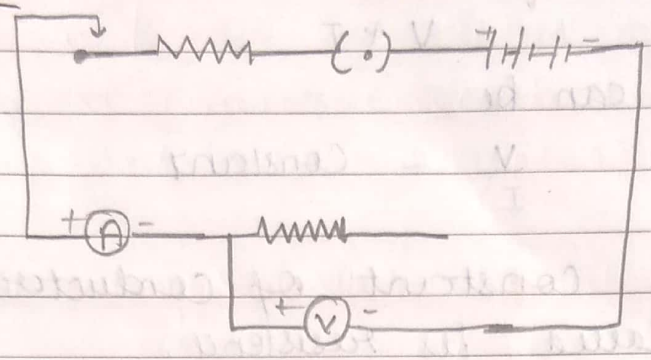

The System arrangement of electric component for measuring the electric current and electric potential with help of rheostat, resistor, voltmeter, ammeter, in electric circuit.

Ohm's Law

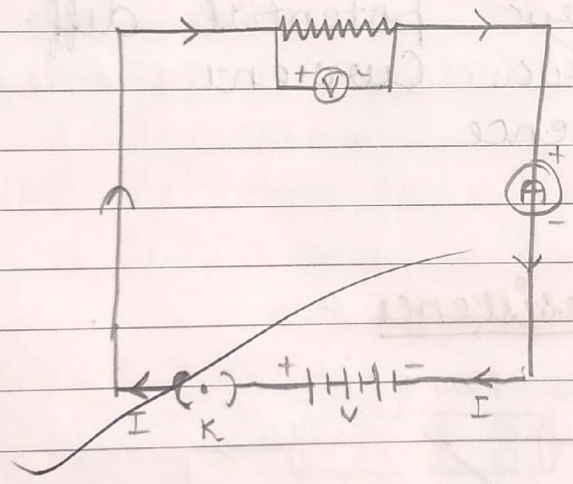

Symbol naming.

1. $\text{---} \text{+} \text{V} \text{---}$ = voltmeter
2. $\text{---} \text{+} \text{A} \text{---}$ = Ammeter
3. I = electric circuit
4. V = Voltage
5. K = Key
6. R = Resistance

from definition \Rightarrow
 $V \propto I$

This can be.

$$\frac{V}{I} = \text{Constant}$$

The constant of conductor at a given temp. is called its resistance.

$$\frac{V}{I} = R$$

$$V = IR$$

Hence, this is ohm's law.


Symbol Naming

V = Electric potential diff.

I = Electric Current

R = Resistance

Electric Resistance :-

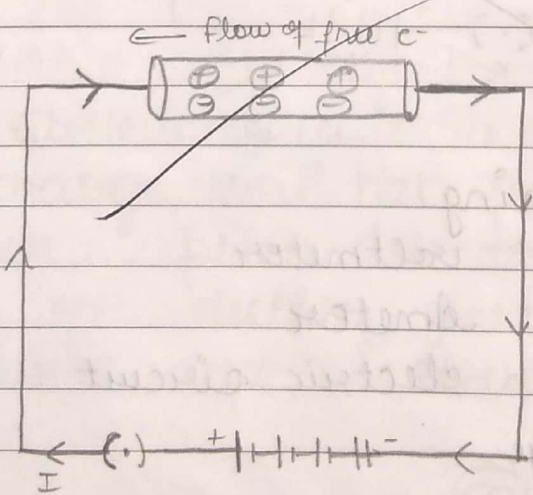

Conventional current flow

⇒ Property of a conductor by virtue of which it opposes the flow of electric current through it.

* Formula

$$R = \frac{V}{I}$$

Resistance = $\frac{\text{Voltage}}{\text{Electric current}}$

formula

$$R = \frac{\rho L}{A}$$

→ Symbol Naming -

R = Resistivity.

L = Length

A = Area

S.I Unit = Ω (ohm)

→ Symbol = Ω

$$R = \frac{V}{I}$$

$$1 \Omega = \frac{1V}{1A}$$

Quantity = It is scalar quantity.

Ques 1. what are the relation b/w current and potential

Ans. $V = IR$

$V \propto I$

The current is directly proportional to potential

- 1. If the potential diff. across the end of a conductor is double, the current flowing through it, it also get doubled
- 2. If the potential diff. across the end of a conductor is halved, the current flowing through it, also get halved (half).

Ques 2. What is relation of current and Resistance?

Sol. Current is inversely proportional to Resistance

$I \propto \frac{1}{R}$

- 1. If the current is flowing through the end of conductor is halved, then the Resistance get doubled
- 2. If the Resistance is halved, then current get doubled.

Ques 3. what are the factor which affect current?

Ans: Resistance and Potential diff. are the factor affect current

Ques 4. Define 1 ohm?

Ans. 1 ohm of circuit is defined as the potential diff. of 1 volt is applied to its end, a current of 1 ampere flows through it.

Ques 1: A electric meter draws a current of 10 when connected to 220 volt. Calculate the Resistance

Ans. Given :-

Current (I) = 10 amp.

Voltage (V) = 220 volt.

Find -

Resistance (R) = $\frac{V}{I}$

We know

$$R = \frac{V}{I}$$

$$R = \frac{220}{10}$$

$$R = 22 \text{ ohm}$$

Ques 2 what are the high and low resistance value as well as current?

Ans. Current:

$$1 \text{ Ka} = 10^3 \text{ A}$$

$$1 \text{ MA} = 10^6 \text{ A}$$

$$1 \text{ mA} = 10^{-3} \text{ A}$$

$$1 \text{ uA} = 10^{-6} \text{ A}$$

Resistance

$$1 \text{ K } \Omega = 10^3 \Omega$$

$$1 \text{ M } \Omega = 10^6 \Omega$$


$$1 \text{ m } \Omega = 10^{-3} \Omega$$

$$1 \text{ u } \Omega = 10^{-6} \Omega$$

Ques 3: The value of current (I) flowing in given resistor for a corresponding value potential difference the across the resistor given below.

I (A)	V (volt)
0.5	1.6
1.0	3.4
2.0	6.7
3.0	10.2
4.0	13.2

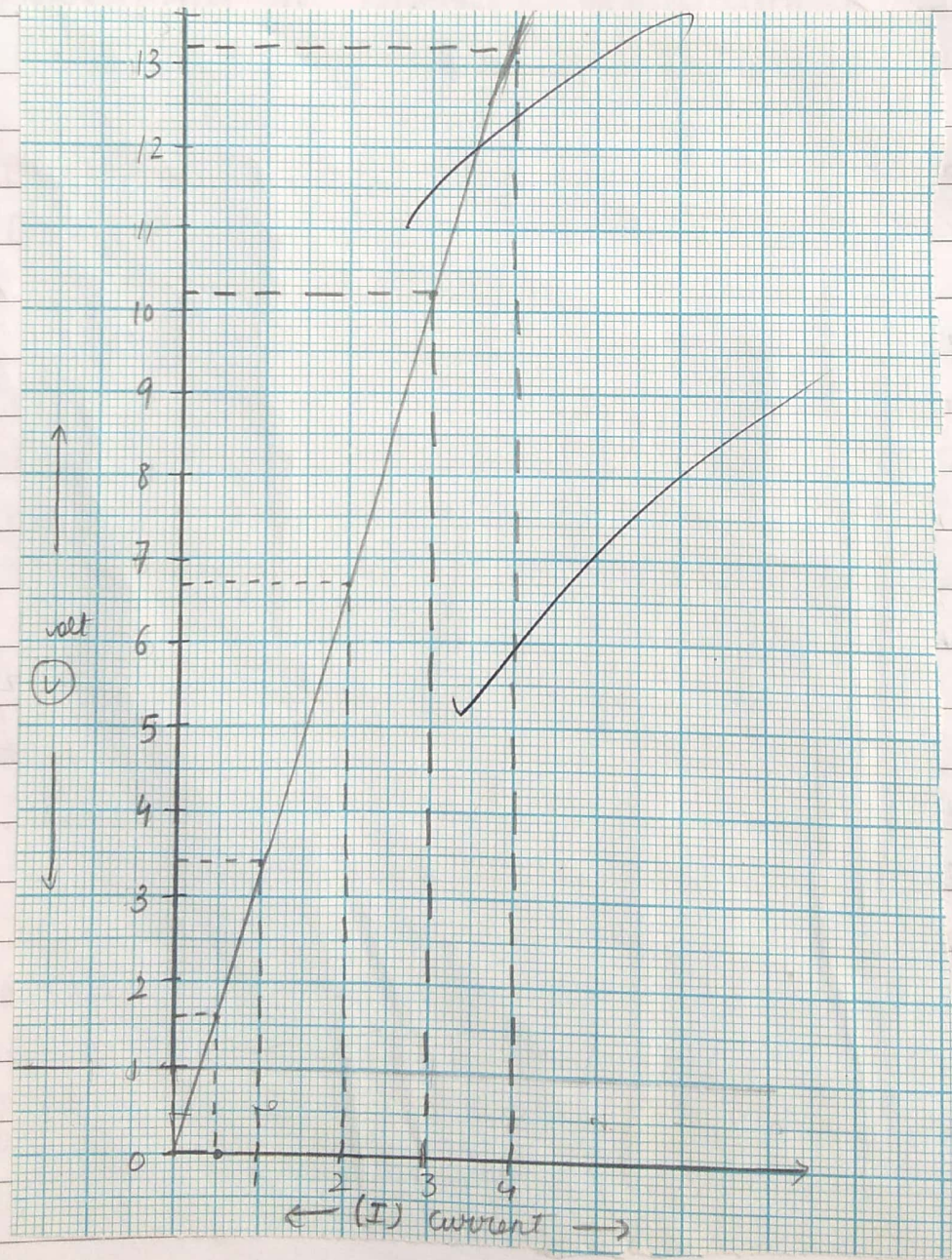* Plot the graph b/w V and I calculate the resistance.




→ Formula to Calculate the resistance from Graph.

$$R = \frac{\Delta V}{\Delta I} = \frac{V_2 - V_1}{I_2 - I_1} \left[\text{slope } \frac{AB}{BC} = \frac{BC}{AC} \right]$$

$$R = \frac{13.2 - 6.2}{4.2}$$
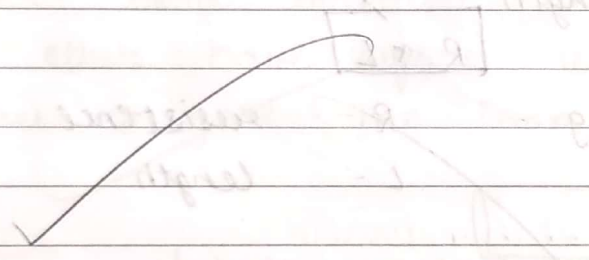
$$R = \frac{13}{2 \times 10^{-2}} = 43.22 \Omega$$



The resistance of a conductor is directly proportional to the length of the conductor and inversely proportional to the area of cross-section of the conductor.

$$R \propto \frac{l}{A}$$

Factor affecting Resistance of Conductor.



The electric resistance of conductor depends upon following factors:

- Length of conductor
- Temp. of conductor
- Nature of Material of conductor.
- Area of cross section of conductor.

Effect of Length on Resist
Resistance of conductor is directly proportional to its length

$$R \propto L$$

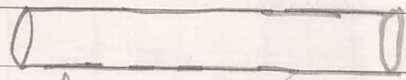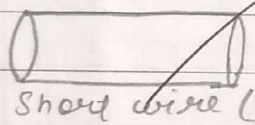* Symbol naming - R - resistance
L - length




□ If the length of conductor is doubled, its resistance also get doubled.

□ If the length of conductor is halved, its resistance also gets halved.

Effect of Cross-section of resistance on a conductor.

The resistance of conductor is inversely proportional to area of cross section.

$$R \propto \frac{1}{A}$$

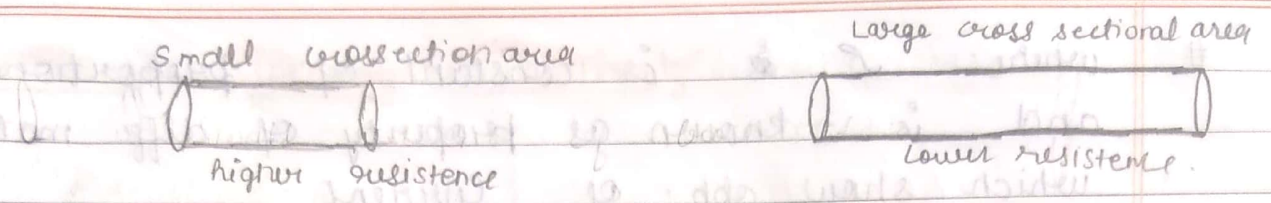

A thick wire has lesser resistance than thin wire.

Effect of temperature on the resistance of a conductor. The resistance of all pure metals increases with increase in temp. and decreases on lowering the temp.

★ Effect of nature of material on the resistance of a conductor: - some material have low resistance, whereas other have higher resistance. Ex. Silver is good than Iron.

Resistivity:

= As from the ohm's Law we study R and dependency of ρ on diff. cases.

$$R = \rho \frac{l}{A}$$

from the factor (1).
 \Rightarrow dependency of Length.
 $R \propto l$ — (1)

from 2nd factor
 $R \propto \frac{1}{A}$ — (2)

Combine (1) and (2)
 we get $R \propto \frac{l}{A}$

$$R = \rho \frac{l}{A}$$

where ρ is constant of proportional and is known as property of diff. material which show app. of current.

Resistivity.

Defination: It is a measure of resisting power of a specified material to the flow of an electric current.

Unit of Resistivity.

* Formula -

$$\rho = \frac{RA}{L}$$

S.I. Unit - "Ohm meter"

Dimension $[M^1 L^3 T^{-3} A^{-2}]$

Factor Unit of resistivity (ρ) = $\frac{\text{ohm} \times (\text{metre})^2}{\text{metre}}$

$$= \frac{\Omega \times m^2}{m}$$

$$= \Omega m$$

Factor affecting Resistivity

$R \propto L \propto \frac{1}{A}$

It does not depend upon length and area of material

2. Nature of material
3. Temp. of material.

Electrical resistivity of some substances at 20°C

★ Category	Material	Resistivity ($\Omega \cdot m$)
Conductors	Metals:	
	Silver	1.60×10^{-8}
	Copper	1.62×10^{-8}
	Aluminium	2.63×10^{-8}
	Tungsten	5.20×10^{-8}
	Nickel	6.84×10^{-8}
	Iron	10.0×10^{-8}
	Chromium	12.9×10^{-8}
	Mercury	94.0×10^{-8}
	Manganese	100×10^{-6}
Semi conductor	Alloys Nichrome	
	Germanium	0.6
	Silicon	2300
Insulators	Glass	$10^{10} - 10^{14}$
	Hard glass	$10^{13} - 10^{16}$
	Ebonite	$10^{15} - 10^{17}$
	Diamond	$10^{12} - 10^{13}$
	Paper (dry)	10^{12}

Difference between Resistance and Resistivity

Parameter	Resistance	Resistivity
Defination	The property of material due to which it opposes the flow of current through it is called resistance	Restivity of material is resistance offered by 1m L of wire of material having an area of cross section of $1m^2$.
Formula	The resistance of conductor depends on its length and thickness	The resistivity of material does not depend on its length or thickness and is the characteristic of given material
Formula dependancy	$R = \frac{V}{I}$ (Potential Diff / Current)	$\rho = \frac{R \times A}{L}$ (Resistance \times Cross Section Area / length of material)
S.I unit	ohm (Ω)	ohm metre ($\Omega\text{-m}$)

8pm
9/5/18
9/5/18

12/05/17

Conductor - those substance which have very low electrical resistivity are called conductors.
ex - Silver the best conductor amongst metals.

Resistors: These substances which have comparatively higher electrical resistivity are called resistors.

Insulators: Those substance which have infinitely high resistivity are called Insulators.

Ques 1
sol. what will be the resistance of metal wire of length 2m and area of crosssection $1.25 \times 10^{-6} \text{ m}^2$, if the resistivity of metal is $1.6 \times 10^{-8} \text{ } \Omega\text{-m}$?

sol $R = \frac{\rho \times l}{A}$

Given Quantity

Here, Resistivity (ρ) = ?

Area of crosssection (A) = $1.25 \times 10^{-6} \text{ } \Omega\text{-m}$
length (l) = 2m.

Resistivity of metal (ρ) = $1.6 \times 10^{-8} \text{ } \Omega\text{-m}$

=> Putting the value

$$1.6 \times 10^{-8} \text{ } \Omega\text{-m} = \frac{R \times 1.25 \times 10^{-6} \text{ m}^2}{2 \text{ m}}$$

$$R = \frac{2 \text{ m} \times 1.6 \times 10^{-8} \text{ } \Omega\text{-m}}{1.25 \times 10^{-6} \text{ m}^2}$$

$$R = \frac{2 \times 1.6 \times 10^{-8+6} \text{ } \Omega}{1.25}$$

$$R = \frac{2 \times 1.6 \times 10^{-2} \text{ } \Omega}{1.25}$$

$$R = 2.56 \times 10^{-2} \text{ } \Omega$$

=> The resistance of metal wire is $2.56 \times 10^{-2} \text{ } \Omega$

Ques 2 The electrical resistivities of iron and mercury are $10.0 \times 10^{-8} \Omega\text{-m}$ and $94.0 \times 10^{-8} \Omega\text{-m}$ respectively which is better conductor.

sol. Iron is a better conductor than mercury because it has a lower resistivity than mercury. We know lower the resistivity, better is conductor.

Ques 3 What are coils of electric toasters and electric irons made of an alloy rather than a pure metal?

Ans. The coils of electric toasters and electric irons are made of an alloy rather than a pure metal's

a. the resistivity of an alloy is higher than that of its constituent pure metals

b. Alloy do not oxidise (burn) readily at high temperature.


~~Ans.~~
seen
14/5/18

Combination of Grouping of Resistors
The resistors may be connected in two ways.

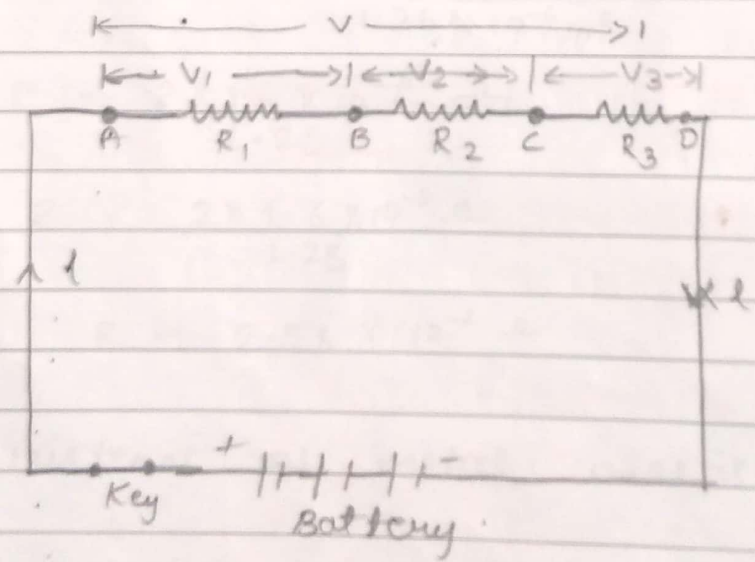(a) Series combination of resistors.
Two or more resistors are said to be connected in series if they are connected end to end consecutively in electric circuit.

the current I passes through each resistor is same.

each resistor has different potential diff. across its ends. But the sum of potential diff. across all resistance is equal to voltage of the battery.



Symbol Naming.
 V = Potential difference
 R = Resistance
 I = Current

Equivalent resistance of three resistors connected in series

Consider three resistors of R_1 , R_2 and R_3 connected in series. Let I be flowing current through each resistor and V be the potential diff across the series combination. If V_1 , V_2 and V_3 potential diff across resistors R_1 , R_2 , R_3 .

$V = V_1 + V_2 + V_3$ --- (1)

By \rightarrow Law $V_1 = IR_1$, $V_2 = IR_2$, $V_3 = IR_3$

\Rightarrow Current flowing through all resistors is same.

\therefore Eq (1) becomes

$$V = IR_1 + IR_2 + IR_3$$

or $V = I(R_1 + R_2 + R_3)$ --- (2)

If R_s be effective or equivalent resistance of series


$$V = IR_s$$

From eq (2) and (3) we get

$$IR_s = I(R_1 + R_2 + R_3)$$

$$\boxed{R_s = R_1 + R_2 + R_3}$$

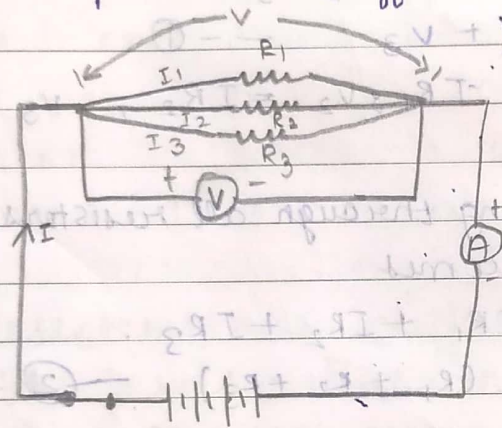Parallel combination of resistors.
Two or more resistors are said to be connected in parallel if one end of a resistor is connected to one end of other resistor and the second end of the first resistor is connected to second end of other resistor, such that potential diff. across resistor is same.



- * All the resistors have the same potential across them.
- * diff. amount of I flows through each resistor. But sum of I flowing through all resistances is equal to total current flowing in circuit.

Consider three resistors of resistance R_1, R_2, R_3 connected in parallel.
 \Rightarrow let v be potential diff across each resistor.
 The current I drawn from cell divides into 3 parts (I_1, I_2, I_3) at junction Point A. Let I_1, I_2, I_3 flow through resistors R_1, R_2, R_3

$$I = I_1 + I_2 + I_3$$

Since potential diff b/w 2 end A & B is V , by Ohm's Law.

Current in R_1 is $I_1 = \frac{V}{R_1}$

" in R_2 is $I_2 = \frac{V}{R_2}$

" in R_3 is $I_3 = \frac{V}{R_3}$

Now, $I = I_1 + I_2 + I_3$

~~$I = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$ — (1)~~

In equivalent resistance of combination b/w points A and B is R_p then,

~~$I = \frac{V}{R_p}$ — (2)~~

from eq (1) and (2) we get,

~~$\frac{V}{R_p} = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$~~

~~$\frac{V}{R_p} = V \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$~~

~~$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$~~

Seen
16/5/18

Assignment

Ques 1:- Resistors of 5Ω , 10Ω , 15Ω and 20Ω are connected in series. Calculate the total resistance of the circuit.

Sol. :- Given Quantity
Resistance $R_1 = 5\Omega$, 10Ω , 15Ω , 20Ω

$R_2 = 10\Omega$

$R_3 = 15\Omega$

$R_4 = 20\Omega$

find :- Total resistance (R_T) = ?

As we know.

$$R_T = R_1 + R_2 + R_3 + R_4$$

$$R_T = 5\Omega + 10\Omega + 15\Omega + 20\Omega$$

$$R_T = 50\Omega \text{ Ans}$$

Ques 2:- Three resistors of 2Ω , 3Ω , and 15Ω are connected in parallel. Calculate the total resistance of the circuit.

Sol. :- Given Quantity =

Resistance (R) = 2Ω , 3Ω , 15Ω

find :- Total Resistance (R) = ?

As we know:

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{R_p} = \frac{1}{2\Omega} + \frac{1}{3\Omega} + \frac{1}{15\Omega}$$

$$= \frac{15 + 10 + 2}{30} = \frac{27}{30} = 1.17\Omega \text{ Ans}$$

??

Ques 1 State the law of combination of resistors in series.

Ans. Page no 27 on N/B.

Ques 2 Why is the series arrangement not used for domestic circuits.

Ans Page no 27.

Ques 3 Air Conditioners, water heaters, etc. do not work properly in series circuit. Give reasons.

Ans

Ques 4.

Sol 4.

~~$$V = IR$$
$$V = I_1 R_1 + I_2 R_2 + I_3 R_3$$
$$V = I(R_1 + R_2 + R_3)$$
$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$~~

??

Ques 5 State the law of combination of resistors in Parallel.


Sol 5. On Page no. 28 in N/B.

Ques 6 what are the characteristics of the combination of resistors in Parallel?


- Sol 1.
1. All other appliances keep working normally
 2. Each electrical appliance has its independent switch, so it can be operated independently.
 3. Each electrical appliance gets same voltage (220V)

Ques 7 Distinguish b/w the resistors connected in series and Parallel.

Ans Resistors in Series

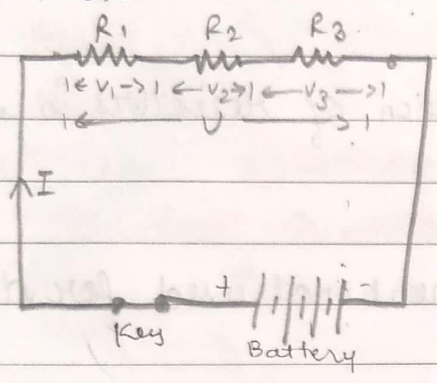

Parallel

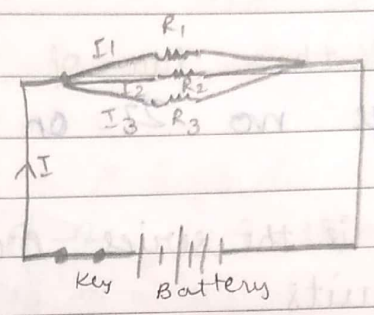


Symbol Naming.
 V = Potential diff.
 I = ~~Const~~ Electric Current
 R = Resistance.

~~Symbol Naming.
 V = Potential diff.
 I = Current
 R = Resistance.~~

Formula
 $V = V_1 + V_2 + V_3$
 $I = \text{Constant } (I_1 = I_2 = I_3 = I)$
 $R_s = R_1 + R_2 + R_3$

~~Formula
 $V = \text{Constant } (V_1 = V_2 = V_3 = V)$
 $I = I_1 + I_2 + I_3$
 $\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$~~

Ques 9.
Sol 9.

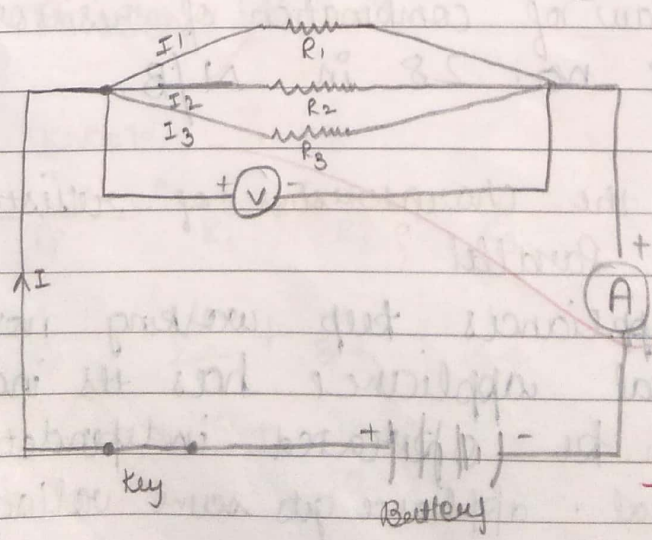

Ques 10

Sol 10 Given Quantity!

$$\text{Resistance (R)} = 8\Omega, 10\Omega, 5\Omega$$

Find: Resistance (R_S) _____?

As we know:

$$R_S = R_1 + R_2 + R_3$$

$$R_S = 8\Omega + 10\Omega + 5\Omega$$

$$R_S = 23\Omega \text{ Ans}$$

Ques 11

Sol 11 Given Quantity!

Four resistor = $5\Omega, 10\Omega, 15\Omega$ or 20Ω

find: Total Resistance (R_p) _____?

As we know:

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}$$


$$\frac{1}{R_p} = \frac{1}{5\Omega} + \frac{1}{10\Omega} + \frac{1}{15\Omega} + \frac{1}{20\Omega}$$

$$\frac{1}{R_p} = \frac{12 + 6 + 4 + 3}{30} = \frac{25}{30} = \frac{5}{6} \Rightarrow \frac{1}{R_p} = \frac{1}{2.4}$$

$$R_p = 2.4\Omega \text{ Ans}$$

22/05/18

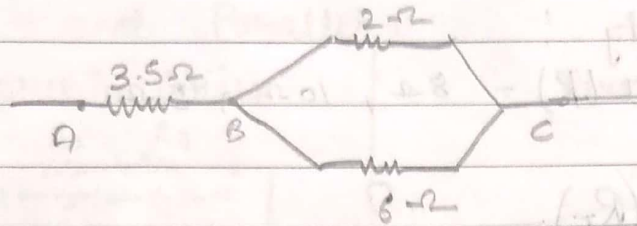Ques 13 Calculate the total resistance of circuit:-
Sol 13.



Sol Case I - Given Quantity

$$R_1 = 2\Omega, R_2 = 6\Omega$$

To find R_p .

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{R_p} = \frac{1}{2} + \frac{1}{6}$$

$$\frac{1}{R_p} = \frac{3+1}{6} = \frac{4}{6}$$


$$R_p = \frac{3}{2}$$

Case II: Given Quantity $R_1 = 3.5\Omega, R_2 = \frac{7}{2}, R_3 = \frac{3}{2}$

$$R_s = R_1 + R_2$$

$$= \frac{7}{2} + \frac{3}{2} = \frac{10}{2} = 5\Omega$$

B

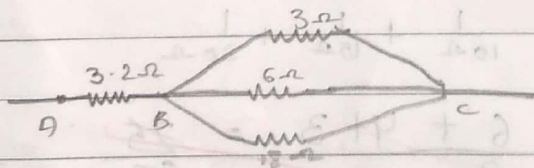

Sol Case I - Given Quantity = $R_1 = 3\Omega, R_2 = 6\Omega, R_3 = 9\Omega$

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{R_p} = \frac{1}{3} + \frac{1}{6} + \frac{1}{9}$$

$$\frac{1}{R_p} = \frac{6+3+1}{18} = \frac{10}{18} = \frac{5}{9}$$

Case II $R_s = R_1 + R_2$
 $= \frac{16}{5} + \frac{9}{5} = \frac{25}{5} = \boxed{5\Omega} \underline{A_1}$

Ques 14 Four resistor are connected in series such that their total resistance is 50Ω . Three resistor of 5Ω , 10Ω , 15Ω - find the fourth.


Sol Given Quantity. $R_s = 50\Omega$,
 $R_1 = 5\Omega$, $R_2 = 10\Omega$, $R_3 = 15\Omega$
 $R_4 = ?$

$R_s = R_1 + R_2 + R_3 + R_4$
 $50 = 5 + 10 + 15 + R_4$
 $50 = 30 + R_4$
 $50 - 30 = R_4$
 $\boxed{20 = R_4}$

Ques 15 Given Quantity $V = 5$, $R = 10$.

Sol $V = IR$
 $I = \frac{V}{R} = \frac{5}{10} = \boxed{0.4A}$

Ques 16:
 (i)

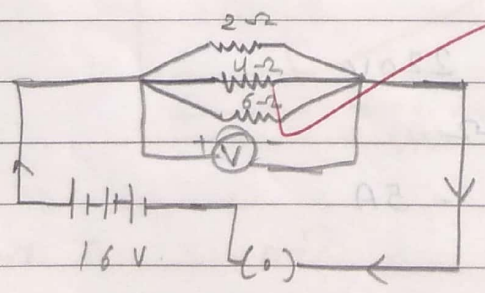

(a) Total resistance of circuit in each resistor

Sol

$$V = IR, \quad I = \frac{V}{R}$$

$$\text{i) } I_1 = \frac{V}{R} = \frac{16}{2} = \boxed{8A}$$

$$\text{ii) } I = \frac{V}{R} = \frac{16}{4} = \boxed{4A}$$

$$\text{iii) } I = \frac{V}{R} = \frac{16}{8} = \boxed{2A}$$

(b) Total current = $8A + 4 + 2 = \boxed{14A}$

(c) Given Quantity

$$R_1 = 2\Omega, \quad R_2 = 4\Omega, \quad R_3 = 8\Omega$$

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{2} + \frac{1}{4} + \frac{1}{8}$$

$$\frac{1}{R_p} = \frac{4+2+1}{8} = \frac{7}{8}$$

$$R_p = \frac{8}{7} = 1.14\Omega$$

Ques 17

Sol: (a) Separately = Volt = 220V

$$R = 44\Omega$$

$$I = \frac{V}{R} = \frac{220}{44} = 5A$$

(b) Series, Volt = 220V.

$$R = 44 + 44 = 88\Omega$$

$$I = \frac{V}{R} = \frac{220}{88} = \frac{5}{2} = 2.5A$$

(C) Parallel = volt = 220V.

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{R_p} = \frac{1}{44} + \frac{1}{44} = \frac{2}{44}$$

$$R_p = 22.$$

$$I = \frac{V}{R} = \frac{220}{22} = 10A.$$

Ques 18

Sol: Given Quantity = $R_1 = 6\Omega$, $R_2 = 8\Omega$, $R_3 = 12\Omega$,
 $R_4 = 24\Omega$.

Highest Resistance.

$$R_s = R_1 + R_2 + R_3 + R_4.$$

$$R_s = 6 + 8 + 12 + 24$$

$$R_s = 50\Omega.$$

Lowest Resistance.


$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{6} + \frac{1}{8} + \frac{1}{12} + \frac{1}{24}.$$

$$\frac{1}{R_p} = \frac{4 + 3 + 2 + 1}{24} = \frac{10}{24}$$

$$R_p = \frac{24}{10} = \boxed{2.4\Omega} \text{ Ans}$$

Ques 19

Sol:

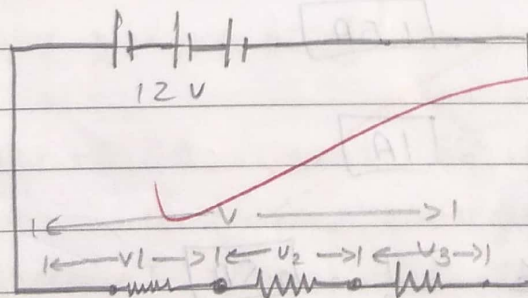

Sol (a) Find I — A?

$$R_s = 6 + 10 + 8 = 24\Omega$$

$$V = 12V$$

$$I = \frac{V}{R} = \frac{12}{24} = \boxed{0.5A}$$

$$\text{b (i) } V_1 = I_1 R_1$$

$$= 0.5 \times 6 = \boxed{3V}$$

$$\text{ii } V_2 = I_2 \times R_2$$

$$= 0.5 \times 8$$

$$= \boxed{4V}$$


$$\text{iii } V_3 = I_3 \times R_3$$

$$= 0.5 \times 10$$

$$= \boxed{5V}$$

Ques 20

Sol:

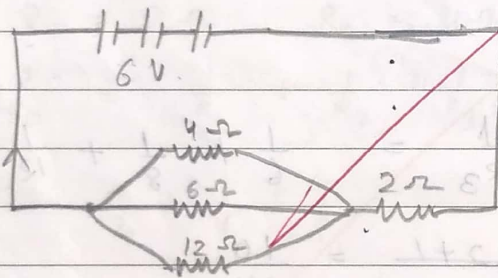

$$\text{Sol: (b) } R_1 = 4\text{-}\Omega, R_2 = 6\text{-}\Omega, 12\text{-}\Omega$$

$$V = 6\text{ V}$$

$$I_1 = \frac{V_1}{R_1} = \frac{6}{4} = \boxed{1.5A}$$

$$I_2 = \frac{V_2}{R_2} = \frac{6}{8} = \boxed{1A}$$

$$I_3 = \frac{V_3}{R_3} = \frac{6}{12} = \frac{1}{2} = \boxed{0.5A}$$

20/05/18

Heating effect of electric current


Due to energy conservation, electrical energy is converted into heat energy which give heat and light. This is called heating effect of electric current.

OR

A current flow through a conductor, the free electrons lose energy which is converted into heat.

Heat Produced in conductor by electric current

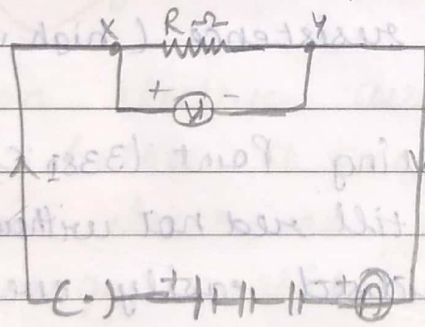consider a conductor XY of resistance $R \Omega$ let a potential diff. (V) be applied across the ends of XY.



$$Q = I \times t \quad \text{--- (1)}$$

when an electric charge Q moves against V , the amount of work done (w)

$$W = Q \times V \quad \text{--- (2)}$$

Ohm's law

$$R = \frac{V}{I}$$

$$V = IR \quad \text{--- (3)}$$

Substituting value of eq (1) and 3 in eq (2)

$$W = Q \times T$$

$$W = I \times t \times I \times t$$

$$W = I^2 \times t \times R$$

Work done = energy

$$W = E = I^2 \times R \times t$$

H is also form of energy

$$H = I^2 R t$$

It is known as Joule's law of heating

Electric Bulb

A electric bulb consist of a filament made tungsten wire. Tungsten is used because it has a large value of resistivity and a high Melting Point.

→ Because:

1. It has a very high resistance (high value of resistivity).
2. It has a high Melting Point (3380°C), so it can be heated till red hot without melting.
3. It does not get oxidised easily even at temp. (2500°C).
4. Its thermal expansion is not very large. So on heating, it does not get loose and cause any insulation Problem.

Bulb is filled with Argon or Nitrogen to prevent oxidation and evaporation of the filament and hence prolong the life of the filament of an electric bulb.

Electric Fuse :-

is a safety device constituting of piece of thin wire of a material (generally an alloy of tin and copper) having a low melting point and high resistance which melts and breaks the circuit of current exceeds a safe value, hence preventing the electrical appliances in circuit from getting damaged.

⇒ Rating of fuse :-

The maximum current which can flow through a fuse without melting it, is called its fuse rating.

⇒

Quiz

Ques 1: when an electric current is passed through a electric bulb, it becomes warm when touched.

Ans because electrical energy converted into heat energy, which make it warm.

Ques 2 what is meant by heating effect of current?

Ans when electrical energy converted into heat and light to produce it heat and light

Ques 3: what is cause of heating effect of electric current?


Ans As current flows through a conductor the free electrons loose energy which is converted into heat.

Heating effect of electric current :-
Due to the energy conservation the electric energy converted into the heat energy is called Heating effect

OR
As current flow through a conductor, the free electrons lose energy which is converted into heat

Electric bulb

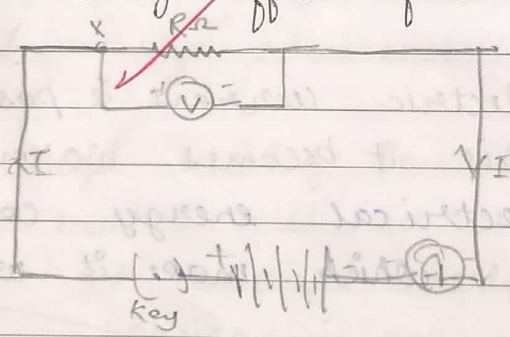Cause of heating effect of electric current :-



Heat produced in a conductor by electric current. Consider a conductor XY of resistance R ohms. If a potential diff. (in volts) be applied across the ends of XY.

$$Q = IXt \quad \text{--- (1)}$$

When an electric charge Q move against V, the amount of work done (W)

$$W = Q \times V \quad \text{--- (2)}$$

#

$$W = Q \times t$$

$$W = I \times t \times I \times R$$

$$W = I^2 \times t \times R$$

Work done = energy.

$$W = E = E^2 \times R \times t$$

H is also form of energy

$$H = I^2 R t$$

#

It is known as Joule's Law of Heating.

#

Electric Bulb.

An electric bulb consist of a filament made of tungsten wire, Tungsten is used because it has a large value of resistivity and a high melting point.

→

Bulb is filled with Argon or Nitrogen to prevent oxidation and evaporation of the filament and hence prolong the life of the filament of an electric bulb

#

Electric fuse:

is a safety device constituting of a piece of thin wire of a material having a low melting point and high resistance which melts and breaks the circuit of the current exceeds a safe values, hence preventing the electrical appliances in circuit from getting damaged.

Electric Power

electric power is defined as the rate of doing electric work per unit time. Electric Power (P) = $\frac{\text{Electrical work done}}{\text{Time}}$.

$$P = \frac{E}{t}$$

$$P = \frac{I^2 R t}{t} = P = \frac{V I t}{t}$$

$$P = V \times I$$

Form of I and R

we know $= V = IR$

and $P = V \times I$ — (1)

put value of V in eq (1)

$$P = IR \times I$$

$$P = I^2 R$$

Form of V and R

$$P = V \times I \text{ — (1)}$$

Ohms Law = $I = \frac{V}{R}$

Put the value of I in eq (1)

$$P = \frac{V \times V}{R}$$

$$P = \frac{V^2}{R}$$

Unit of Electric power.

$$P = V \times I$$

then,

$$1P = 1V \times 1A$$

$$1P = 1 \text{ watt (1w)}$$

1 Watt = when 1 Ampere current flows through an electrical circuit when a potential diff. of 1 volt is applied.

$$1 \text{ Kilowatt} = 1 \text{ kW} = 1000 \text{ W}$$

$$1 \text{ Mega watt (MW)} = 10^6 \text{ W}$$

$$1 \text{ Micro watt } \mu\text{W} = 10^{-6} \text{ W}$$

$$1 \text{ mili watt} = 10^{-3} \text{ W}$$

$$1 \text{ giga watt } 1 \text{ gw} = 10^9 \text{ W}$$

$$1 \text{ nano watt } 1 \text{ nw} = 10^{-9} \text{ W}$$

In Series

$$R_T = R_1 + R_2$$

$$R_T = 10\Omega + 10\Omega$$

$$R_T = 20\Omega$$

In Parallel

$$\frac{1}{R_P} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R_P} = \frac{1}{20} + \frac{1}{10}$$

$$= \frac{1+2}{20}$$

$$\frac{1}{R_P} \times \frac{3}{3} = \frac{3}{20}$$

$$3R_P = 20$$

$$R_P = \frac{20}{3}$$

~~Incomplete
sub~~

(C) Short type - II Question.

Ques: Calculate the Resistance of 5m length wire of cross-section 0.01mm^2 and Resistivity 50×10^{-8} ohmmeter.

sol. Given Quantity-

$$\text{Length } (L) = 5\text{m}$$

$$\text{Area of cross-section } (A) = 0.01\text{mm}^2$$

$$\text{Resistivity } (\rho) = 50 \times 10^{-8} \Omega\text{m}$$

find Resistance Ω ?

As we know.

$$R = \frac{\rho L}{A}$$

Symbol Naming.

R = Resistance.

ρ = Resistivity.

L = Length.

A = Area.


Putting the values in above formula.

$$R = \frac{50 \times 10^{-8} \Omega\text{m} \times 5\text{m}}{0.01\text{m}^2 \times 10 \times 10^{-6}}$$

$$R = 25 \times 10^{-2} \Omega$$

Resistance of wire is $25 \times 10^{-2} \Omega$.

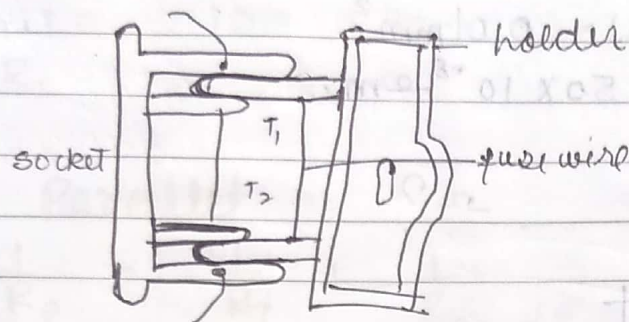Ques ii) What is a fuse and How does it work?
Ans. Fuse -




An electric fuse is a safety device consisting of a piece of thin wire of material having low melting point and high resistance, which melts and breaks the circuit if the current exceeds a safe value, hence preventing the electrical appliances in the circuit from getting damaged.

Working of fuse

1. Only when the fuse holder is inserted in fuse socket, the circuit of our domestic wiring is complete. So, under normal circumstances, the fuse wire is intact and electric current is available through wiring.
2. When a short circuit occurs, touching of live wire and neutral wire takes place or overloading occurs due to flow of extremely large current in circuit due to excessive use of electrical appliances at same time, the current in circuit exceeds the specified value to the which fuse wire gets heated up.

Ques iii: Draw the circuit diagram to verify ohm's law?

Sol

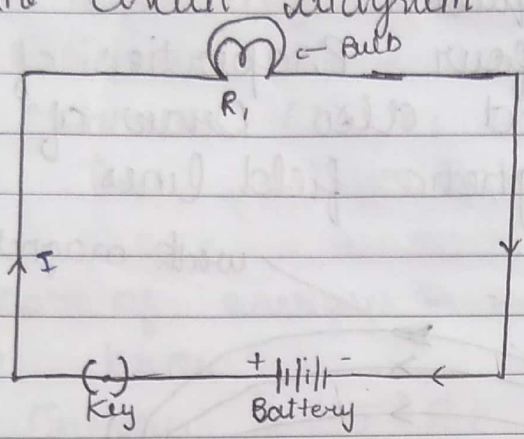

Symbol Naming
 +| | | - = Battery
 (.) = Key
 = Bulb
 I = Current

Acc. to Ohm's law the electric current flowing through a conductor is directly proportional to the potential diff. across its ends, provided the temp. and other physical conditions of conductor remain same.

$$V \propto I$$

$$V = IR$$

$$\frac{V}{I} = R \text{ Constant}$$

$$R = \frac{V}{I}$$

$$V = I \times R$$

V = Potential diff.

I = Electric Current

R = Resistance


$$I = \frac{V}{R}$$

(D) Long answer question.

Ques i) Write any four Properties of magnetic field lines and also Draw a diagram to show magnetic field lines.

Sol.

Diagram,

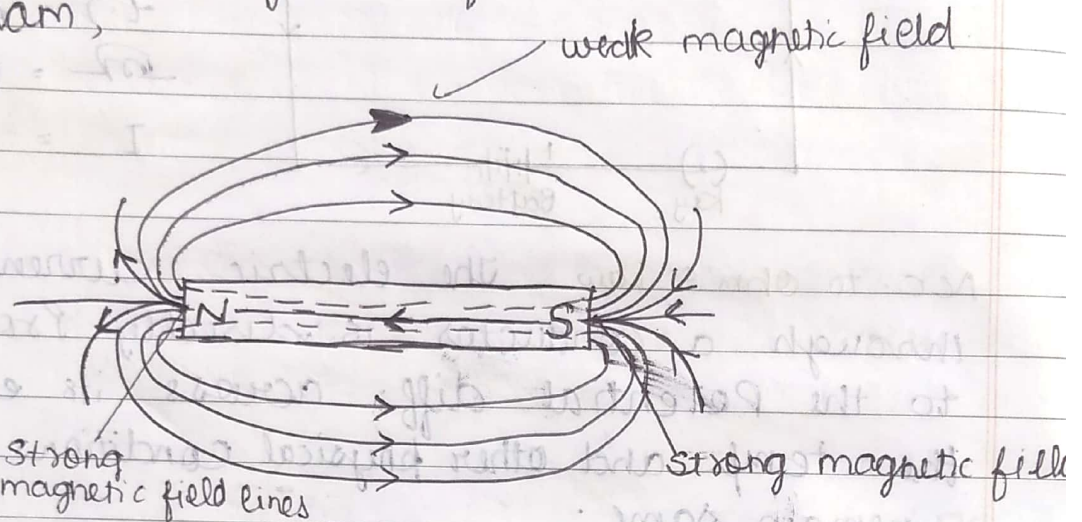

Properties of Magnetic field lines

1. Each Magnetic field line forms a closed curve.
2. The relative strength of Magnetic field shown by degree of closeness of field lines.
3. No two magnetic field lines can intersect each other.
4. The Magnetic field line emerges from north pole and merge at south pole.
5. Although magnetic field lines are not real, they represent a magnetic field which is real.

Ques ii)

sol(ii)

Given Quantity.

Resistance (R) = 20 Ω

Current (I) = 10A

Time (t) = 30hr.

Find.

cost of energy = — ₹

AS we know.

Energy = $I^2 R t$

= 10A × 10A × 20 × 3hr.

= 6KWH

A unit charge = ₹4.

6RWH charge is = 6 × 4

= ~~₹24~~ ₹24

One day cost of Heat oven is = ₹24

30 days cost of " " " " = 24 × 30

= ₹720.

★ Working of DC Motor.

- Let us assume the coil ABCD is initially in horizontal position. When switch is pressed current enters the coil through carbon brushes B₁ and split ring C₁. The flow of current direction BADC and it leaves through C₂ & B₂.
- The direction of current in side AB is from B to A and magnetic field North to South. Applying Fleming's left hand rule to side AB, force is downward perpendicular to plane of paper.
- The direction of current in side CD of coil is from D to C and direction of magnetic field is same again from N to S. By applying Fleming's left hand rule to side CD the force direction is upward perpendicular to plane of paper.
- These two equal, opposite and parallel forces acting on two sides of coil AB and CD form a torque. Due to this, side AB of coil is pushed down and side CD of coil is pushed up. This makes coil move in anticlockwise direction.
- During rotation when coil reaches vertical position, the brushes B₁ and B₂ lose contact with split ring C₁ & C₂ and current in coil is cut off. The coil continues its motion due to inertia of motion. It rotates until it covers a rotation of 180°.

6. In 180° position, the sides AB and CD are interchanged. As result, split ring C is now contact with B_2 and split ring A. Therefore, the current continuous to flow in the direction CPAB. According Fleming's left hand rule the coil AB is now experience a force in upward direction and Perpendicular to plane of paper whereas coil CD experience a force in upward direction and the coil CD experience force in downward direction.

Seen
23/11/18

7. The coil while rotating reaching vertical position. In this position, once again, the brushes and split rings lose contact with each other and current in coil cut off. The coil continue flow due to inertia of motion till it complete an angle of 360° one revolution.

8. This process is repeated again and again the coil continuous to rotate as long as current is passing through it. A wheel can be mounted the axle attached to rotating coil along axis.

SBG STUDY