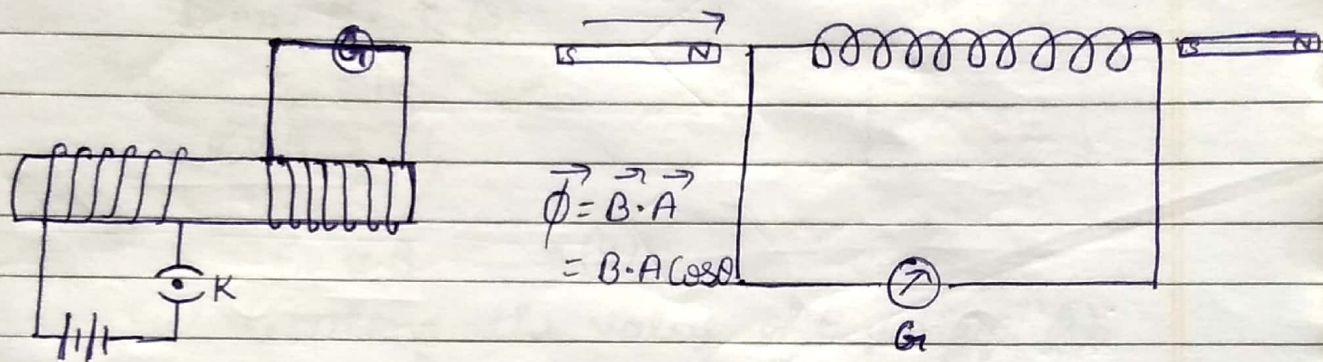


# SBG STUDY

## Chapter-6 Unit-4. Electromagnetic Induction & AC

### Faraday's Experiment:



### Faraday's Laws of electromagnetic induction:

It can be stated as follows:


First Law: Whenever the magnetic flux linked with a closed circuit changes, an emf (& hence a current) is induced in it which lasts only so long as the change in flux is taken place. This phenomenon is called electromagnetic induction.

Second Law: The magnitude of the induced emf is equal to the rate of change of magnetic flux linked with the closed circuit. Mathematically


$$|\mathcal{E}| = \frac{d\phi}{dt}$$

Lenz's Law: This law states that the direction of the induced current is such that it opposes the cause which produces it, i.e. it opposes the ~~cause which~~ change in magnetic field.

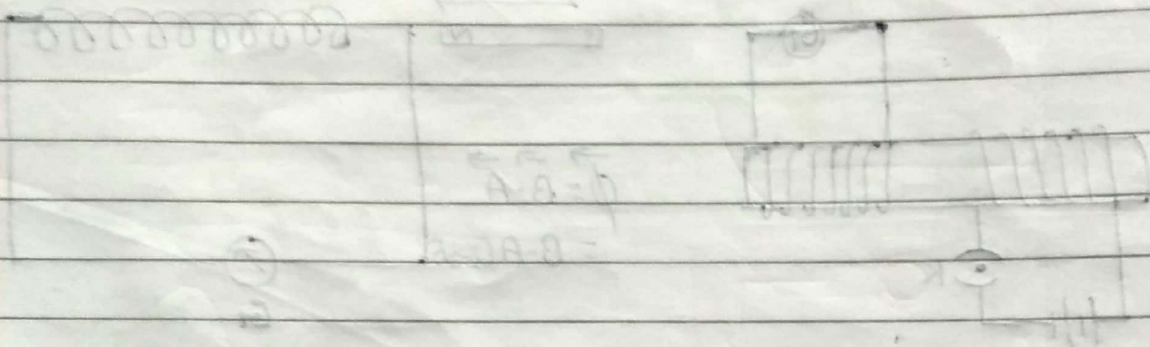To show that Lenz's Law is in agreement with the law of conservation of energy :-




Motional emf from Faraday's Law :-

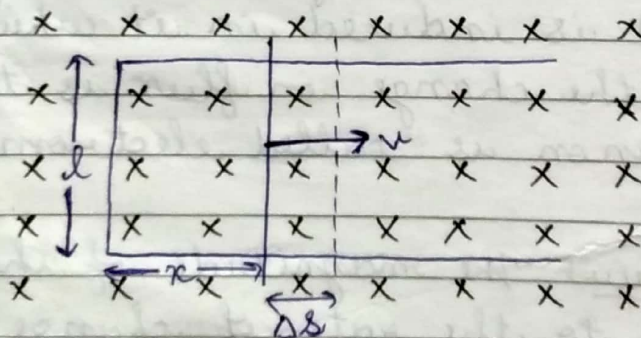

$$e = \frac{d\phi}{dt}$$

$$= \frac{-B \cdot \Delta A}{\Delta t} \Rightarrow \frac{-Bl \Delta x}{\Delta t}$$

$$e = -Blv$$

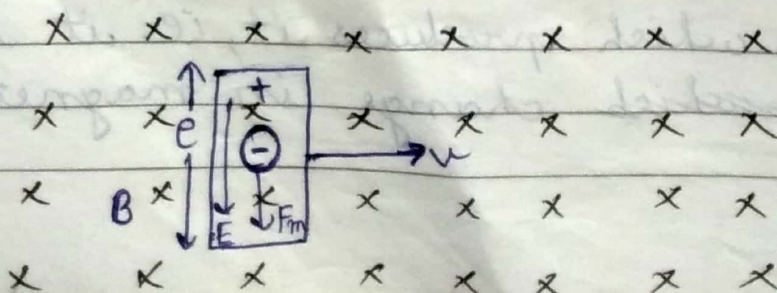

Work.

$$F_m = e v B \sin 90^\circ$$

$$F_m = e v B \rightarrow (1)$$

$$e = E l \rightarrow (2)$$

$$F_e = q E \rightarrow (3)$$

$$e = E l$$
  
$$F_e = q E$$

$$F_m = F_e$$
  
$$q v B = q E$$
  
$$E = v B$$

From (1) & (3)

$$F_m = F_e$$
  
$$q v B = q E$$

$$e = v B l$$

$$E = v B \rightarrow (4)$$

Substituting the value of E in eq. (2)

$$e = v B l$$

Relation between induced charge and change in magnetic flux:

$$|e| = \frac{d\phi}{dt}$$

$$i = \frac{\Delta q}{\Delta t} = \frac{e}{R}$$

$$\frac{\Delta q}{\Delta t} = \frac{\Delta \phi}{\Delta t} \cdot \frac{1}{R}$$

$$\Delta \phi = R \cdot \Delta q$$


$$\Delta A = \pi l^2$$

$$e = \frac{\Delta \phi}{\Delta t}$$

$$= \frac{B \Delta A}{\Delta t}$$

$$= \frac{B \pi l^2}{T}$$
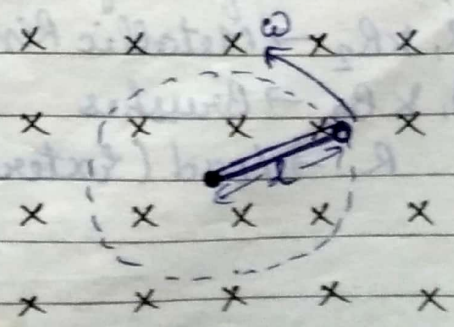
$$= \frac{B \pi l^2}{2\pi/\omega} \Rightarrow e = \frac{1}{2} B l^2 \omega \quad \therefore \left( \omega = \frac{\theta}{t} = \frac{2\pi}{T} \right)$$



# Methods of generating induced emf :-


## AC Generators:-

$$t = T/4 \quad S \rightarrow P$$

$$t = T/2 \quad 0$$

$$t = 3T/4 \quad P \rightarrow S$$

$$t = T \quad 0$$

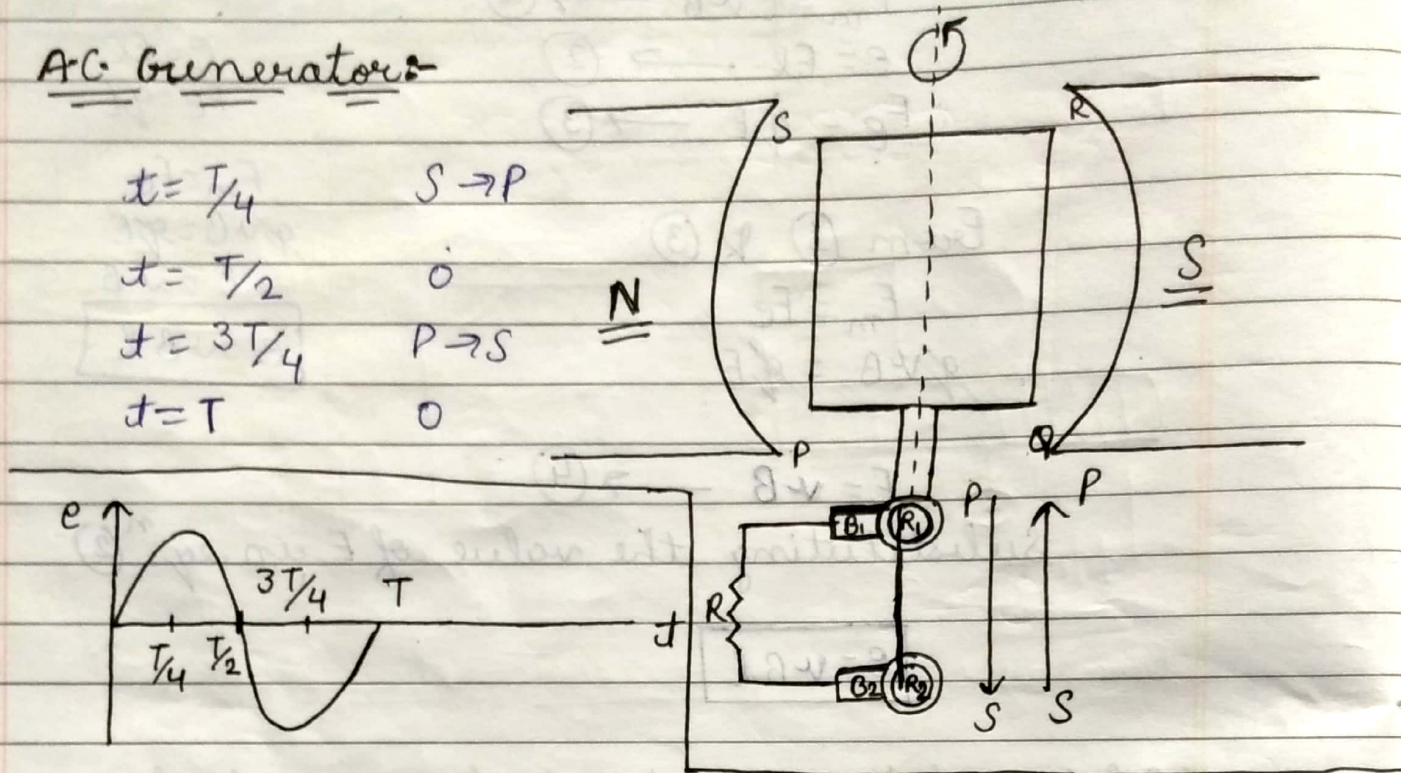

$$\omega = \frac{\theta}{T} \Rightarrow \theta = \omega t \rightarrow \textcircled{1}$$

$$\phi = NBA \cos \theta$$

$$\phi = NBA \cos \omega t$$

$$\frac{d\phi}{dt} = e = -NBA \omega \sin \omega t$$

$$e = NBA \omega \sin \omega t$$

$$e_0 = NBA \omega = e_{\text{max}}$$

$$\therefore e = e_0 \sin \omega t$$

$$\omega = \frac{\theta}{T}$$

$$\theta = \omega T$$

$$\phi = NBA \cos \theta$$

$$\phi = NBA \cos \omega t$$

$$\frac{d\phi}{dt} = e$$

$$e = -NBA \omega \sin \omega t$$

$$e = NBA \omega \sin \omega t$$

PQRS = coil

N, S = poles of magnets


R<sub>1</sub> & R<sub>2</sub> → Metallic Rings

B<sub>1</sub> & B<sub>2</sub> → Brushes

R → Load (external)
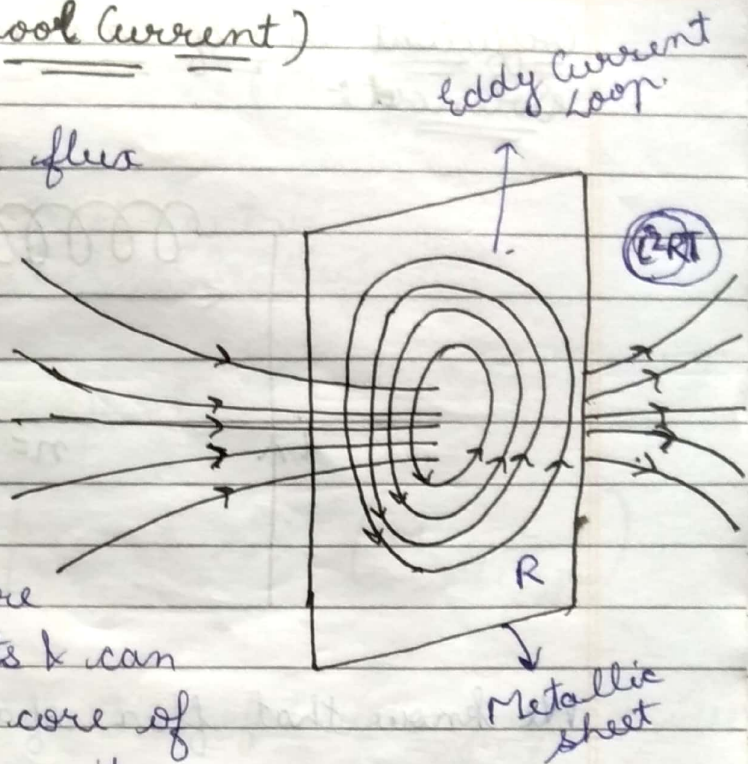
## Eddy Current :- (Whirlpool Current)

When change<sup>g</sup> magnetic flux is linked with a metallic shield or conductor then currents<sup>n</sup> are produced over the surface of conductor in the form of concentric loops. These ~~currents~~<sup>circuits</sup> are known as eddy currents & can be minimised in the core of transformers by making it laminated core. These current are unwanted current.




## Self Induction :-

It is the phenomenon of production of induced emf <sup>in a coil</sup> ~~than~~ a changing current passing ~~by~~ through it. <sub>when</sub>

$$\phi \propto i$$

$$\phi = Li, \quad L = \frac{\phi}{i}$$

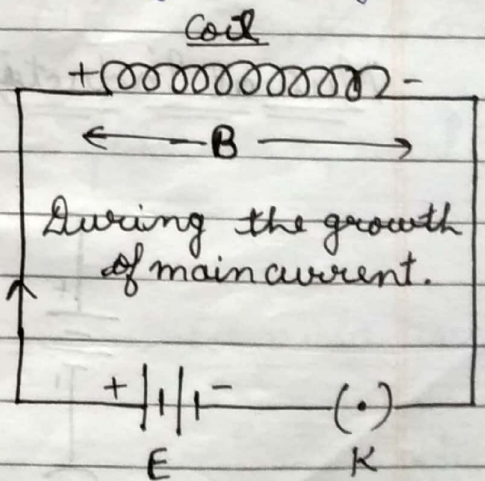→ Coefficient of self induction of a coil.




$$\frac{d\phi}{dt} = L \frac{di}{dt}$$

$$e = -L \frac{di}{dt}$$

$$L = \frac{-e}{di/dt}$$

SI unit of L is HENRY

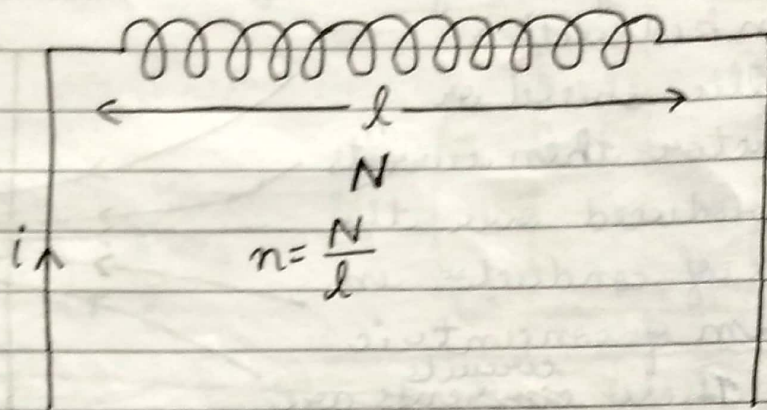Coefficient of self induction of a long straight Solenoid:



We know that flux of a coil,  $\phi = Li \rightarrow (1)$


$$\begin{aligned} \phi &= NBA \\ &= (nl)(\mu_0 ni)A \rightarrow (2) \end{aligned}$$

Equating (1) & (2)

$$Li = \mu_0 n^2 l A i$$

$$L = \mu_0 n^2 l A$$

Mutual Induction (M):

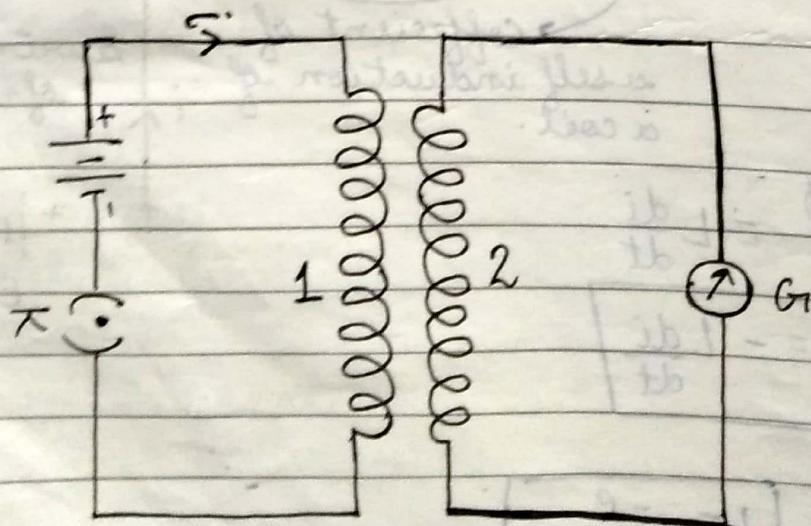

$$\phi_{21} \propto i_1$$

$$\therefore \left( M = \frac{\phi_{21}}{i_1} \right)$$

$$\phi_{21} = M i_1$$


→ Coefficient of Mutual Induction

$$\frac{d\phi_{21}}{dt} = M \frac{di_1}{dt}$$

$$e = M \frac{di_1}{dt}$$

$$\therefore \left( M = \frac{-e}{di/dt} \right)$$

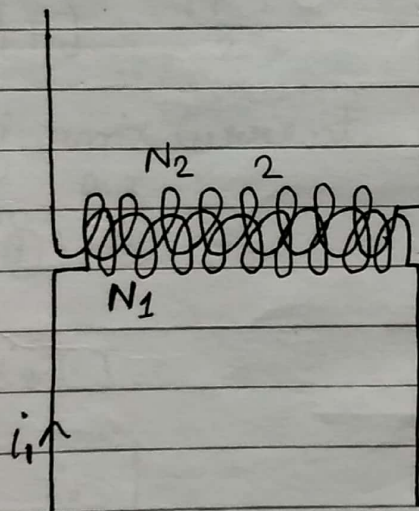Coefficient of Mutual Induction of two long solenoids:



$$\phi_{21} = M i_1 \rightarrow \textcircled{1}$$

$$\phi_{21} = N_2 B_1 A$$

$$= N_2 (\mu_0 n_1 i_1) A$$

$$\phi_{21} = (n_2 l) (\mu_0 n_1 i_1 A) \textcircled{2}$$

Equating eq.  $\textcircled{1}$  &  $\textcircled{2}$

$$M i_1 = \mu_0 n_1 i_1 A n_2 l$$

$$M = \mu_0 n_1 n_2 l A$$

Ex 36

(S.L. Aurora)

Ans.  $l = 30 \text{ cm} = 0.30 \text{ m}$

$A = 250 \text{ cm}^2 = 25 \times 10^{-4} \text{ m}^2, N = 500$

Formula used

$$e = -L \frac{di}{dt}$$

Alternating current :- ~~(After this topic)~~

Avg. value of A.C. =  $(I_m \times I_m)$

In case of ordinary current

$$dq = i dt$$

$$dq = i_0 \sin \omega t$$

$$\textcircled{1} \rightarrow i = I_m \sin \omega t$$

$$A = R \cdot i = R \cdot I_m \sin \omega t$$

$$A \cdot i = R \cdot I_m^2 \sin^2 \omega t$$

$$A \cdot i = R \cdot I_m^2 \sin^2 \omega t$$

$$\textcircled{2}$$

② x ①

$$A \cdot i = R \cdot I_m^2 \sin^2 \omega t$$

$$A \cdot i = R \cdot I_m^2 \sin^2 \omega t$$

Example

$$i = I_m \sin \omega t$$

$$A = 220 \text{ V}, R = 20 \text{ ohm}, N = 200$$



## RMS Value of AC :-

$$H/dH = \int_0^T i^2 R dt = \int_0^T i^2 \sin^2 \omega t R dt$$

$$= i_0^2 R \int_0^T \sin^2 \omega t dt$$

$$= i_0^2 R \int_0^T \left( \frac{1 - \cos 2\omega t}{2} \right) dt$$

$$= \frac{i_0^2 R}{2} \left[ \int_0^T 1 dt - \int_0^T \frac{\sin 2\omega t}{2\omega} dt \right]$$

$$= \frac{i_0^2 R}{2} \left[ T - \frac{1}{2\omega} \left[ \sin 2 \frac{2\pi}{T} T - \sin 2 \cdot \frac{2\pi}{T} \cdot 0 \right] \right]$$

$$= \frac{i_0^2 R}{2} [T] = \frac{i_0^2 R T}{2} \rightarrow \textcircled{1}$$

In case of rms current

$$H = i_{rms}^2 R \cdot T$$


Equating  $\textcircled{1} \times \textcircled{2}$

$$i_{rms}^2 R \cdot T = \frac{i_0^2 R T}{2}$$

$$i_{rms} = \frac{i_0}{\sqrt{2}}$$

$$i_v = 0.707 i_0$$


~~Virtual~~ Virtual Current

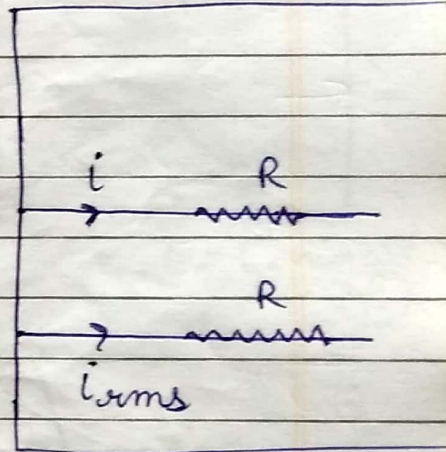
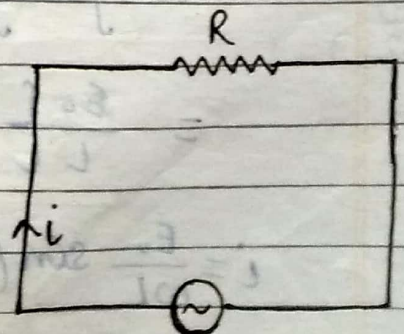
## A.C. Through a pure resistor :-

$$i = \frac{E}{R} = \frac{E_0 \sin \omega t}{R} = \frac{E_0}{R} \sin \omega t$$


$$= i_0 \sin \omega t \rightarrow \textcircled{2}$$





$$E = E_0 \sin \omega t \rightarrow \textcircled{1}$$

Comparing ① & ②, we conclude that Phase Diagram

$E$  and  $i$  remain in same phase.

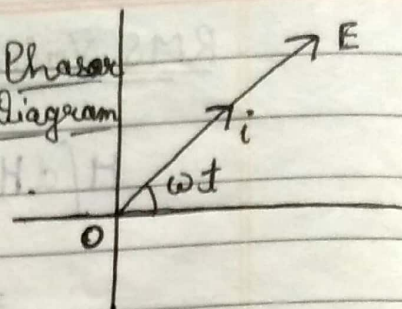

A.C. through pure inductor :-

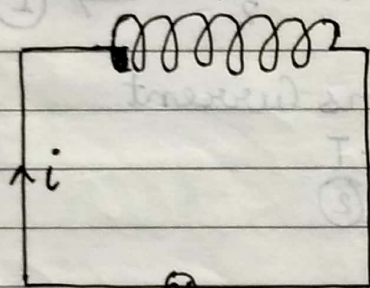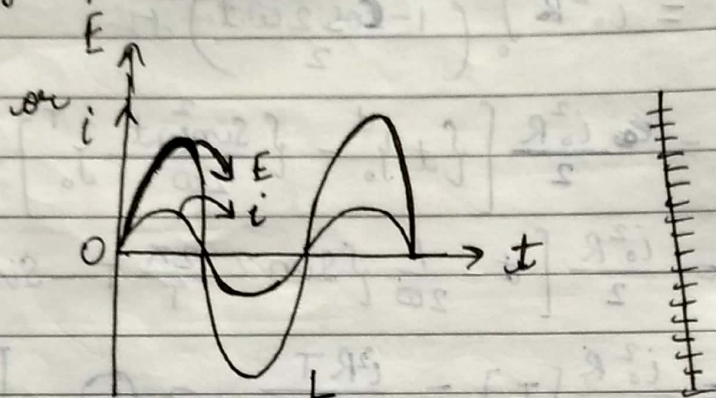

$$E = E_0 \sin \omega t \longrightarrow \textcircled{1}$$

$$E = L \frac{di}{dt}$$

$$E_0 \sin \omega t = L \frac{di}{dt}$$

$$di = \frac{E_0}{L} \sin \omega t dt$$


$$i = \int di = \int \frac{E_0}{L} \sin \omega t dt$$

$$= \frac{E_0}{L} \left[ -\frac{\cos \omega t}{\omega} \right]$$

$$i = \frac{E_0}{\omega L} \sin \left( \omega t - \frac{\pi}{2} \right) \longrightarrow \textcircled{2}$$

$\therefore$  We conclude that,  $E$  leads  $i$  by an angle of  $\frac{\pi}{2}$  in

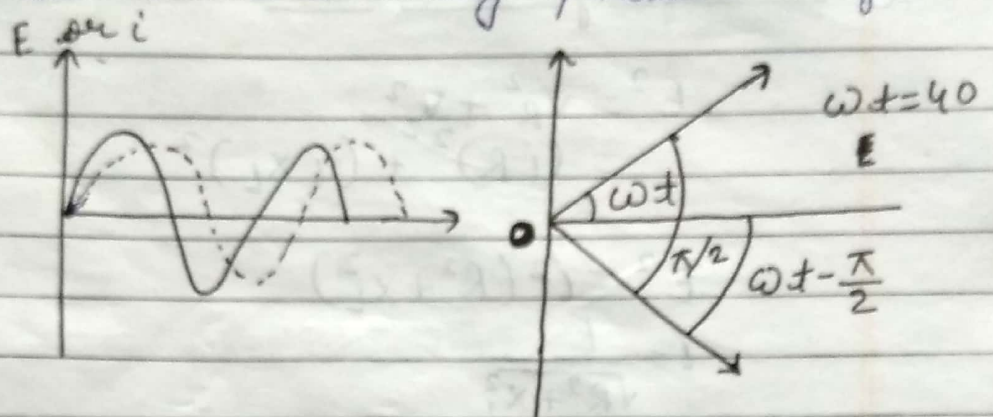phase which can be shown by phasor diagram





AC through pure Capacitor


$$q = CE = CE \cdot \sin \omega t$$

$$i = \frac{dq}{dt} = CE \cdot \omega \cos \omega t$$
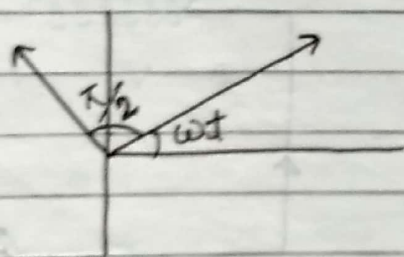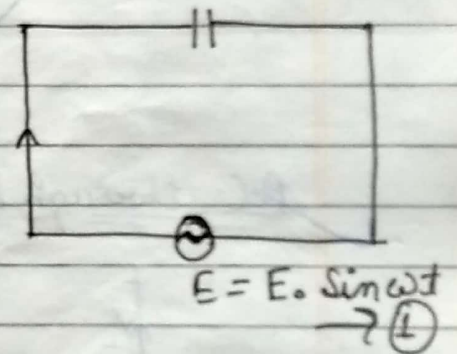
$$i = \frac{E}{(1/\omega C)} \sin(\omega t + \pi/2)$$



$$\rightarrow \textcircled{2}$$

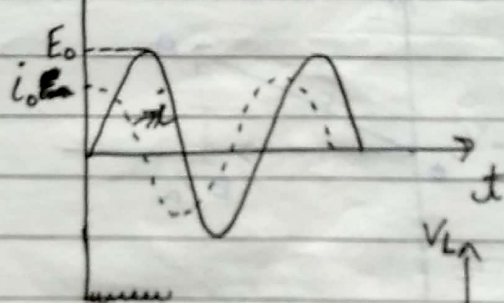


Comparing ① & ② we conclude that  
E lags behind by  $\frac{\pi}{2}$   
or i leads ahead by  $\frac{\pi}{2}$

$$X_L = \omega L$$

$$i = \frac{E_0}{\omega L} \sin(\omega t - \frac{\pi}{2})$$

$$X_C = \frac{1}{\omega C}$$
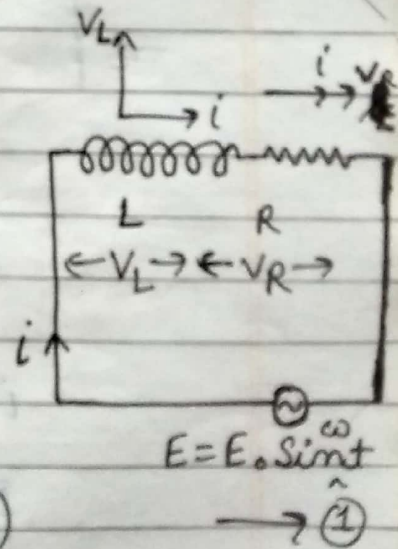
$$i = \frac{E_0}{1/\omega C} \sin(\omega t + \frac{\pi}{2})$$



Stays

A.C. through LR circuit :-

$$E^2 = V_R^2 + V_L^2$$

$$= (iR)^2 + (iX_L)^2$$

$$E^2 = i^2 (R^2 + X_L^2)$$



$$i = \frac{E}{\sqrt{R^2 + X_L^2}}$$

$$i = \frac{E}{Z}$$

where  $Z = \sqrt{R^2 + X_L^2}$

Impedance of LR circuit.

A.C. through LCR series circuit :-

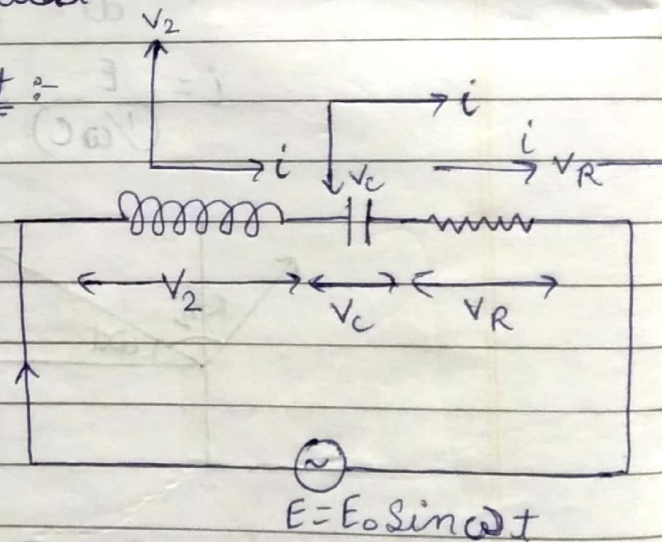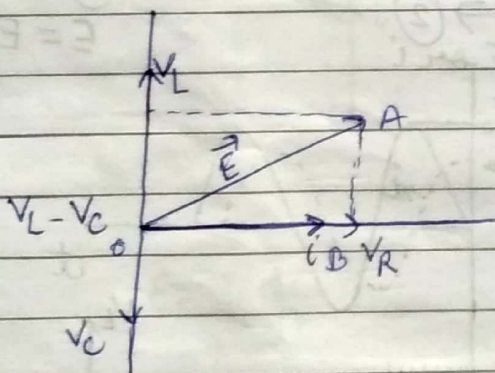

In  $\Delta OAB$

$$E^2 = V_R^2 + (V_L - V_C)^2$$

$$= (iR)^2 + [iX_L - iX_C]^2$$

$$E^2 = i^2 [R^2 + (X_L - X_C)^2]$$

$$i = \frac{E}{\sqrt{R^2 + (X_L - X_C)^2}}$$

$$i = \frac{E}{Z}$$

Impedance of

Q To find out the phase difference between  $E$  &  $i$ ?

Ans

$$\tan \phi = \frac{BA}{OA} = \frac{V_L - V_C}{V_R} = \frac{iX_L - iX_C}{iR} = \frac{X_L - X_C}{R}$$

$$\phi = \tan^{-1} \left( \frac{X_L - X_C}{R} \right)$$

$\therefore$  Where  $X_L = \omega L = 2\pi fL =$  Inductive reactance

$X_C = \frac{1}{\omega C} = \frac{1}{2\pi fC} =$  Capacitive reactance.

A.C through R.C circuit :



$$E^2 = V_C^2 + V_R^2$$

$$E^2 = (iX_C)^2 + (iR)^2$$

$$E = i\sqrt{R^2 + X_C^2}$$


$$i = \frac{E}{\sqrt{R^2 + X_C^2}}$$

$$i = \frac{E}{Z}$$

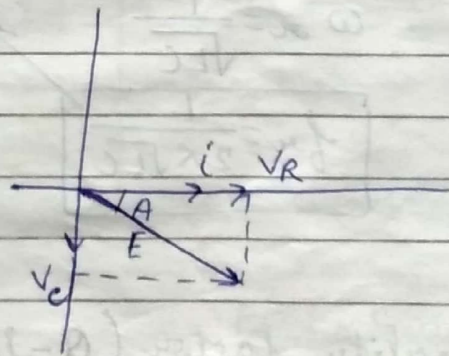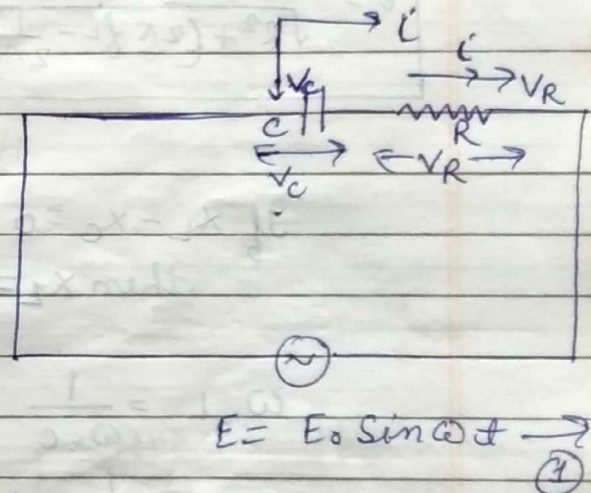

$$\tan \phi = \frac{V_C}{V_R} \Rightarrow \frac{iX_C}{iR} = \frac{X_C}{R} \Rightarrow \phi = \tan^{-1} \left( \frac{X_C}{R} \right)$$

Ex 21. (S.L. Arora.)

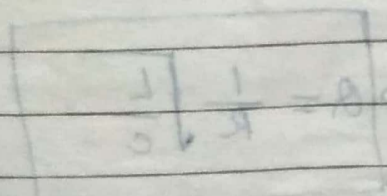


Resonance in LCR series circuit :-

$$i = \frac{E}{Z} = \frac{E}{\sqrt{R^2 + (X_L - X_C)^2}}$$

$$\tan \phi = \frac{V_L - V_C}{V_R} = \frac{X_L - X_C}{R}$$
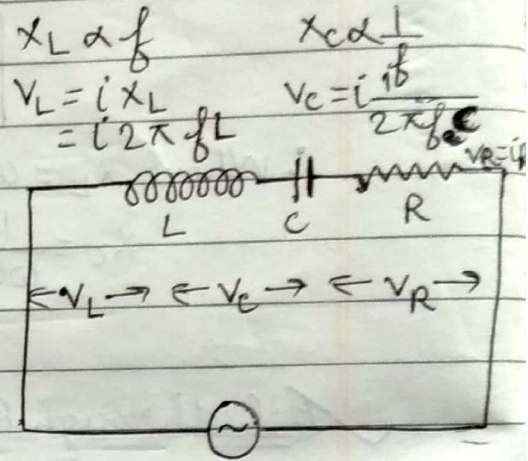
$$i = \frac{E}{\sqrt{R^2 + (2\pi fL - \frac{1}{2\pi fC})^2}}$$



If  $X_L - X_C = 0$   
then  $X_L = X_C$

$$E = E_0 \sin \omega t \rightarrow \text{①}$$

$$E = E_0 \sin 2\pi f t$$


$$E \propto \sin f$$

$$\omega_{xL} = \frac{1}{\omega_{xC}}$$

$$\omega_{x} = \frac{1}{\sqrt{LC}}$$

$$f_{x} = \frac{1}{2\pi\sqrt{LC}}$$

frequency of resonance

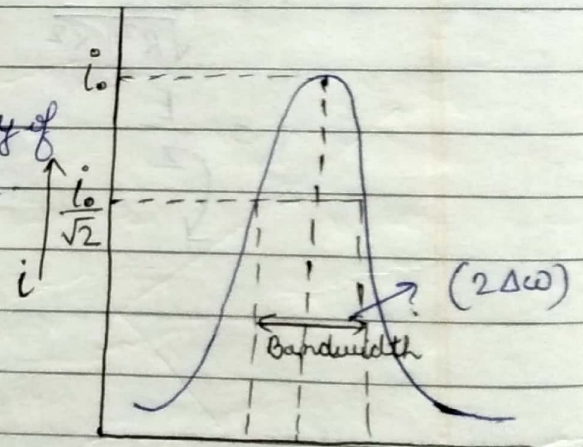

Quality factor (Q-factor) :-

$$Q = \frac{V_L \text{ or } V_C \text{ at resonance}}{V_R \text{ at resonance}}$$

$$= \frac{iX_L}{iR} = \frac{X_L}{R} = \frac{\omega_{xL}}{R}$$

$$= \frac{\frac{1}{\sqrt{LC}} \cdot L}{R}$$

$$\Rightarrow Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$\omega_1 \quad \omega_x \quad \omega_2$$

$$\omega_x = 2\pi f_x$$

Example

Q43. (SL Anura) Page no. 7-26.

Ans.  $I = 0.49 \text{ A}$

$E_{\text{rms}} = 220 \text{ V}$

$R = 400 \Omega$

$f = 50 \text{ Hz}$

$X_C = 200 \Omega$

(i)  $V_R = iR$

$V_C = iX_C = i \times 200$

(ii)  $X_L = X_C$


$2\pi fL = X_C$

$L = \frac{X_C}{2\pi f} = \frac{200 \times 7}{2 \times 22 \times 50} = 0.64 \text{ H}$

Power in AC LCR circuit:-

In one complete cycle

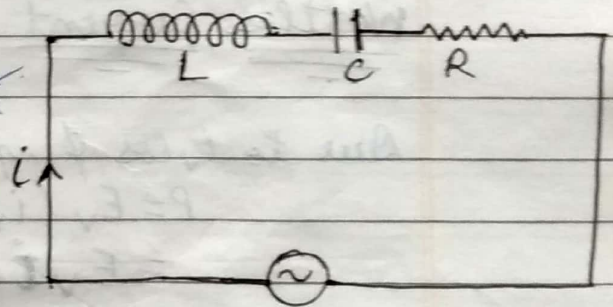~~$P = \frac{W}{T} = \frac{\int_0^T i^2 R dt}{T}$~~   
 ~~$= \frac{R}{T} \int_0^T i^2 dt$~~   
 ~~$= \frac{R}{T} \int_0^T i_0^2 \sin^2 \omega t dt$~~   
 ~~$= \frac{R i_0^2}{T} \int_0^T \sin^2 \omega t dt$~~



$E = E_0 \sin \omega t \rightarrow (1)$

$P = \frac{W}{T} = \frac{\int dW}{T} = \frac{1}{T} \int_0^T E i dt$

$= \frac{1}{T} \int_0^T E_0 \sin \omega t \cdot i_0 \sin(\omega t + \phi) dt$

$= \frac{E_0 i_0}{T} \int_0^T \sin \omega t \sin(\omega t + \phi) dt$

$= \frac{E_0 i_0}{T} \frac{T}{2} \cos \phi$  ----- on evaluating the integration.

$$P = \frac{E_0}{\sqrt{2}} \frac{i_0}{\sqrt{2}} \cos \phi$$

$$P = E_{rms} I_{rms} \cos \phi$$

where,

$$\cos \phi = \frac{VR}{E} = \frac{iR}{iZ} = \frac{R}{Z}$$

$$= \frac{R}{\sqrt{R^2 + (X_L - X_C)^2}}$$

Is called as Power factor.

Q. What is the value of power factor at the time of resonance?

Ans. ~~At resonance~~ At resonance  $\phi = 0 \therefore \cos \phi = 1$ .

Wattless Current :-

Due to  $i_v \cos \phi$ , power dissipated is

$$P = E_v (i_v \cos \phi) \cos 0$$


$$= E_v i_v \cos \phi \rightarrow \textcircled{1}$$

Again power dissipated due to

$i_v \sin \phi$

$$P = E_v (i_v \sin \phi) \cdot \cos 90^\circ$$

$$= 0$$

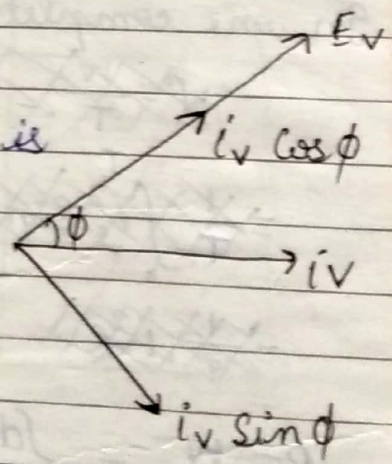

LC Oscillations :-



Transformer:

$$e_1 = N_1 \frac{d\phi}{dt}$$

$$e_2 = \frac{N_2 d\phi}{dt}$$

$$\frac{e_2}{e_1} = \frac{N_2}{N_1} \rightarrow (1)$$

For ideal transformer


$$P_1 = P_2$$

$$e_1 i_1 = e_2 i_2$$

$$\frac{e_2}{e_1} = \frac{i_1}{i_2} \rightarrow (2)$$


$$\frac{e_2}{e_1} = \frac{i_1}{i_2} = \frac{N_2}{N_1} = K$$

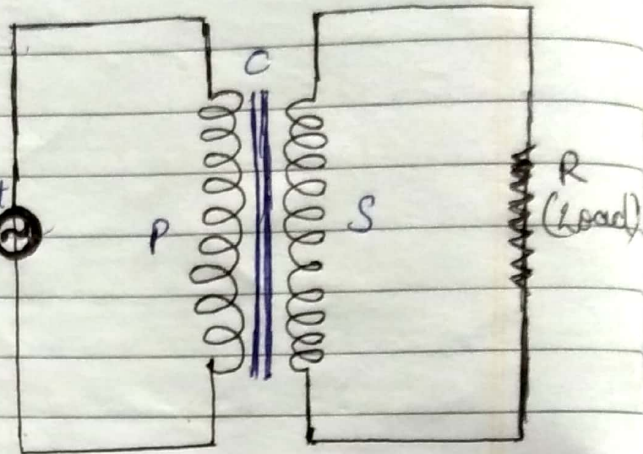Transformation Ratio  
 $K > 1$  step up,  $K < 1$  step down.



Q, no. ~~7.25~~ 7.25 (SL. Arora) Page no. 7.73.

Ans.

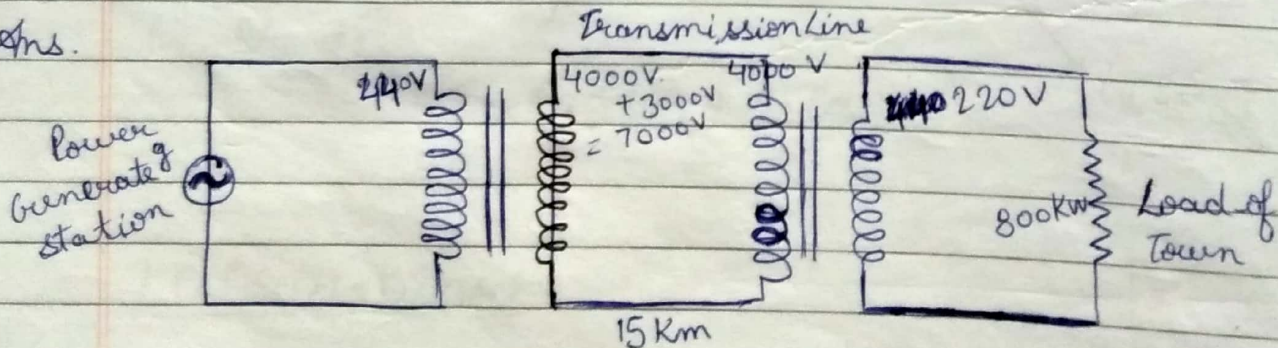

Length of wire line = 30 km

$$R = 0.5 \times 30$$

$$= 10 \Omega$$

Current flowing through transmission line

$$i = \frac{P}{V} = \frac{800 \times 10^3}{4000}$$

$$= 200 \text{ A}$$

Power lost by transmission line  
 $i^2 R = (200)^2 \times 15 \text{ W} = 600 \text{ kW}$

Potential drop across the transmission line  $= iR$   
 $= 200 \times 15$   
 $= 3000 \text{ V}$

$\therefore$  Rating or characteristics of transformers at the plant  $= 4000 + 3000 = 7000 \text{ V}$

Hence step up transformers at the plant is  
 $440 \text{ V} - 7000 \text{ V}$ .

Q. ex. 68. (S.L. Arora) Page no. 7.46.

Ans.  $E_1 = 220 \text{ V}$ ,  $E_2 = 22 \text{ V}$ ,  $Z_2 = 220 \Omega$

$$I_2 = \frac{E_2}{Z_2} = \frac{22}{220} = 0.1 \text{ A}$$

If there are no energy losses, then

Input power = Output power i.e.  $E_1 I_1 = E_2 I_2$

$$I = \frac{E_2 I_2}{E_1} = \frac{22 \times 0.1}{220} = 0.01 \text{ A}$$

Q. ex 69. (S.L. Arora) Page no. 7.46.

Ans.  $N_1 = 500$ ,  $N_2 = 1000$ ,  $E_1 = 200 \text{ V}$ ,  $R_2 = 100 \Omega$

$$E_2 = \frac{N_2}{N_1} E_1 = \frac{1000}{500} \times 200 = 400 \text{ V}$$

$$I_2 = \frac{E_2}{R_2} = \frac{4000}{1000} = 4 \text{ A}$$

# SBG STUDY

$$E_1 I_1 = E_2 I_2$$
$$I_1 = \frac{E_2 I_2}{E_1} = \frac{400 \times 4}{200} = 8 \text{ A.}$$

## Important Questions:

- Q1. What is the principle of meter bridge? How will you determine the resistance of a resistor.
- Q2. What is the principle of potentiometer?
- Q3. A cell is connected (EMF = 6V) across a resistance wire of length 600 cm. Assuming the internal resistance of cell to be zero. Calculate the potential gradient of the potentiometer. If a primary cell of unknown emf  $E$  is connected as shown in fig. Calculate the emf  $E$  of this test cell.
- Q4. Write the working of a cyclotron with the labelled diagram. State the principle also.
- Q5. With the help of a well labelled diagram explain the principle and working of a coil galvanometer. Write two important properties of the wire used for suspending the coil. What is radial magnetic field.

Fig. of Q3.

