

TEC-302

1171

Printed Pages : 4

Paper ID & Roll No. to be filled in your Answer Book

Roll No.

--	--	--	--	--	--	--	--	--	--

**B.Tech. II Year III Sem.
Odd Examination, 2015**

DIGITAL ELECTRONICS AND DESIGN ASPECT*Time: 3.00 Hours]**[Max. Marks: 100***Answer Any Four****(4x5=20)**

1.1 Convert the numbers into desired base

(a) $(A6BF5)_{16} = ()_2$

(b) $(101.01)_2 = ()_{10}$

(c) $(7.FD6)_{16} = ()_8$

1.2 Subtract $(1010)_2$ from $(1111)_2$ using 2's complements.
Subtract by direct method also and compare.1.3 Add the following BCD numbers (a)1001 and 0100 and
(b)00011001 and 000101001.4 Encode data bits 0101 into a 7-bit even parity hamming
code.

1.5 Simplify the Boolean function

$$F(A,B,C,D) = \sum_m(1,3,7,11,15) + \sum_d(0,2,5)$$

Answer Any Four

(4x5=20)

2.1 An 8-to-1 MUX has inputs A, B, C connected to the selection inputs S₂, S₁ and S₀ respectively. The data inputs D₀ through D₇, are as follows D₁=D₂=D₇=0, D₃=D₅=1, D₀=D₄=D, D₆= \bar{D} . Determine the Boolean expression that the MUX implements.

2.2 Show how a 16-input MUX is used to generate the function, $Y = \overline{ABCD} + BCD + \overline{ABC} + ABC\bar{D}$

2.3 What is race around condition? How is it avoided in master slave flip flop?

2.4 Explain Differences between PLA and PAL in detail.

2.5 Show the logic requires to convert a 10-bit gray code to binary and use the logic to convert the following gray code to binary (a) 1010000000 (b) 0011001100

Answer Any Two

(2x10=20)

3.1 Design a MOD -6 Counter using K-map.

3.2 What is a ripple counter? Why is it named so?

- 3.3 An 8-Mhz square wave clocks a 5-bit ripple counter. What is the frequency of the last flip flop? What is the duty cycle of this output waveform?

Answer Any Two (2x10=20)

- 4.1 Explain the parameters used to characterise logic families.
- 4.2 Give two advantages and one disadvantage of totem pole output arrangement.
- 4.3 Draw the circuit diagram of negative logic AND gate with 3 inputs.

Answer Any Two (2x10=20)

- 5.1 Explain static -1 and static -0 Hazard with one example
- 5.2 Explain one method for elimination of static hazard.
- 5.3 Differentiate between RAM and ROM. How many 16K x 1 RAMs are required to achieve a memory with word capacity of 16K and a word length of 8 bits?

—x—