

BECT – 303

Roll No

--	--	--	--	--	--	--	--	--	--

Odd Semester Examination, 2019-2020

B. TECH. (ECE/CSE ,SEMESTER- III)

DIGITAL ELECTRONICS

Time: 03:00 Hours

Max. Marks:100

Total no. of printed pages: 1

Note: Attempt all questions.

Q1. Attempt any four questions from the following :

4x5=20

- Convert following:
 - $(35614)_7 = ()_{12}$
 - $(100100111000.0111)_{BCD} = ()_{10}$
- $f(A,B,C,D,E) = \sum m(0, 1, 7, 9, 11, 13, 15, 16, 17, 23, 25, 27)$
- Sketch the following equation using one AND and one OR gate only:
 $Y = (A+B)(A+C)$
- Perform $(1011)_2 - (0100)_2$ using 1's complement method.
- Write short note on De Morgan's theorem.
- Encode the data bits 0101 into a seven bit even parity Hamming Code.

Q2. Attempt any four questions from the following :

4x5=20

- Design a full adder using two half adder.
- Implement a full adder using 8:1 multiplexer.
- Design four bit Priority Encoder.
- Implement the following function using 4 to16 line decoder.
 $f = \sum m(1,2,4,7,8,11,12,13)$
- Write short notes on PAL and PLA.
- Design a circuit for two bit magnitude comparator.

Q3. Attempt any two questions from the following :

2x10=20

- Design a S-R flip flop. Explain its applications and disadvantages.
- Explain the operation of 4 bit Ring counter. Also draw its timing diagram.
- What is race around condition? How it can be removed, explain.

Q4. Attempt any two questions from the following :

2x10=20

- Define the characteristics of logic families.
- Design a Two input NOR gate using CMOS. Also explain its parameters.
- Explain the working of TTL logic family.

Q5. Attempt any two questions from the following :

2x10=20

- What is meant by Hazard in a logic network? Discuss different types of Hazards.
- Draw circuit diagram of MOS dynamic RAM cell. Also explain its working.
- A 16x4 size memory is available. Expand its word size so as to obtain a 16x8 memory.