

TEC 301

Roll No.

--	--	--	--	--	--	--	--	--	--

ODD SEMESTER EXAMINATION 2019-20

B. TECH III SEM (Old Syllabus)

**ELECTRONIC DEVICES AND CIRCUITS**

[Total Marks: 100]

[3 HOURS]

Total no. of printed pages: 2

**Note: Attempt all the questions**  
**All questions carry equal marks**

- Q1.** Attempt any four parts of the following: (5\*4)
- Why are intrinsic semiconductors not suitable for applications in electronic devices?
  - What do you understand by miller indices? How is this obtained that describes a plane in a crystal?
  - Draw and explain the hysteresis curve of magnetic materials?
  - Copper has FCC structure, and the atomic radius is  $1.278 \text{ \AA}$ . Calculate the density of Copper crystal. The atomic weight of copper is 63.5 and Avogadro number is  $6.023 \times 10^{23}$ .
  - Explain paramagnetic and ferromagnetic materials in detail?
- Q2.** Attempt any four parts of the following: (5\*4)
- Explain the advantage of negative feedback in an amplifier?
  - Explain emitter follower with advantage and applications?
  - Discuss the role of Ebers moll model and hybrid pi model used for BJT.
  - Explain the h-parameter high-frequency model.
  - For a CE amplifier circuit with h-parameters  $h_{ie} = 23k\Omega$ ,  $h_{re} = 6 \times 10^{-4}$ ,  $h_{fe} = 50$ ,  $h_{oe} = 25 \text{ mA/V}$  and load resistance  $R_L = 4k \text{ ohm}$ , source resistance  $R_s = 10k \text{ ohm}$ . Compute  $A_v$ ,  $A_i$ ,  $R_i$  and  $R_o$ .
- Q3.** Attempt any two parts of the following: (10\*2)
- What is the relation between the transfer gain with feedback  $A_f$  and that would feedback  $A$ ? Define negative feedback. List the five characteristics of an amplifier which are modified by negative feedback.
  - Explain the working of Wein-bridge oscillator with a neat diagram and obtain the condition of oscillations. Discuss the frequency range limitation seen in various sine wave oscillators.
  - Draw the circuit and explain the operation of UJT oscillator? Write the advantage and disadvantage of this oscillator?
- Q4.** Attempt any two parts of the following: (10\*2)
- What is the multistage amplifier circuit? Show that the overall gain is given by the product of the gains of different stages.

- (b) Draw the circuit and explain the operation of the Darlington amplifier? Write the advantage and disadvantage of this amplifier? What is the bootstrapping in this amplifier?
- (c) Explain the working of Double Tuned voltage amplifier with a suitable diagram; the voltage Gain of a cascaded amplifier is 100 Db. Determine the value of the input signal if 20 v output is desired from this amplifier?

**Q5.** Attempt any two parts of the following: **(10\*2)**

- (a) Explain the operation of Astable multivibrator? Explain the Switching time and frequency of oscillation for this multivibrator?
  - (b) Explain monostable multivibrator as a frequency divider. Why is monostable multivibrator is called delay circuit?
  - (c) State the role of commutating capacitors in Bistable multivibrator. Explain the unsymmetrical triggering and symmetrical triggering of the Bistable multivibrator. Where are Bistable multi vibrator applied?
-