

TEC-301

59

Printed Pages : 4

Roll No. to be filled in your Answer Book

Roll No.

| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|
| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|

B.Tech

End Semester Examination Dec. 2014 (Semester: III)

Electronic Devices and Circuit

Paper ID:-410021

Time : Three Hours]

[Max. Marks : 100

Note: Attempt all questions, the marks assigned to each question is indicated at question itself.

Q.1. Attempt any FOUR :

5x4=20

- Design an astable multivibrator for output amplitude of 15 volts and square wave of 500Hz, use silicon transistors having $(h_{fe})_{min}=40$ for transistor, $R=140k\Omega$, $(I_c)_{sat}=6mA$ and $(V_{ce})_{sat}=0.2$ volt.
- What do you mean by tuned amplifier? Explain a single tuned inductively coupled transistor amplifier.
- Describe the crystal oscillator. What is the advantage of a crystal oscillator over an LC oscillator?
- Explain Hall Effect and give some applications of Hall Effect.
- What is the function of speed-up capacitor in a bistable multivibrator circuit?

- (f) State and briefly explain Barkhausen criterion of oscillation. Draw the circuit diagram of general oscillator.

Q.2. Attempt any FOUR :

5X4=20

- (a) What is the basic difference among the three types of multivibrators?
- (b) Explain "overall voltage gain of a multistage amplifier is less than the product of individual stages"
- (c) The lattice constant of a face-centered cubic lattice is $4.25 \frac{1}{n}$. Determine the
- Effective number of atoms per unit cell and
 - Volume density of atoms.
- (d) Explain the operation of transistor as an amplifier.
- (e) Give the h-parameter model for CE configuration. Also define each of the terms used.
- (f) Given $V_{CC} = V_{BB} = 5$ volt, $h_{fe} = 20$, $I_{CON} = 10$ mA and V_{BE} cut-off for transistor = -1 volt. Determine the values of R_1 , R_2 , R_3 , R_4 , R_{L1} and R_{L2} for a bistable-multivibrator.

Q.3. Attempt any TWO :

10x2=20

- (a) Draw the circuit of an emitter coupled differential amplifier and explain its working.
- (b) The h-parameters of a CE amplifier are as follows- $h_{ie} = 1100 \Omega$, $h_{re} = 2.5 \times 10^{-4}$, $h_{fe} = 50$, $h_{oe} = 24 \mu A/V$ if the load resistance $R_L = 10 k \Omega$ and source resistance $R_s = 1 k \Omega$, find the voltage and current gains. Derive the formula used.

- (c) What is Darlington amplifier? Write the main characteristics of it.

Q.4. Attempt any TWO :

10x2=20

- (a) Explain the principle of working of Wein bridge oscillator circuit. Explain why negative feedback in addition to the usual positive feedback is employed in Wein bridge oscillator.
- (b) Draw the small signal equivalent circuit of FET amplifier in CS connection and derive the equation of voltage gain and output resistance.
- (c) Define negative feedback and positive feedback. An amplifier with current feedback has following specifications: $h_{fe}=100\Omega$, $h_{ie}=2000\Omega$, $R_1=15000\Omega$, $R_2=5600\Omega$, $R_e=100\Omega$ and $R_L=470\Omega$ calculate the value of voltage gain and input resistance of the amplifier with and without feedback.

Q.5. Attempt any TWO :

10x2=20

- (a) Draw a neat circuit diagram of emitter-coupled monostable multivibrator. Explain its constructional features and operating principle.
- (b) In a transistor Colpitt's oscillator, $L=100\mu H$, $C_1=0.01\mu F$, $C_2=0.001\mu F$ and $C_c=10\mu F$. Determine
- (i) Operating frequency
 - (ii) Feedback fraction
 - (iii) Minimum gain to sustain oscillations
 - (iv) Emitter resistance R_e if $R_c=2.5k\Omega$

- (c) Distinguish between ferromagnetic, paramagnetic and diamagnetic materials, mentioning at least one example of each.

--X--