

BECT- 302

Roll No.

--	--	--	--	--	--	--	--	--	--

ODD SEMESTER EXAMINATION, 2019-20

B.Tech. (Semester- III)

ELECTRONIC MEASUREMENT AND INSTRUMENTATION**Total Marks: 100****Time: 3 Hours****Total no. of printed pages: 2**

Note: Attempt all questions. All questions carry equal marks.

1. Attempt any four parts:**5x4=20**

- What is Dynamic Response? Explain the various types of dynamic response. How are they differ from dynamic characteristics?
- A voltmeter has a range of 0-10 V. The true value of the measured voltage is 5V, while the read value is 5.95. What is the absolute error and relative error?
- Write the need of calibration and explain process of calibration.
- Distinguish between direct and indirect methods of measurement. Give examples to support your answer.
- What is the principle of working of magnetic recorders? Explain the recording process.
- Differentiate between accuracy and precision.

2. Attempt any four parts:**5x4=20**

- Compare features of digital and analog voltmeters based on advantages and applications.
- Write the different DSO applications.
- Derive an expression for the sensitivity of a Wheatstone bridge.
- Explain Series ohmmeter.
- Write a short note on PMMC instruments.
- Derive the inductance formula for Maxwell's bridge with suitable diagram.

3. Attempt any two parts:**10x2=20**

- (i) Draw the scheme of a Multi-range ammeter. Design a multi-range DC ammeter with an internal resistance 10Ω . The full scale deflection currents is 10mA and it is required to measure 0 to 50mA, 0 to 100mA and 0 to 250mA.

P.T.O

(ii) Bring out the difference between CRO and recorders. Draw the schematic of a simple X-Y recorder.

b) Explain the working of Digital Data Recording. Give its applications.

c) (i) Define the following with respect to the measuring system:

(1) True value

(2) Static correction

(3) Relative error

(4) Reproducibility

(ii) Explain the working of a True RMS voltmeter.

4. Attempt any two parts:

10x2=20

a) Define Sensitivity and deflection factor of a Cathode Ray Tube (CRT). What are the role of the following in CROs:

(i) Isolation Shield

(ii) Time base generator circuit

(iii) X-Channel

(iv) Triggered Sweep

b) A voltmeter having a sensitivity of 100V on its 150 V scale when connected across an unknown resistor in series with a mili-ammeter. When the mili-ammeter reads 5mA, Calculate

(i) apparent resistance of the unknown resistor.

(ii) actual resistance of the unknown resistor and

(iii) error due to the loading effect of voltmeter.

c) Explain D/A and A/D converters w.r.t signal conditioning of the inputs.

5. Attempt any two parts:

10x2=20

a) Explain the basic elements of a function generator. What is the importance of (i) Duty Cycle (ii) Rise time

b) (i) Explain with the help of a diagram the working of simple multimeter.

(ii) Explain an arrangement for the measurement of Standing Wave Ratio.

c) Draw a circuit diagram of Q-meter and explain its working. Give its applications.