

TEE-301 (ECE)

1281

Odd Semester Examination, 2017-18

B.TECH. (SEMESTER-III)

NETWORK ANALYSIS AND SYNTHESIS


Time: 03:00 Hours

Max Marks : 100

1. Attempt any four of the following :

[5X4]


- What is the fundamental loop matrix and how it is formed?
- Define the term: Tree, Co Tree, Tie set & cut set.
- Write the matrix node equation using the nodal analysis & the matrix loop equation using the loop analysis in graph theory.
- List the essential properties of a linear network system.
- For the graph shown in figure, consider the tree formed by branches (2, 3, 4), using this tree write A, B,

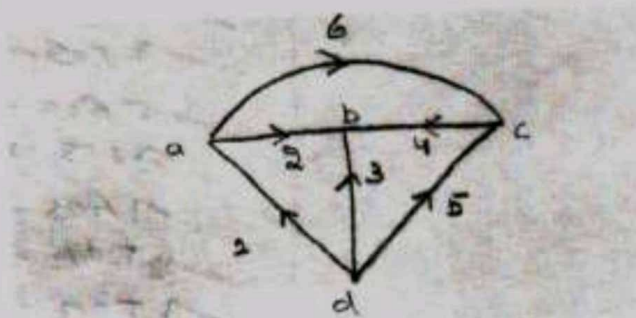

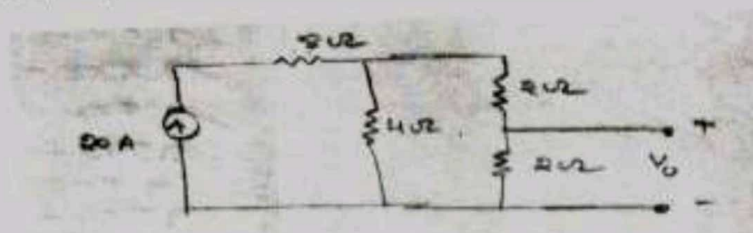
2. Attempt any four of the following :

[5X4]

- State and explain Thevenin's Theorem.
- Verify the reciprocity theorem for the circuit shown in the figure.



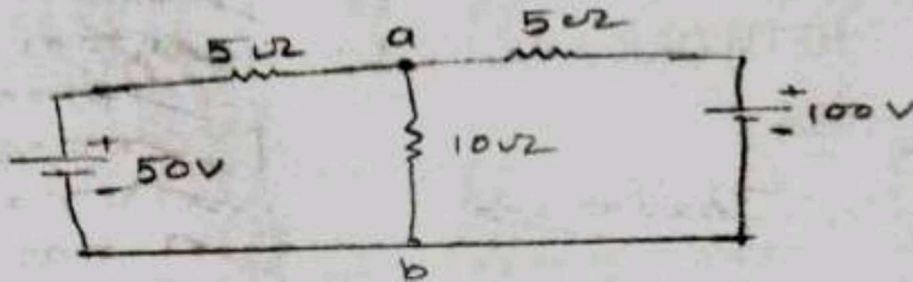- (c) What is maximum power transfer theorem and prove that the overall efficiency of circuit supplying maximum power is 50%.
- (d) Find the Norton equivalent across the point a-b




- (e) State and prove Millman's Theorem for ac voltage source.


[10X2]

3. Attempt any two of the following

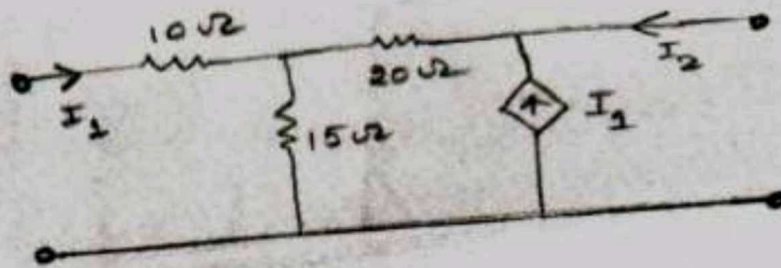
- (a) Obtain Z parameter of the network shown in fig whether the network shown is symmetrical or reciprocal or not.



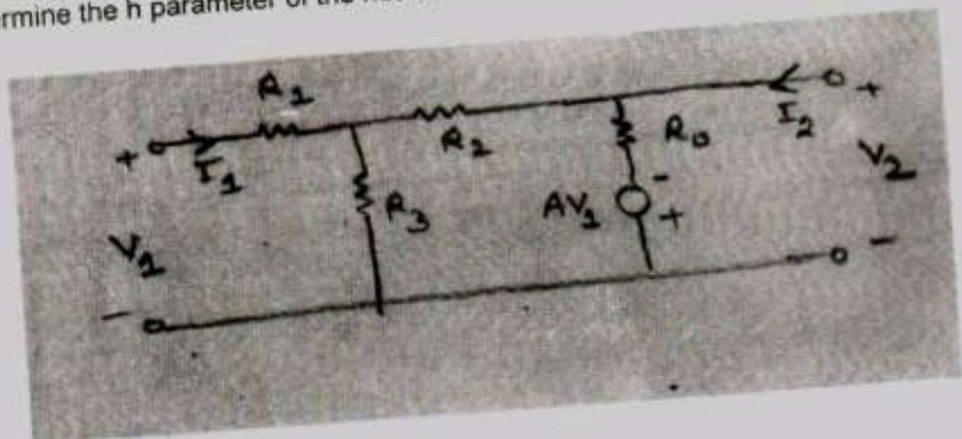- (b) Determine the h parameter of the network shown in fig.



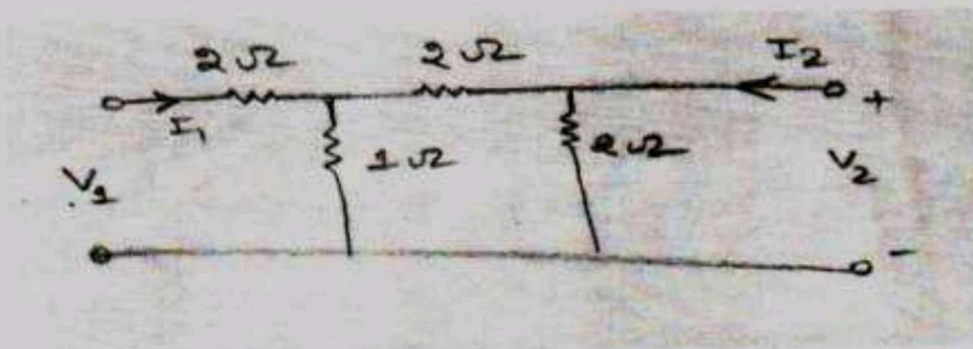(c) For the network shown in fig Calculate



- (i) Z parameters
- (ii) Y parameters
- (iii) ABCD parameters
- (iv) h parameters

4. Attempt any two of the following :

[10x2]

(a) Find the laplace transform of the function:

- (i) Impulse function
- (ii) Unit step function
- (iii) Ramp function
- (iv) Parabolic function

(b) Find the inverse laplace transform of the given function and draw the pole zero diagram

$$H(s) = \frac{s(s+1)}{(s+4)(s^2+6s+5)}$$

(c) Determine inverse laplace transform of the following function using convolution integral.

$$F(s) = F_1(s) \cdot F_2(s) = \frac{s+1}{s(s^2+4)}$$

5. Attempt **any two** of the following : [10x2]

- (a) For the network function given below: Synthesize in foster form one and cauer form one.

$$Y(s) = \frac{2(s+1)(s+3)}{(s+2)(s+4)}$$

- (b) An impulse is applied to the input of a system and the output is observed to be the time function e^{-2t} . Find the transform function of the system and check the stability of the system by pole zero plot.

- (c) Realize the following RC driving point impedance function in foster I form and cauer II form:

$$Z(s) = \frac{s^2 + 4s + 3}{s^2 + 4s}$$
