

TEE-301A

1219

Odd Semester Examination 2018-19

B.TECH. (EEE/EN) (SEMESTER-III)

NETWORK ANALYSIS AND SYNTHESIS

Time: 03:00 Hours

Max Marks : 100

Note:- Attempt all questions.

Q1. Attempt any four:

(4×5=20)

- a. Define incidence matrix and also write its properties.
- b. Differentiate between twig matrix and link matrix with a suitable example.
- c. Write the properties of RL driving point impedance function.
- d. What is frequency response?
- e. Write the concept of complex frequency.
- f. Differentiate between Ladder and Lattice network

Q2. Attempt any four:

(4×5=20)

- a. Define poles, zeros and pole zero plot.
- b. How the location of poles affects the system performance ?
- c. Define positive real function and mention its properties.
- d. What is the difference between network analysis and network synthesis ?
- e. Two identical sections of the network shown in Fig. 2e are cascaded. Determine T-parameter of the resulting network :

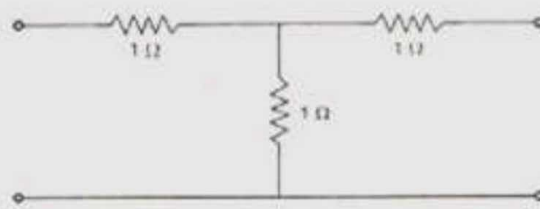


Fig 2.e

f. Write short note on the following term of networks :

- (i) Transfer function
- (ii) Inverse transform voltage ratio

Q3. Attempt any two:

(2×10=20)

a. Explain the following term:

- (i) Tree and co-tree
- (ii) Node and branch
- (iii) Twig and chord
- (iv) Incidence matrix
- (v) Tie set and cut set.

b. Determine the current I for the circuit as shown in Fig. 3b by using Millman's theorem :

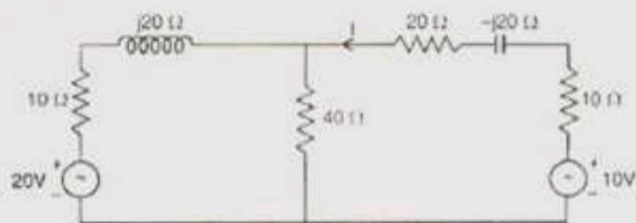


Fig. 3b

c. State and prove Tellegen's theorem with a suitable example.

Q4. Attempt any two:

(2×10=20)

- Derive transmission parameter in terms of open circuit and short circuit impedance of a two port network.
- Draw the graph and hence obtain the f-cut set for the given reduced incidence matrix A of graph :

$$A = \begin{bmatrix} 0 & 0 & 1 & 1 & 1 & 0 & -1 \\ 0 & 1 & 0 & 0 & -1 & 1 & 1 \\ -1 & 0 & -1 & 0 & 0 & -1 & 0 \end{bmatrix}$$

- Show the function $F(s) = s(3s+8) / (s+1)(s+3)$ represents an R-L impedance. Synthesize the impedance in foster-I form.

Q5. Attempt any two:

(2×10=20)

- Determine the Y-parameter for the network shown in Fig. 5a. Find its equivalent circuit using Y- parameter and find whether the network is (i) reciprocal (ii) symmetrical :

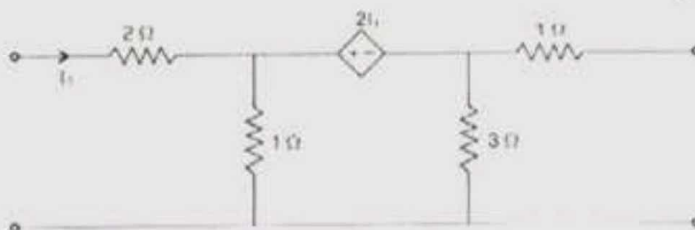


Fig. 5a

- What are the step to draw the Bode plot ?
- The current transform in a network is given by the expression, $I(s) = 5s / (s+1)(s+3)$. Draw its pole-zero plot and hence find the time domain response.

-----x-----