

TEE-603

63

Even Semester Examination 2017-18

B.TECH. (SEMESTER-VI)

POWER ELECTRONICS

Time: 03:00 Hours

Max Marks : 100

Note: All questions are compulsory.

1. Attempt any FOUR questions.

- (A) Draw and explain the V-I characteristics of SCR.
- (B) Explain various modes of operation of an SCR?
- (C) Discuss the turn on and turn off characteristics of an SCR.
- (D) Explain the operation of an SCR using two transistor model.
- (E) Draw the circuit symbol of various switches. Mention the characteristics of an ideal switch.
- (F) Discuss the constructional feature and operation of TRIAC?

2. Attempt any FOUR questions.

- (A) Explain the need of commutation in thyristor circuit. Discuss any class B commutation method with circuit diagram & wave form.
- (B) A step up chopper with dc source voltage = 240V, load resistance = 15Ω has a voltage drop of 3V across chopper switch. When the duty cycle is of 0.2, calculate
 - (a) Average output voltage
 - (b) RMS values of output voltage.

- (c) Chopper efficiency.
 - (d) Effective input resistance of chopper neglecting the switching loss
 - (C) What is dc chopper? Describe the working principle of boost converter.
 - (D) Discuss the difficulty faced during the parallel operation of an SCR. How the this problem is rectified.
 - (E) Describe the principle of dc step down chopper operation and derive their expression?
 - (F) Discuss various protection scheme of an SCR. How the low power gate drive circuit is protected from high power SCR circuit.
3. Attempt any two questions.
- (A) Discuss the effect of source inductance on the output voltage of a 3 phase full wave converter. Draw necessary waveform.
 - (B) Draw circuit diagram of 3 phase dual converter & explain its working in continuous current mode and discontinuous current mode of operation. How are the firing angles of both converters decided?
 - (C) Explain the operation of single phase full wave bridge converter for highly inductive load with the help of circuit diagram. A single phase full converter bridge connected to RLE type load. The source voltage is 220V, 50 Hz. The average load current of 10A is constant over working range. For $R=0.4\Omega$ and $L=2\text{mH}$, compute
 - (a) Range of firing angle delay when $E=110\text{V}$
 - (b) Average output voltage when firing angle is 80° .
4. Attempt any two questions
- (A) How 1 phase full wave mid point type converter is different from 1 phase full wave bridge type converter. Describe the operation of 1-ph two pulse mid-point

converter with relevant voltage and current waveform for continuous conduction and discontinuous conduction?

(B) Sketch output voltage waveform for a 3-ph to 3-ph cycloconverter for a firing angle delay of 30° and also obtain their expression for converter?

(C) Describe the effect of source inductance on the performance of a 3-ph full converter with waveform?

5. Attempt any two questions

(A) A single phase full bridge inverter may be connected to a load consisting of (a) R (b) RL load (c) RLC underdamped. For all these loads, draw the load voltage & load current waveform under steady operating conditions. Discuss the nature of these waveforms.

(B) Explain the working of voltage source inverter in 120° mode of operation?

(C) What is current source inverter, describe a single phase capacitor-commutated CSI connected to load R with help of power circuit diagram and waveform for getting signals, load current, capacitor voltage, input voltage, voltage across one thyristor.

----- x -----