

TEC-602

263

Even Semester Examination 2017-18

B.TECH (SEMESTER-VI)

V L S I CIRCUIT DESGN

Time: 03:00 Hours

Max Marks : 100

Note: Attempt ALL question. All Question carry equal marks.

Q1. Attempt any four parts of following:

(5x4=20)

- (A) Explain the threshold voltage of a MOS device and explain its significance?
- (B) What are the advantages of BICMOS technology over CMOS technology?
- (C) Explain the fabrication steps for CMOS using Twin Tub technology?
- (D) Explain the VLSI design flow and explain each block?
- (E) Explain electrical properties of MOS and derive various equations for it.?
- (F) What is pass transistor? Explain with suitable example also implement Half adder circuit by NMOS Pass Transistor logic?

Q2. Attempt any four parts of following:

(5x4=20)

- (A) Derive expression of power dissipation in CMOS Inverter?
- (B) Explain Lambda design rule and its physical significance in VLSI domain?
- (C) Derive expression for pull-up to pull-down ratio for NMOS inverter driver by another NMOS inverter?
- (D) $F = \{A.(D+E)+B.C\}'$ Realize this function using CMOS technology?

- (E) Discuss the architecture and advantages of FPGA? What are the different type of Xilinx FPGA?
- (F) Describe the channel length modulation in the MOSFET?

Q3. Attempt any two parts of following:

(10x2=20)

- (A) Derive DC Characteristic of CMOS Inverter? Derive its Voltage and current equation?
- (B) Explain the concept of Pipelining and Timing issues in VLSI Circuit?
- (C) Implement NAND and NOR gate having two input with CMOS logic?

Q4. Attempt any two parts of following:

(10x2=20)

- (A) Implement BCD to gray code converter using PLA?
- (B) Explain the operation of 6-Transistor SRAM with proper circuit diagram? Also write difference between DRAM & SRAM?
- (C) Define the term Controllability and Observability for VLSI circuits with examples?

Q5. Attempt any two parts of following:

(10x2=20)

- (A) Discuss briefly testing and verification of VLSI Circuits?
- (B) Explain in details Built in self-Testing (BIST) for circuit testing in VLSI?
- (C) What do you mean by electrical logical Stuck-at-0 & stuck-at-1 faults, explain with suitable examples?

----- X -----